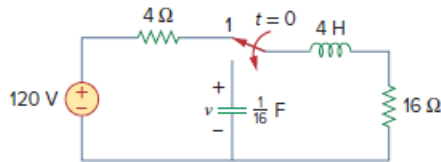


Problem

The switch in Fig. 16.77 has been in position 1 for $t < 0$. At $t = 0$, it is moved from position 1 to the top of the capacitor at $t = 0$. Please note that the switch is a make before break switch; it stays in contact with position 1 until it makes contact with the top of the capacitor and then breaks the contact at position 1. Determine $v(t)$.

Figure 16.77:



Step-by-step solution

Step 1 of 5

Refer to circuit diagram in Figure 16.77 in the textbook.

The switch has been in position 1 for $t < 0$. Thus, the circuit will remain in the steady state in position 1 and the inductor connected will be replaced by a short circuit.

Redraw the circuit as shown in Figure 1.

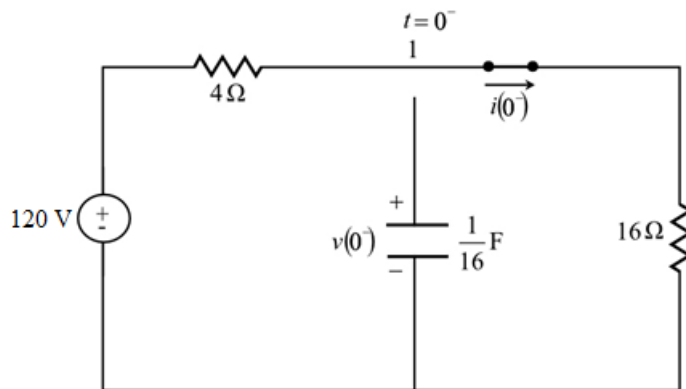


Figure 1

Step 2 of 5

Apply Kirchhoff's voltage law in Figure 1.

$$4i(0^-) + 16i(0^-) = 120$$

$$20i(0^-) = 120$$

$$i(0^-) = \frac{120}{20}$$

$$= 6 \text{ A}$$

Since the capacitor is disconnected from the circuit, the voltage across the capacitor at $t = 0^-$ is zero, that is,

$$v(0^-) = 0 \text{ V}$$

Step 3 of 5

At $t = 0$, the switch is connected to the capacitor branch. Replace the circuit by its s-domain equivalent for this connection as shown in Figure 2.

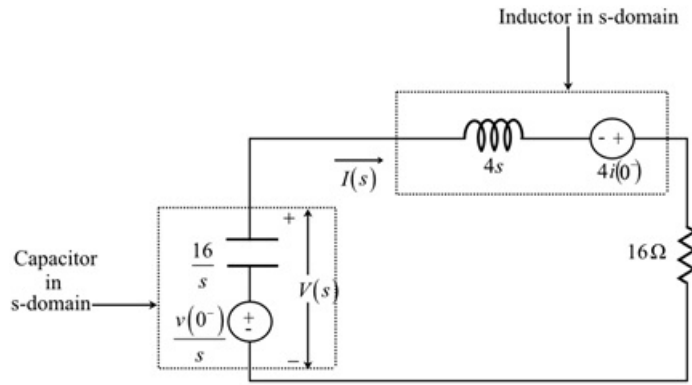


Figure 2

Step 4 of 5

Apply Kirchhoff's voltage law in Figure 2.

$$-\frac{v(0^-)}{s} + \left(\frac{16}{s} + 4s + 16\right)I(s) - 4i(0^-) = 0$$

Substitute 6 A for $i(0^-)$ and 0 V for $v(0^-)$.

$$-\frac{0}{s} + \left(\frac{16}{s} + 4s + 16\right)I(s) - (4)(6) = 0$$

$$\left(\frac{16 + 4s^2 + 16s}{s}\right)I(s) = 24$$

$$I(s) = \frac{6s}{s^2 + 4s + 4}$$

Step 5 of 5

Calculate $V(s)$ from Figure 2.

$$V(s) = \left(\frac{16}{s}\right)[-I(s)] - \frac{v(0^-)}{s}$$

Substitute $\frac{6s}{s^2 + 4s + 4}$ for $I(s)$ and 0 V for $v(0^-)$.

$$\begin{aligned} V(s) &= \left(\frac{16}{s}\right)\left(-\frac{6s}{s^2 + 4s + 4}\right) - 0 \\ &= -\left(\frac{16}{s}\right)\left(\frac{6s}{(s+2)^2}\right) \\ &= -\frac{96}{(s+2)^2} \end{aligned}$$

Apply inverse Laplace transform.

$$v(t) = -96te^{-2t}u(t) \text{ V}$$

Therefore, the value of $v(t)$ is $\boxed{-96te^{-2t}u(t) \text{ V}}$.