

Problem

(a) Find the Laplace transform of the voltage shown in Fig. 16.80(a). (b) Using that value of $v_s(t)$ in the circuit shown in Fig. 16.80(b), find the value of $v_o(t)$.

Figure 16.80(a):


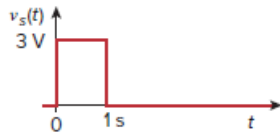


Figure 16.80(b):

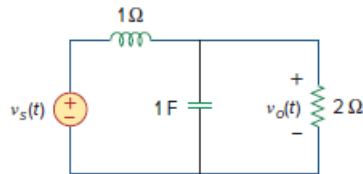

Step-by-step solution

Step 1 of 3

(a)

Refer to Figure 16.80(a) in the textbook.

The voltage $v_s(t)$ is defined as follows:

$$v_s(t) = 3u(t) - 3u(t-1)$$

Take the Laplace transform of $v_s(t)$ as follows:

$$L\{v_s(t)\} = L\{3u(t)\} - L\{3u(t-1)\}$$

$$V_s = 3L\{u(t)\} - 3L\{u(t-1)\}$$

Since $L\{u(t)\} = \frac{1}{s}$ and $L\{u(t-1)\} = \frac{e^{-s}}{s}$, therefore,

$$\begin{aligned} V_s(s) &= 3\left(\frac{1}{s}\right) - 3\left(\frac{e^{-s}}{s}\right) \\ &= \frac{3}{s}(1 - e^{-s}) \end{aligned}$$

Hence, the Laplace transform of $v_s(t)$ is $\boxed{\frac{3}{s}(1 - e^{-s})}$.

Step 2 of 3

(b)

Refer to Figure 16.80(b) in the textbook.

The inductor is shown with value 1Ω . Thus, consider it as a resistor with value 1Ω .

In s -domain, the impedance of 1 F capacitor is $\frac{1}{s}$.

Redraw the circuit as shown in Figure 1.

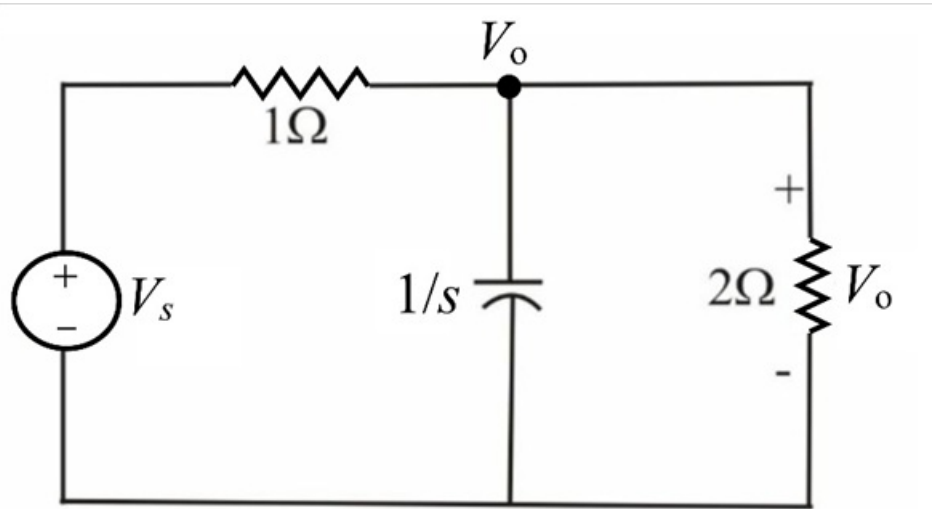


Figure 1

Step 3 of 3

Apply Kirchhoff's current law at node V_o .

$$\frac{V_o - V_s}{1} + \frac{V_o}{\left(\frac{1}{s}\right)} + \frac{V_o}{2} = 0$$

$$(1 + s + 0.5)V_o = V_s$$

$$V_o = \frac{V_s}{(s + 1.5)}$$

Substitute $\frac{3}{s}(1 - e^{-s})$ for V_s .

$$\begin{aligned} V_o &= \frac{3}{s(s + 1.5)}(1 - e^{-s}) \\ &= \frac{3}{s(s + 1.5)} - \frac{3}{s(s + 1.5)}e^{-s} \\ &= \left(\frac{2}{s} - \frac{2}{s + 1.5}\right) - \left(\frac{2}{s} - \frac{2}{s + 1.5}\right)e^{-s} \end{aligned}$$

Calculate the inverse Laplace transform of V_o as follows:

$$\mathcal{L}^{-1}\{V_o\} = \mathcal{L}^{-1}\left\{\left(\frac{2}{s} - \frac{2}{s + 1.5}\right) - \left(\frac{2}{s} - \frac{2}{s + 1.5}\right)e^{-s}\right\}$$

Since,

$$\mathcal{L}^{-1}\left\{\frac{1}{s}\right\} = u(t)$$

$$\mathcal{L}^{-1}\left\{\frac{1}{s + 1.5}\right\} = e^{-1.5t}u(t)$$

$$\mathcal{L}^{-1}\left\{\frac{e^{-s}}{s}\right\} = u(t - 1)$$

$$\mathcal{L}^{-1}\left\{\frac{e^{-s}}{s + 1.5}\right\} = e^{-1.5(t-1)}u(t - 1)$$

Therefore,

$$v_o(t) = (2 - 2e^{-1.5t})u(t) - (2 - 2e^{-1.5(t-1)})u(t - 1) \text{ V}$$

Hence, the value of $v_o(t)$ is $\boxed{(2 - 2e^{-1.5t})u(t) - (2 - 2e^{-1.5(t-1)})u(t - 1) \text{ V}}$.