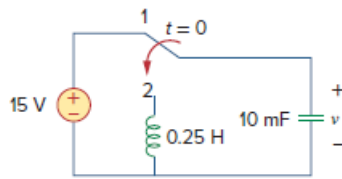


Problem

The switch in Fig. 16.87 moves from position 1 to position 2 at $t = 0$. Find $v(t)$, for all $t > 0$.

Figure 16.87:



Step-by-step solution

Step 1 of 2

Capacitor at $t = 0^+$ behaves like a short circuit and at $t = \infty$ it behaves like an open circuit.

Inductor at $t = 0^+$ acts like an open circuit and at $t = \infty$ acts like a short circuit.

Infinite amount of time switch is at position "1" capacitor voltage and inductor current cannot change instantaneously.

$$v(0^-) = v(0^+) = 15 \text{ V}$$

$$i_L(0^-) = i_L(0^+) = 0 \text{ A}$$

With initial values the switch is at position "2" at $t = 0$ sec.

Step 2 of 2

Apply the Kirchhoff's voltage law.

$$\frac{-15}{s} - \frac{I(s)}{s(0.01)} - 0.25sI(s) = 0$$

$$I(s) = \frac{-(15/s)}{\left[\frac{100}{s} + 0.25s\right]}$$

$$= \frac{-15}{[100 + 0.25s^2]}$$

Determine the expression for the voltage $v(s)$.

$$v(s) = \frac{15}{s} + \frac{I(s)}{s(0.01)}$$

$$= \frac{15}{s} + \frac{(-15)100}{s(100 + 0.25s^2)}$$

$$= \frac{15}{s} - \frac{1500}{s(0.25)\left(s^2 + \frac{100}{0.25}\right)}$$

$$= \frac{15}{s} - \frac{6000}{s(s^2 + 400)}$$

$$= \frac{(60/8)}{s - j20} + \frac{(60/8)}{s + j20}$$

$$= \frac{7.5}{s - j20} + \frac{7.5}{s + j20}$$

Applying inverse Laplace transform.

$$v(t) = 7.5 \left(\frac{e^{j20t} + e^{-j20t}}{2} \right) \times 2u(t)$$

$$= 15 \cos(20t)u(t) \text{ V}$$

Hence the voltage across the capacitor is $15 \cos(20t)u(t) \text{ V}$.