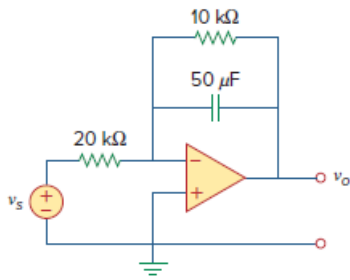


Problem

For the op amp circuit in Fig. 16.89, find $v_o(t)$ for $t > 0$. Take $v_s = 12 e^{-5t} u(t)$ V.

Figure 16.89:



Step-by-step solution

Step 1 of 2

Refer to Figure 16.89 in the text book.

Determine the feedback impedance of the circuit.

$$\begin{aligned} Z_F(s) &= \left(\frac{1}{sC} \right) \parallel R \\ &= \frac{\left(\frac{1}{sC} \right) R}{\frac{1}{sC} + R} \\ &= \frac{R}{1 + sCR} \end{aligned}$$

Substitute $10 \text{ k}\Omega$ for R and $50 \text{ }\mu\text{F}$ for C .

$$\begin{aligned} Z_F(s) &= \frac{10000}{1 + s(10000)(50 \times 10^{-6})} \\ &= \frac{10000}{1 + 0.5s} \\ &= \frac{20000}{s + 2} \end{aligned}$$

Step 2 of 2

Express the source voltage in Laplace domain.

$$V_s(s) = \frac{12}{s+5}$$

Determine the output voltage expression.

$$\begin{aligned} V_o(s) &= -\frac{Z_F(s)}{20 \text{ k}\Omega} V_s(s) \\ &= -\left(\frac{\frac{20000}{s+2}}{20000} \right) \left(\frac{12}{s+5} \right) \\ &= -\left(\frac{12}{(s+2)(s+5)} \right) \\ &= \frac{4}{s+5} - \frac{4}{s+2} \end{aligned}$$

Apply inverse Laplace transform.

$$v_o(t) = 4(e^{-5t} - e^{-2t})u(t)$$

Thus, the expression of $v_o(t)$ is $\boxed{4(e^{-5t} - e^{-2t})u(t)}$.