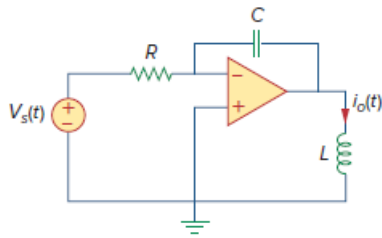


Problem

For the op-amp circuit in Fig. 16.99, find the transfer function, $T(s) = I(s)/V_s(s)$. Assume all initial conditions are zero.

Figure 16.99:



Step-by-step solution

Step 1 of 5

Refer to Figure 16.99 in the textbook.

Transform the circuit in Figure 16.99 to frequency domain.

The Laplace transform of $v_s(t)$ is $V_s(s)$ and $i_o(t)$ is $I(s)$.

The Laplace transform of inductance L is sL

The Laplace transform of capacitance C is $\frac{1}{sC}$

Assume that the all the initial conditions for the circuit should be zero.

Step 2 of 5

The frequency domain circuit is shown in Figure 1.

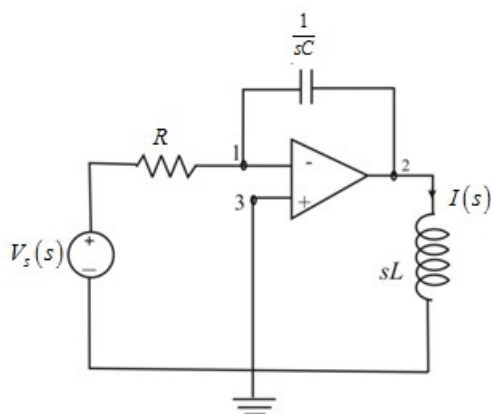


Figure 1

Step 3 of 5

Assume voltage at node 1 is $V_1(s)$, voltage at node 2 is $V_2(s)$, voltage at node 3 is $V_3(s)$.

Apply Kirchhoff's current law at node 1.

$$\frac{V_1(s) - V_s(s)}{R} + \frac{V_1(s) - V_2(s)}{1/sC} = 0$$

$$V_1(s) \left[\frac{1}{R} + sC \right] - sCV_2(s) = V_s(s) \left[\frac{1}{R} \right] \dots\dots (1)$$

$$V_1(s) \left[\frac{1}{R} + sC \right] - sCV_2(s) = V_s(s) \left[\frac{1}{R} \right]$$

Step 4 of 5

Use virtual ground concept, which is the voltage at positive terminal is equal to voltage at negative terminal, if negative feedback is provided in the circuit.

Therefore, voltage at node 3 is equal to voltage at node 1 and voltage at node 3 is equal to zero volts.

$$V_3(s) = 0 \text{ V}$$

$$V_1(s) = V_3(s)$$

$$V_1(s) = 0 \text{ V}$$

Substitute 0 V for $V_1(s)$ in equation (1).

$$(0) \left[\frac{1}{R} + sC \right] - sCV_2(s) = V_s(s) \left[\frac{1}{R} \right]$$

$$V_s(s) \left[\frac{1}{R} \right] = -sCV_2(s)$$

$$V_2(s) = -\frac{V_s(s)}{sRC}$$

Step 5 of 5

The voltage at node 2 is calculated by using Ohm's law in Figure 1.

$$V_2(s) = sLI_o(s) \dots\dots (2)$$

Substitute $-\frac{V_s(s)}{sRC}$ for $V_2(s)$ in equation (2).

$$sLI_o(s) = -\frac{V_s(s)}{sRC}$$

$$\frac{I_o(s)}{V_s(s)} = -\frac{1}{RLCs^2}$$

Therefore, the transfer function $T(s)$ is $\boxed{-\frac{1}{RLCs^2}}$.