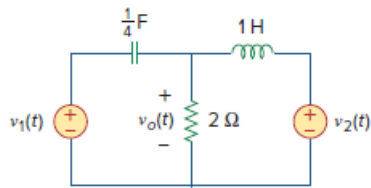


Problem


Develop the state equations for the circuit shown in Fig. 16.102.

Figure 16.102:



Step-by-step solution

Step 1 of 2

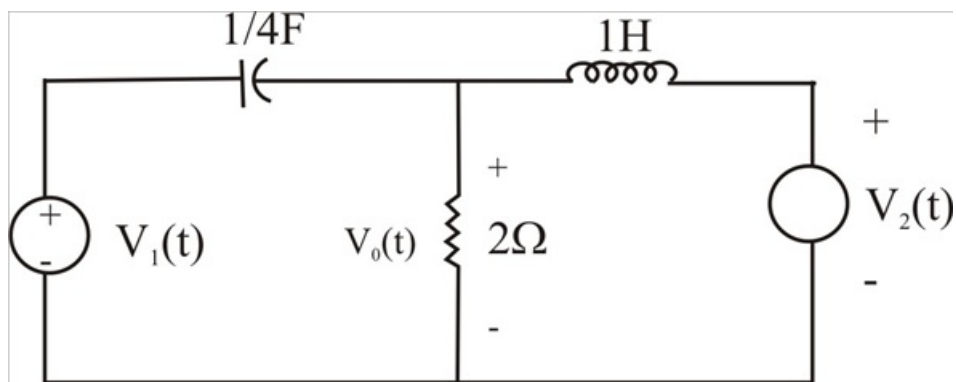

Step 2 of 2

First select the Inductor current i_L current flowing left to *RIGHT* and capacitor voltage V_C (Voltage positive on left and negative on right) to be state variables.

Applying KCL we get;

$$\frac{-V_C'}{4} + \frac{V_o}{2} + i_L' = 0; V_C' = 4i_L' + 2V_o$$

$$i_L' = V_o - V_2; V_o = -V_C + V_L$$

$$V_C' = 4i_L' - 2V_C + 2V_1; i_L' = -V_C + V_1 - V_2$$

$$\begin{bmatrix} i_L' \\ V_C' \end{bmatrix} = \begin{bmatrix} 0 & -1 \\ 4 & -2 \end{bmatrix} \begin{bmatrix} i_L \\ V_C \end{bmatrix} + \begin{bmatrix} 1 & -1 \\ 2 & 0 \end{bmatrix} \begin{bmatrix} V_1(t) \\ V_2(t) \end{bmatrix}$$

$$V_o(t) = \begin{bmatrix} 0 & -1 \end{bmatrix} \begin{bmatrix} i_L \\ V_C \end{bmatrix} + \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} V_1(t) \\ V_2(t) \end{bmatrix}$$