


Problem

It is desired to realize the transfer function

$$\frac{V_2(s)}{V_1(s)} = \frac{2s}{s^2 + 2s + 6}$$

using the circuit in Fig. 16.108. Choose $R = 1 \text{ k}\Omega$ and find L and C .

Figure 16.108:

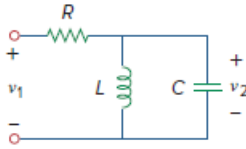

Step-by-step solution

Step 1 of 2

$$SL \parallel \frac{1}{SC} = \frac{SL \cdot \frac{1}{SC}}{SL + \frac{1}{SC}} = \frac{SL}{1 + S^2 LC}$$

$$\frac{V_2}{V_1} = \frac{\frac{SL}{1 + S^2 LC}}{R + \frac{SL}{1 + S^2 LC}} + \frac{SL}{S^2 RLC + SL + R}$$

$$\frac{V_2}{V_1} = \frac{S \cdot \frac{1}{RC}}{S^2 + \frac{S}{RC} + \frac{1}{LC}}$$

Step 2 of 2

Comparing this with the given transfer function,

$$2 = \frac{1}{RC} \quad 6 = \frac{1}{LC}$$

$$\text{If } R = 1 \text{ k}\Omega \quad C = \frac{1}{2R} = 500 \mu\text{F}$$

$$L = \frac{1}{6C} = 333.3 \text{ H}$$