


Problem

Synthesize the transfer function

$$\frac{V_o(s)}{V_{in}(s)} = \frac{10^6}{s^2 + 100s + 10^6}$$

using the topology of Fig. 16.111. Let $Y_1 = 1/R_1$, $Y_2 = 1/R_2$, $Y_3 = sC_1$, $Y_4 = sC_2$. Choose $R_1 = 1 \text{ k}\Omega$ and determine C_1 , C_2 , and R_2 .

Figure 16.111:

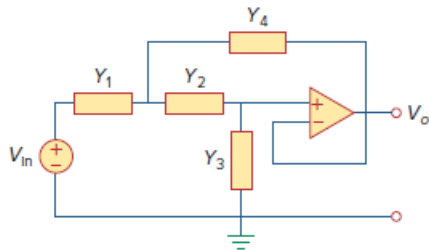


Step-by-step solution

Step 1 of 4

Consider the circuit shown below, we notice that
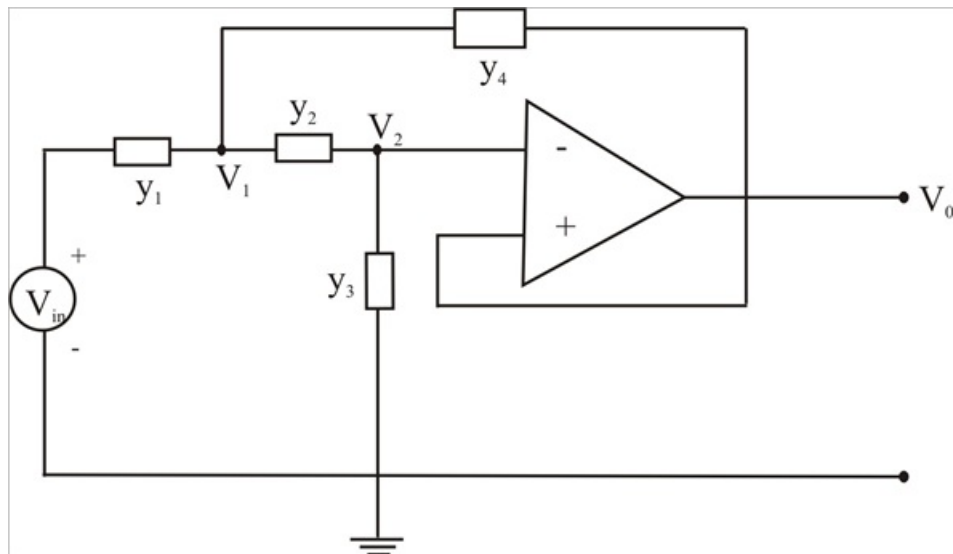
$$V_3 = V_o \quad \text{and} \quad V_2 = V_3 = V_o$$



Step 2 of 4

At node 1,

$$(V_{in} - V_1)Y_1 = (V_1 - V_o)Y_2 + (V_1 - V_o)Y_4$$

$$V_{in}Y_1 = V_1(Y_1 + Y_2 + Y_4) - V_o(Y_2 + Y_4) \quad -(1)$$

At node 2,

$$(V_1 - V_o)Y_2 = (V_o - 0)Y_3$$

$$V_1Y_2 = (Y_2 + Y_3)V_o$$

$$V_{12} = \frac{Y_2 + Y_3}{Y_2}V_o \quad -(2)$$

Step 3 of 4

Substituting (2) in to (1)

$$V_{in}Y_1 = \frac{Y_2 + Y_3}{Y_2}(Y_1 + Y_2 + Y_4)V_O - V_O(Y_2 + Y_4)$$

$$V_{in}Y_1Y_2 = V_O(Y_1Y_2 + Y_2^2 + Y_2Y_4 + Y_1Y_3 + Y_2Y_3 + Y_3Y_4 - Y_2^2 - Y_2Y_4)$$

$$\frac{V_O}{V_{in}} = \frac{Y_1Y_2}{(Y_1Y_2 + Y_1Y_3 + Y_2Y_3 + Y_3Y_4)}$$

Y_1 and Y_2 must be resistive, while Y_3 and Y_4 must be capacitive

$$\text{let } Y_1 = \frac{1}{R_1} \quad Y_2 = \frac{1}{R_2} \quad Y_3 = sC_1 \quad Y_4 = sC_2$$

$$\frac{V_O}{V_{in}} = \frac{\frac{1}{R_1R_2}}{\frac{1}{R_1R_2} + \frac{sC_1}{R_1} + \frac{sC_1}{R_2} + s^2C_1C_2}$$

Step 4 of 4

$$\text{Choose } R_1 = 1K\Omega \quad \text{then } \frac{1}{R_1R_2C_1C_2} = 10^6 \quad \text{and } \frac{R_1 + R_2}{R_1R_2C_2} = 100$$

We have three equations and four unknowns. Thus there is a family of solutions, one such solution is

$$R_2 = 1K\Omega \quad C_1 = 50\mu F \quad C_2 = 20\mu F$$