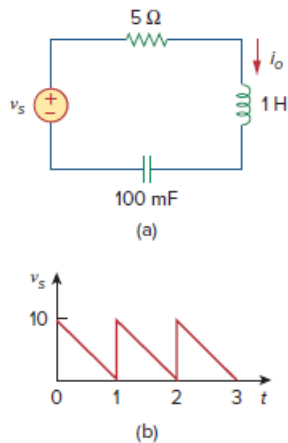


Problem

Find the response i_o for the circuit in Fig. 17.72(a), where $v_s(t)$ is shown in Fig. 17.72(b).

Figure 17.72:



Step-by-step solution

Step 1 of 6

Refer to Figure 17.36 in the textbook for the circuit and waveform.

From the waveform, the time period is, $T = 1 \text{ s}$.

Therefore, the angular frequency is,

$$\begin{aligned}\omega_0 &= \frac{2\pi}{T} \\ &= \frac{2\pi}{1} \\ &= 2\pi \text{ rad/s}\end{aligned}$$

Express the periodic voltage waveform in Fourier series. Write the general expression of the Fourier series.

$$v_s(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t) \dots\dots (1)$$

Here, a_0 , a_n , and b_n are coefficients of Fourier series.

Calculate the value of the Fourier coefficient a_0 of Fourier series.

$$\begin{aligned}a_0 &= \frac{1}{T} \int_0^T v_s(t) dt \\ &= \frac{1}{1} \int_0^1 10(1-t) dt \\ &= 10 \left[t - \frac{t^2}{2} \right]_0^1 \\ &= 10 \left[1 - \frac{1}{2} \right] \\ &= 5\end{aligned}$$

Step 2 of 6

Calculate the value of the Fourier coefficient a_n of Fourier series.

$$\begin{aligned}a_n &= \frac{2}{T} \int_0^T v_s(t) \cos n\omega_0 t dt \\&= \frac{2}{1} \int_0^1 10(1-t) \cos n(2\pi)t dt \\&= 20 \int_0^1 (1-t) \cos 2\pi n t dt \\&= 20 \left[\frac{1}{2\pi n} \sin 2\pi n t - \frac{1}{4\pi^2 n^2} \cos 2\pi n t - \frac{t}{2\pi n} \sin 2\pi n t \right]_0^1 \\&= 20 \left[-\frac{1}{4\pi^2 n^2} + -\frac{1}{4\pi^2 n^2} \right] \\&= 0\end{aligned}$$

Step 3 of 6

Calculate the value of the Fourier coefficient b_n of Fourier series.

$$\begin{aligned}b_n &= \frac{2}{T} \int_0^T v_s(t) \sin n\omega_0 t dt \\&= \frac{2}{1} \int_0^1 10(1-t) \sin n\omega_0 t dt \\&= 20 \int_0^1 (1-t) \sin n\omega_0 t dt \\&= 20 \left[-\frac{1}{2n\pi} \cos(2n\pi t) - \frac{1}{4n^2\pi^2} \sin(2n\pi t) + \frac{t}{2n\pi} \cos(2n\pi t) \right]_0^1 \\&= 20 \left[-\frac{1}{2n\pi} - 0 + \frac{1}{2n\pi} - \left(-\frac{1}{2n\pi} - 0 + 0 \right) \right] \\&= 20 \left[\frac{1}{2n\pi} \right] \\&= \frac{10}{n\pi}\end{aligned}$$

Step 4 of 6

Recall equation (1).

$$v_s(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

Substitute the values of the coefficients a_0, a_n and b_n in equation (1).

$$\begin{aligned} v_s(t) &= 5 + \sum_{n=1}^{\infty} \left((0) \cos n2\pi t + \frac{10}{n\pi} \sin n2\pi t \right) \\ &= 5 + \sum_{n=1}^{\infty} \left(\frac{10}{n\pi} \sin 2n\pi t \right) \text{ V} \end{aligned}$$

Calculate the impedance of the 1H inductor.

$$\begin{aligned} Z_L &= j\omega_n L \\ &= j\omega_n (1) \\ &= j\omega_n \end{aligned}$$

Calculate the impedance of the 100 mF capacitor.

$$\begin{aligned} Z_C &= \frac{1}{j\omega_n C} \\ &= \frac{1}{j\omega_n (100 \times 10^{-3})} \\ &= -j \frac{10}{\omega_n} \end{aligned}$$

Step 5 of 6

From the Figure 17.72(a), the current I_o is,

$$\begin{aligned} I_o &= \frac{V_s}{5 + Z_L + Z_C} \\ &= \frac{V_s}{5 + j\omega_n - \frac{j10}{\omega_n}} \end{aligned}$$

For dc component, $\omega_n = 0$.

Therefore,

$$\begin{aligned} I_o &= \frac{V_s}{5 + j(0) - \frac{j10}{0}} \\ &= 0 \end{aligned}$$

Step 6 of 6

For the nth harmonic,

$$\begin{aligned}
 I_o &= \frac{\frac{10}{n\pi} \angle 0^\circ}{5 + j2\pi n - \frac{j10}{2\pi n}} \\
 &= \frac{10}{5n\pi + j(2n^2\pi^2 - 5)} \\
 &= \frac{10}{\sqrt{25n^2\pi^2 + (2n^2\pi^2 - 5)^2}} \angle -\tan^{-1}\left(\frac{2n^2\pi^2 - 5}{25n^2\pi^2}\right) \\
 &= A_n \angle -\phi_n
 \end{aligned}$$

The response of the circuit is,

$$i_o(t) = \sum_{n=1}^{\infty} A_n \sin(2n\pi t + \phi_n)$$

Here,

$$\begin{aligned}
 A_n &= \frac{10}{\sqrt{25n^2\pi^2 + (2n^2\pi^2 - 5)^2}} \\
 \phi_n &= -\tan^{-1}\left(\frac{2n^2\pi^2 - 5}{25n^2\pi^2}\right)
 \end{aligned}$$

Therefore, the response of the circuit, $i_o(t)$ is $\boxed{\sum_{n=1}^{\infty} A_n \sin(2n\pi t + \phi_n)}$.