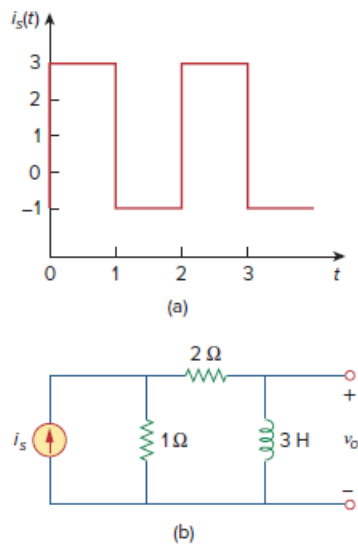


Problem

If the periodic current waveform in Fig. 17.73(a) is applied to the circuit in Fig. 17.73(b), find v_o .

Figure 17.73:



Step-by-step solution

Step 1 of 12

Consider the circuit shown in Figure 1.

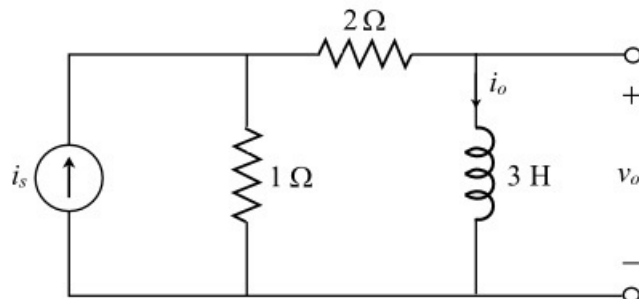


Figure 1

Step 2 of 12

Consider the periodic current waveform shown in Figure 2.

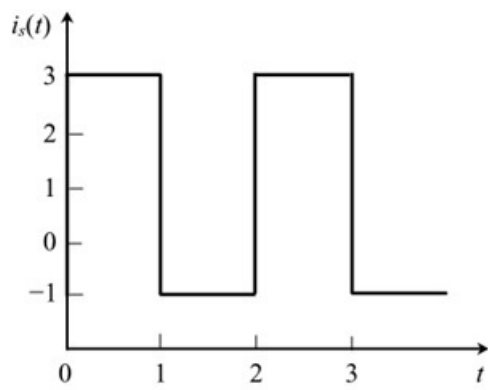


Figure 2

Step 3 of 12

Consider the waveform shown in figure 2.

The time period is 2 sec.

Therefore, the angular frequency is,

$$\begin{aligned}\omega_0 &= \frac{2\pi}{T} \\ &= \frac{2\pi}{2} \\ &= \pi \text{ rad/s}\end{aligned}$$

Step 4 of 12

Express the periodic current waveform in Figure 2 in Fourier series. Write the general expression of the Fourier series.

$$i_s(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t) \dots\dots (1)$$

Here, a_0 , a_n , and b_n are coefficients of Fourier series.

Calculate the value of the Fourier coefficient a_0 of Fourier series.

$$\begin{aligned}a_0 &= \frac{1}{T} \int_0^T i_s(t) dt \\ &= \frac{1}{2} \int_0^1 3 dt + \frac{1}{2} \int_1^2 -1 dt \\ &= 1.5(1-0) + 0.5(2-1) \\ &= 2\end{aligned}$$

Step 5 of 12

Calculate the value of the Fourier coefficient a_n of Fourier series.

$$\begin{aligned} a_n &= \frac{2}{T} \int_0^T i_s(t) \cos n\omega_0 t dt \\ &= \frac{2}{2} \int_0^1 3 \cos n\omega_0 t dt + \frac{2}{2} \int_1^2 1 \cos n\omega_0 t dt \\ &= \frac{3}{n\omega_0} \sin n\omega_0 t \Big|_0^1 + \frac{1}{n\omega_0} \sin n\omega_0 t \Big|_1^2 \end{aligned}$$

Substitute π for ω_0 .

$$\begin{aligned} a_n &= \frac{1}{n\pi} [3 \sin n\pi] + \frac{1}{n\pi} [\sin 2n\pi - \sin n\pi] \quad (\text{since } \omega_0 = \pi) \\ &= \frac{1}{n\pi} [2 \sin n\pi + \sin 2n\pi] \quad \left(\begin{array}{l} \text{since } \sin n\pi = 0 \\ \sin 2n\pi = 0 \end{array} \right) \\ &= 0 \end{aligned}$$

Calculate the value of the Fourier coefficient b_n of Fourier series.

$$\begin{aligned} b_n &= \frac{2}{T} \int_0^T i_s(t) \sin n\omega_0 t dt \\ &= \frac{2}{2} \int_0^1 3 \sin n\omega_0 t dt + \frac{2}{2} \int_1^2 1 \sin n\omega_0 t dt \\ &= \frac{-3}{n\omega_0} \cos n\omega_0 t \Big|_0^1 - \frac{1}{n\omega_0} \cos n\omega_0 t \Big|_1^2 \end{aligned}$$

Substitute π for ω_0 .

$$b_n = \frac{-3}{n\pi} \cos n\pi t \Big|_0^1 - \frac{1}{n\pi} \cos n\pi t \Big|_1^2$$

Step 6 of 12

Continue the calculations.

$$\begin{aligned} b_n &= \frac{-3}{n\pi} [\cos n\pi - 1] - \frac{1}{n\pi} [\cos 2n\pi - \cos n\pi] \\ &= \frac{3}{n\pi} [1 - \cos n\pi] - \frac{1}{n\pi} [1 - \cos n\pi] \quad (\text{since } \cos 2n\pi = 1) \\ &= \frac{2}{n\pi} [1 - \cos n\pi] \end{aligned}$$

Recall equation (1).

$$i_s(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

Substitute the values of the coefficients a_0, a_n and b_n in equation (1).

$$\begin{aligned} i_s(t) &= a_0 + \sum_{n=1}^{\infty} ((0) \cos n\pi t + b_n \sin n\pi t) \\ &= 2 + \sum_{n=1}^{\infty} \left(\frac{2}{n\pi} [1 - \cos n\pi] \sin n\pi t \right) \\ &= 2 + \sum_{n=1}^{\infty} \left(\frac{2}{n\pi} [1 - \cos n\pi] \cos(n\pi t - 90^\circ) \right) \end{aligned}$$

Step 7 of 12

The phasor form of current $i_s(t)$ for nth harmonic is,

$$I_s = \sqrt{\frac{2^2(1 - \cos n\pi)^2}{1 + (n\pi)^2}} \angle -90^\circ$$

$$= \frac{2(1 - \cos n\pi)}{(n\pi)} \angle -90^\circ$$

Step 8 of 12

Apply the current division rule to Figure 1.

$$i_o = \left[\frac{1}{1 + 2 + j\omega_n 3} \right] i_s$$

$$= \frac{i_s}{3 + 3j\omega_n}$$

Here,

$$\omega_n = n\omega_0$$

$$i_o = \frac{i_s}{3 + 3jn\omega_0}$$

Substitute π for ω_0 .

$$i_o = \frac{i_s}{3 + 3jn\pi}$$

Step 9 of 12

Calculate the output voltage across inductor from Figure 1.

$$V_o = (j\omega_n 3)i_o$$

$$= (jn\omega_0 3)i_o$$

Substitute π for ω_0 .

$$V_o = (j3\pi n)i_o$$

Substitute $\frac{i_s}{3 + 3jn\pi}$ for i_o .

$$V_o = (j3\pi n) \left(\frac{i_s}{3 + 3jn\pi} \right) \dots\dots (2)$$

Step 10 of 12

Calculate the DC component of output voltage.

Substitute the term 2 for i_s in equation (2).

$$V_o = \frac{j3n\pi}{1 + j3n\pi} \{2\}$$

$$= \frac{j\pi n}{1 + j\pi n} \{2\}$$

$$= \frac{j\pi \times 0}{1 + j\pi \times 0} \{2\} \quad (\text{since for } n = 0)$$

$$= 0$$

Step 11 of 12

Recall equation (2).

$$V_o = (j3\pi n) \left(\frac{I_s}{3 + jn\pi} \right)$$

Calculate the output voltage for n^{th} harmonic.

Substitute $\left[\frac{2(1 - \cos n\pi)}{(n\pi)} \angle -90^\circ \right]$ for I_s .

$$\begin{aligned} V_n &= \frac{j3n\pi}{1 + j3n\pi} \left\{ \sum_{n=1}^{\infty} \frac{2(1 - \cos n\pi)}{(n\pi)} \angle -90^\circ \right\} \\ &= \frac{j1}{1 + j\pi n} \left\{ \sum_{n=1}^{\infty} 2(1 - \cos n\pi) \angle -90^\circ \right\} \\ &= \frac{2(1 - \cos n\pi)}{\sqrt{1 + (n\pi)^2}} \angle 90^\circ - \tan^{-1}(n\pi) - 90^\circ \\ &= \left[\frac{2(1 - \cos n\pi)}{\sqrt{1 + (n\pi)^2}} \angle -\tan^{-1}(n\pi) \right] \text{ V} \end{aligned}$$

Step 12 of 12

Therefore,

$$v_o(t) = \left[0 + \sum_{n=1}^{\infty} \frac{2(1 - \cos n\pi)}{\sqrt{1 + (n\pi)^2}} \cos(n\pi t - \tan^{-1} n\pi) \right] \text{ V}$$

Therefore, the output voltage $v_o(t)$ is $\boxed{\sum_{n=1}^{\infty} \frac{2(1 - \cos n\pi)}{\sqrt{1 + (n\pi)^2}} \cos(n\pi t - \tan^{-1} n\pi) \text{ V}}.$