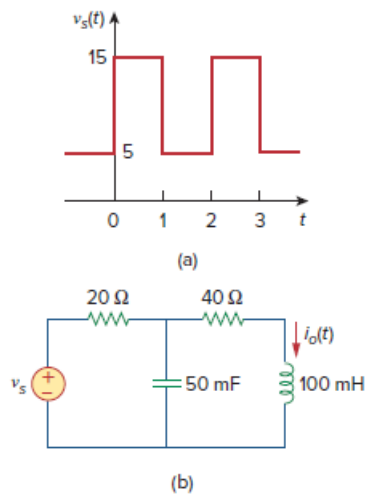


Problem

If the periodic voltage in Fig. 17.75(a) is applied to the circuit in Fig. 17.75(b), find $i_o(t)$.

Figure 17.75:



Step-by-step solution

Step 1 of 9

Refer to Equation 17.3 in the textbook.

The Fourier series is,

$$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

Where,

$$\omega_0 = \frac{2\pi}{T} \text{ is the fundamental frequency.}$$

The function is,

$$f(t) = \begin{cases} 15, & 0 < t < 1 \\ 5, & 1 < t < 2 \end{cases}$$

Step 2 of 9

The time period is, $T = 2$.

Determine the value of ω_0 .

$$\begin{aligned}\omega_0 &= \frac{2\pi}{2} \\ &= \pi\end{aligned}$$

Determine the value of a_0 .

$$\begin{aligned}a_0 &= \frac{1}{T} \int_0^T f(t) dt \\ &= \frac{1}{2} \int_0^2 f(t) dt \\ &= \frac{1}{2} \int_0^1 f(t) dt + \frac{1}{2} \int_1^2 f(t) dt \\ &= \frac{1}{2} \int_0^1 15 dt + \frac{1}{2} \int_1^2 5 dt \\ &= \frac{15}{2} + \frac{5}{2} \\ &= 10\end{aligned}$$

Step 3 of 9

Determine the value of a_n .

$$\begin{aligned}a_n &= \frac{2}{T} \int_0^T f(t) \cos(n\omega_0 t) dt \\ &= \frac{2}{2} \int_0^2 f(t) \cos(n\pi t) dt \\ &= \int_0^1 15 \cos(n\pi t) dt + \int_1^2 5 \cos(n\pi t) dt \\ &= \frac{15}{n\pi} [\sin(n\pi t)]_{t=0}^{t=1} + \frac{5}{n\pi} [\sin(n\pi t)]_{t=1}^{t=2} \\ &= \frac{15}{n\pi} \sin(n\pi) + \frac{5}{n\pi} (\sin(2n\pi) - \sin(n\pi)) \\ &= 0\end{aligned}$$

Step 4 of 9

Determine the value of b_n .

$$\begin{aligned}b_n &= \frac{2}{T} \int_0^T f(t) \sin(n\omega_0 t) dt \\ &= \frac{2}{2} \int_0^2 f(t) \sin(n\pi t) dt \\ &= \int_0^1 15 \sin(n\pi t) dt + \int_1^2 5 \sin(n\pi t) dt \\ &= \frac{15}{n\pi} [-\cos(n\pi t)]_{t=0}^{t=1} + \frac{5}{n\pi} [-\cos(n\pi t)]_{t=1}^{t=2} \\ &= \frac{15}{n\pi} [1 - \cos(n\pi)] + \frac{5}{n\pi} [\cos(n\pi) - \cos(2n\pi)] \\ &= \frac{15}{n\pi} [1 - \cos(n\pi)] + \frac{5}{n\pi} [\cos(n\pi) - 1] \\ &= \frac{10}{n\pi} [1 - \cos(n\pi)]\end{aligned}$$

Step 5 of 9

The Fourier series is,

$$\begin{aligned} f(t) &= a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t) \\ &= 10 + \sum_{n=1}^{\infty} (b_n \sin n\omega_0 t) \\ &= 10 + \sum_{n=1}^{\infty} \left\{ \frac{10}{n\pi} [1 - \cos(n\pi)] \sin(n\pi t) \right\} \end{aligned}$$

Step 6 of 9

Refer to Figure 17.75 in the textbook.

Use Kirchhoff's voltage law in the frequency domain.

$$\begin{aligned} \mathbf{I}_s &= \frac{1}{20 + \frac{(40 + j\omega 0.1) \left(\frac{20}{j\omega} \right)}{40 + j\omega 0.1 + \frac{20}{j\omega}}} \mathbf{V}_s \\ &= \frac{1}{20 + \frac{20(40 + j\omega 0.1)}{j\omega 40 + 20 - 0.1\omega^2}} \mathbf{V}_s \\ &= \frac{j\omega 40 + 20 - 0.1\omega^2}{20(j\omega 40 + 20 - 0.1\omega^2) + 20(40 + j\omega 0.1)} \mathbf{V}_s \\ &= \frac{j\omega 40 + 20 - 0.1\omega^2}{j\omega 802 + 1200 - 2\omega^2} \mathbf{V}_s \end{aligned}$$

[Comments \(1\)](#)



Anonymous

please tell me this is not a serious chegg step

Step 7 of 9

By current division, $\mathbf{I}_o$ can be expressed as follows:

$$\begin{aligned} \mathbf{I}_o &= \frac{\left(\frac{20}{j\omega} \right)}{40 + j\omega 0.1 + \frac{20}{j\omega}} \mathbf{I}_s \\ &= \frac{20}{j\omega 40 + 20 - 0.1\omega^2} \mathbf{I}_s \\ &= \frac{20}{j\omega 40 + 20 - 0.1\omega^2} \cdot \frac{j\omega 40 + 20 - 0.1\omega^2}{j\omega 802 + 1200 - 2\omega^2} \mathbf{V}_s \\ &= \frac{20}{j\omega 802 + 1200 - 2\omega^2} \mathbf{V}_s \end{aligned}$$

Step 8 of 9

Substitute $\omega_n = n\pi$ in the equation.

$$\mathbf{I}_o = \frac{20}{jn\pi 802 + 1200 - 2n^2\pi^2} \times \mathbf{V}_s$$

For the n-th harmonic,

$$v_s(t) = 10 + \sum_{n=1}^{\infty} \left\{ \frac{10}{n\pi} [1 - \cos(n\pi)] \sin(n\pi t) \right\}$$

$$\mathbf{V}_s = \frac{10}{n\pi} [1 - \cos(n\pi)] \angle -90^\circ$$

For dc component, $\omega_n = 0$ or $n = 0$.

$$\begin{aligned} \mathbf{I}_{\text{dc}} &= \lim_{n \rightarrow 0} \left| \frac{20}{jn\pi 802 + 1200 - 2n^2\pi^2} \times \mathbf{V}_{\text{dc}} \right| \\ &= \lim_{n \rightarrow 0} \left| \frac{20}{1200} \times 10 \right| \\ &= \frac{1}{6} \end{aligned}$$

Determine the expression for $\mathbf{I}_o$.

$$\begin{aligned} \mathbf{I}_o &= \frac{20}{j\omega 802 + 1200 - 2\omega^2} \mathbf{V}_s \\ &= \frac{20}{jn\pi 802 + 1200 - 2n^2\pi^2} \mathbf{V}_s \\ &= \frac{20}{jn\pi 802 + 1200 - 2n^2\pi^2} \cdot \frac{10}{n\pi} [1 - \cos(n\pi)] \angle -90^\circ \\ &= \frac{20}{\sqrt{(n\pi 802)^2 + (1200 - 2n^2\pi^2)^2} \angle \tan^{-1} \left(\frac{802n\pi}{1200 - 2n^2\pi^2} \right)} \cdot \frac{10}{n\pi} [1 - \cos(n\pi)] \angle -90^\circ \\ &= \frac{200 \times 2 \angle \left[-90^\circ - \tan^{-1} \left(\frac{802n\pi}{1200 - 2n^2\pi^2} \right) \right]}{n\pi \sqrt{(n\pi 802)^2 + (1200 - 2n^2\pi^2)^2}}, n \text{ is odd} \\ &= \frac{400 \angle \left[-90^\circ - \tan^{-1} \left(\frac{802n\pi}{1200 - 2n^2\pi^2} \right) \right]}{n\pi \sqrt{(n\pi 802)^2 + (1200 - 2n^2\pi^2)^2}}, n \text{ is odd} \\ &= \frac{400 \angle \left[-90^\circ + \tan^{-1} \left(\frac{802n\pi}{2n^2\pi^2 - 1200} \right) \right]}{n\pi \sqrt{(n\pi 802)^2 + (1200 - 2n^2\pi^2)^2}}, n \text{ is odd} \end{aligned}$$

In the time domain, determine the expression for $\mathbf{I}_o$.

$$\begin{aligned}
 i_o(t) &= \frac{1}{6} + \frac{400}{\pi} \sum_{k=1}^{\infty} \frac{\cos \left[n\pi t + \left[-90^\circ + \tan^{-1} \left(\frac{802n\pi}{2n^2\pi^2 - 1200} \right) \right] \right]}{n\sqrt{(n\pi 802)^2 + (1200 - 2n^2\pi^2)^2}}, n = 2k - 1 \\
 &= \frac{1}{6} + \frac{400}{\pi} \sum_{k=1}^{\infty} \frac{\sin \left[n\pi t + \tan^{-1} \left(\frac{802n\pi}{2n^2\pi^2 - 1200} \right) \right]}{n\sqrt{(n\pi 802)^2 + (1200 - 2n^2\pi^2)^2}}, n = 2k - 1 \\
 &= \frac{1}{6} + \frac{400}{\pi} \sum_{k=1}^{\infty} \frac{\sin \left[n\pi t + 90^\circ - \cot^{-1} \left(\frac{802n\pi}{2n^2\pi^2 - 1200} \right) \right]}{n\sqrt{(n\pi 802)^2 + (1200 - 2n^2\pi^2)^2}}, n = 2k - 1 \\
 &= \frac{1}{6} + \frac{400}{\pi} \sum_{k=1}^{\infty} \frac{\sin \left[n\pi t + 90^\circ - \tan^{-1} \left(\frac{2n^2\pi^2 - 1200}{802n\pi} \right) \right]}{n\sqrt{(n\pi 802)^2 + (1200 - 2n^2\pi^2)^2}}, n = 2k - 1
 \end{aligned}$$

Thus, the output current $i_o(t)$ is,

$$i_o(t) = \frac{1}{6} + \frac{400}{\pi} \sum_{k=1}^{\infty} \frac{\sin \left[n\pi t + 90^\circ - \tan^{-1} \left(\frac{2n^2\pi^2 - 1200}{802n\pi} \right) \right]}{n\sqrt{(n\pi 802)^2 + (1200 - 2n^2\pi^2)^2}}, n = 2k - 1$$

[Comments \(1\)](#)



Anonymous

problem needs to be updated for the new edition of the book.