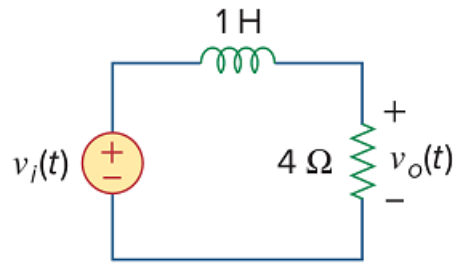


Problem


Determine $v_o(t)$ in Fig. 18.19 if $v_i(t) = 5\text{sgn}(t) = (-5 + 10u(t))$ V.



Step-by-step solution

Step 1 of 10

The given circuit is

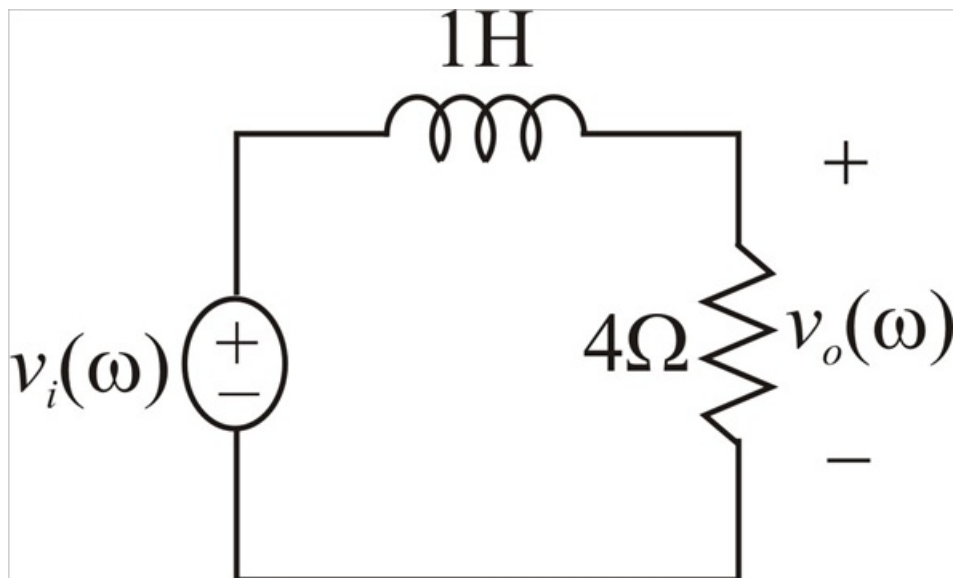

Step 2 of 10

The given input voltage is $v_i(t) = 5\text{sgn}(t) = (-5 + 10u(t))$ V

We know that $\mathcal{F}\{1\} = 2\pi\delta(\omega)$

And $\mathcal{F}\{u(t)\} = \pi\delta(\omega) + \frac{1}{j\omega}$

The Fourier transform of the input voltage is

$$\mathcal{F}\{v_i(t)\} = \mathcal{F}\{-5 + 10u(t)\}$$

Step 3 of 10

$$V_i(\omega) = -5F \{1\} + 10F \{u(t)\}$$

$$V_i(\omega) = -5[2\pi\delta(\omega)] + 10\left[\pi\delta(\omega) + \frac{1}{j\omega}\right]$$

$$V_i(\omega) = -10\pi\delta(\omega) + 10\pi\delta(\omega) + \frac{10}{j\omega}$$

$$V_i(\omega) = \frac{10}{j\omega}$$

Step 4 of 10

In frequency domain,

$$R \rightarrow R$$

$$4\Omega \rightarrow 4\Omega$$

$$L \rightarrow j\omega L$$

$$1\text{ H} \rightarrow j\omega \times 1$$


$$1\text{ H} \rightarrow j\omega\Omega$$

$$v_i(t) \rightarrow V_i(\omega)$$

$$v_o(t) \rightarrow V_o(\omega)$$

Step 5 of 10

The circuit in frequency domain is

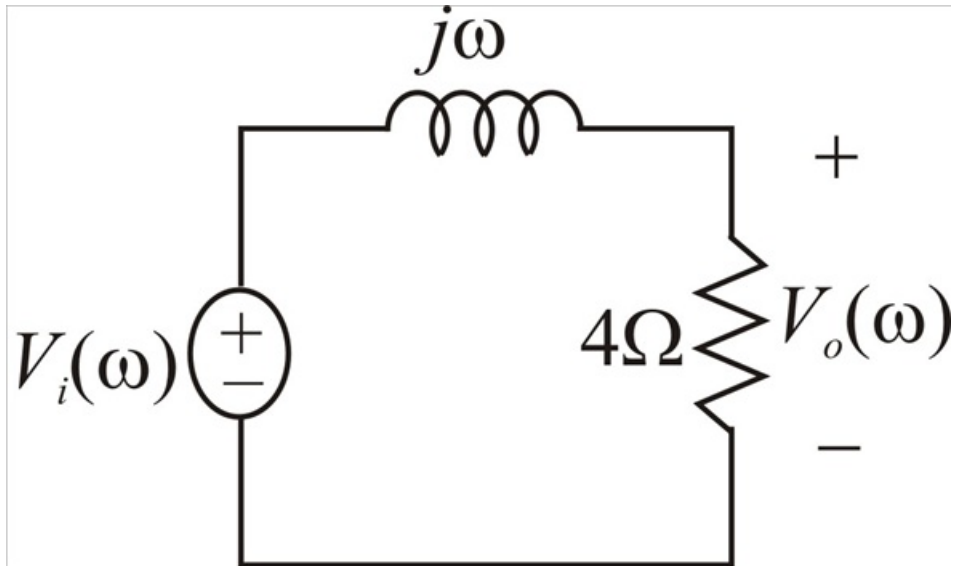

Step 6 of 10

By voltage division rule,

$$V_o(\omega) = \frac{4}{4 + j\omega} V_i(\omega)$$

$$V_o(\omega) = \frac{4}{4 + j\omega} \left[\frac{10}{j\omega} \right]$$

$$V_o(\omega) = \frac{40}{j\omega(4 + j\omega)}$$

Using partial fractions method

$$\frac{40}{j\omega(4+j\omega)} = \frac{A}{j\omega} + \frac{B}{4+j\omega}$$

$$\frac{40}{j\omega(4+j\omega)} = \frac{A(4+j\omega) + B(j\omega)}{j\omega(4+j\omega)}$$

$$40 = A(4+j\omega) + B(j\omega) \dots\dots\dots (1)$$

Step 8 of 10

Consider $j\omega = -4$

$$40 = A(4-4) + B(-4)$$

$$40 = 0 - 4B$$

$$B = -\frac{40}{4}$$

$$\therefore B = -10$$

Step 9 of 10

Consider constants on both sides of equation (1),

$$4A = 40$$

$$\therefore A = 10$$

$$V_o(\omega) = \frac{10}{j\omega} - \frac{10}{4+j\omega}$$

We know that

$$\mathcal{F}^{-1}\left\{\frac{2}{j\omega}\right\} = \text{sgn}(t) = -1 + 2u(t)$$

$$\mathcal{F}^{-1}\left\{\frac{1}{a+j\omega}\right\} = e^{-at}u(t)$$

Step 10 of 10

Using above two equations apply inverse Fourier transform on both sides of $V_o(\omega)$, we get:

$$\mathcal{F}^{-1}\{V_o(\omega)\} = \mathcal{F}^{-1}\left\{5\frac{2}{j\omega} - \frac{10}{4+j\omega}\right\}$$

$$v_o(t) = 5\mathcal{F}^{-1}\left\{\frac{2}{j\omega}\right\} - 10\mathcal{F}^{-1}\left\{\frac{1}{4+j\omega}\right\}$$

$$v_o(t) = 5[-1 + 2u(t)] - 10[e^{-4t}u(t)]$$

$$v_o(t) = -5 + 10u(t) - 10e^{-4t}u(t)$$

$$\therefore \boxed{v_o(t) = -5 + 10(1 - e^{-4t})u(t) \text{ V}}$$