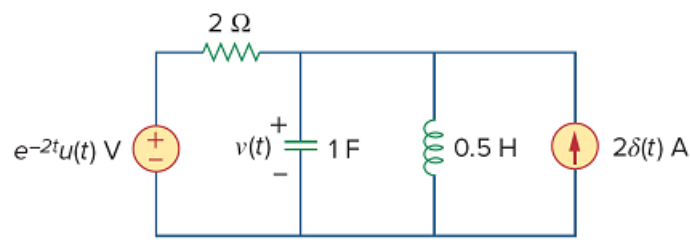


Problem

Determine the Fourier transform of $v(t)$ in the circuit shown in Fig. 18.43.

Figure 18.43



Step-by-step solution

Step 1 of 2

Refer to Figure 18.43 in the textbook.

The Fourier transform of voltage source is,

$$F(e^{-2t}u(t)) = \frac{1}{2 + j\omega}$$

The Fourier transform of current source is,

$$F(2\delta(t)) = 2$$

Draw the circuit in frequency domain.

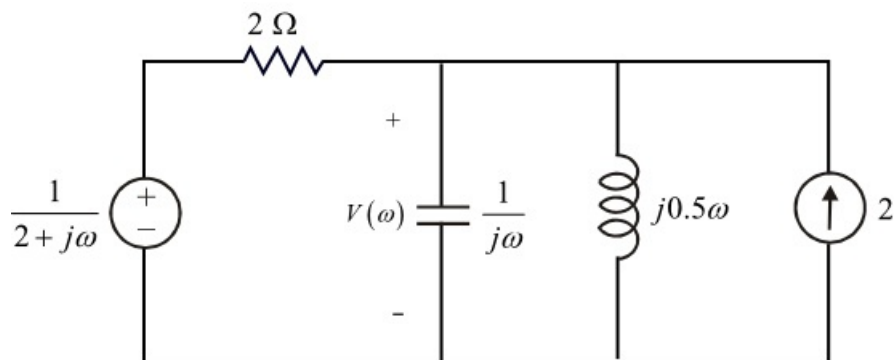


Figure 1

Step 2 of 2

Write the Kirchhoff's current law at node $V(\omega)$.

$$\frac{V(\omega) - \frac{1}{2 + j\omega}}{2} + \frac{V(\omega)}{\frac{1}{j\omega}} + \frac{V(\omega)}{j0.5\omega} - 2 = 0$$

$$\frac{V(\omega) - \frac{1}{2 + j\omega}}{2} + j\omega V(\omega) + \frac{V(\omega)}{j0.5\omega} - 2 = 0$$

$$V(\omega) \left(\frac{1}{2} + j\omega + \frac{1}{j0.5\omega} \right) = \frac{1}{2(2 + j\omega)} + 2$$

$$V(\omega) \left(\frac{j0.5\omega - \omega^2 + 2}{j\omega} \right) = \frac{1 + 8 + 4j\omega}{2(2 + j\omega)}$$

$$V(\omega) = \frac{(9 + 4j\omega)(j\omega)}{2(2 + j\omega)(j0.5\omega - \omega^2 + 2)}$$

$$V(\omega) = \frac{2j\omega(4.5 + 2j\omega)}{(2 + j\omega)(4 - 2\omega^2 + j\omega)}$$

Therefore, the Fourier transform of $v(t)$ is $V(\omega) = \frac{2j\omega(4.5 + 2j\omega)}{(2 + j\omega)(4 - 2\omega^2 + j\omega)}$.