


Problem

Obtain the current $i_o(t)$ in the circuit of Fig. 18.44.

(a) Let $i(t) = \text{sgn}(t)$ A.

(b) Let $i(t) = 4[u(t) - u(t - 1)]$ A.

Figure 18.44

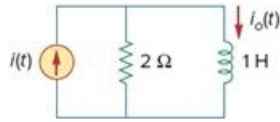

Step-by-step solution

Step 1 of 4

By current division,

$$I_o = \frac{2}{2 + j\omega} I(\omega)$$

Step 2 of 4

(A) for $i(t) = 5 \text{sgn}(t)$

$$I(\omega) = \frac{10}{j\omega}$$

$$I_o = \frac{2}{2 + j\omega} \cdot \frac{10}{j\omega} = \frac{20}{j\omega(2 + j\omega)}$$



let $I_o = \frac{20}{s(s+2)} = \frac{A}{2s} + \frac{B}{s+2}$, $A = 10$, $B = -10$

$$I_o(\omega) = \frac{10}{j\omega} - \frac{10}{2 + j\omega}$$

$$i_o(t) = 5 \text{sgn}(t) - 10e^{-2t}u(t) \text{ A}$$

Step 3 of 4

(B)

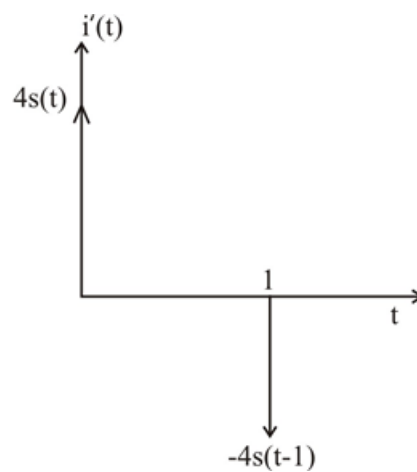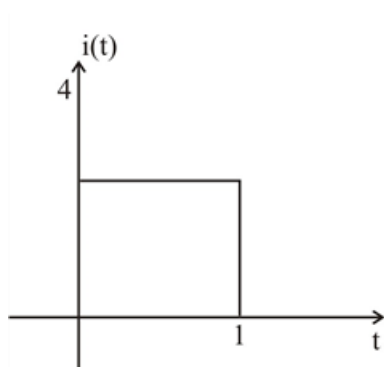

$$i'(t) = 4s(t) - 4s(t-1)$$

$$j\omega I(\omega) = 4 - 4e^{-j\omega}$$

$$I(\omega) = \frac{4(1 - e^{-j\omega})}{j\omega}$$

$$I_o \frac{8(1 - e^{-j\omega})}{j\omega(2 + j\omega)} = 4 \left(\frac{1}{j\omega} - \frac{1}{2 + j\omega} \right) (1 - e^{-j\omega})$$

$$= \frac{4}{j\omega} - \frac{4}{2 + j\omega} - \frac{4e^{-j\omega}}{j\omega} + \frac{4e^{-j\omega}}{2 + j\omega}$$

$$i_o(t) = 2\operatorname{sgn}(t) - 2\operatorname{sgn}(t-1) - 4e^{-2t}u(t) + 4e^{-2(t-1)}u(t-1) A.$$