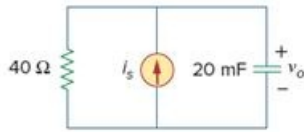


Problem

Find $v_o(t)$ in the circuit of Fig. 18.45, where $i_s = 5e^{-t}u(t)$ A.


Figure 18.45



Step-by-step solution

Step 1 of 7

Given circuit diagram is

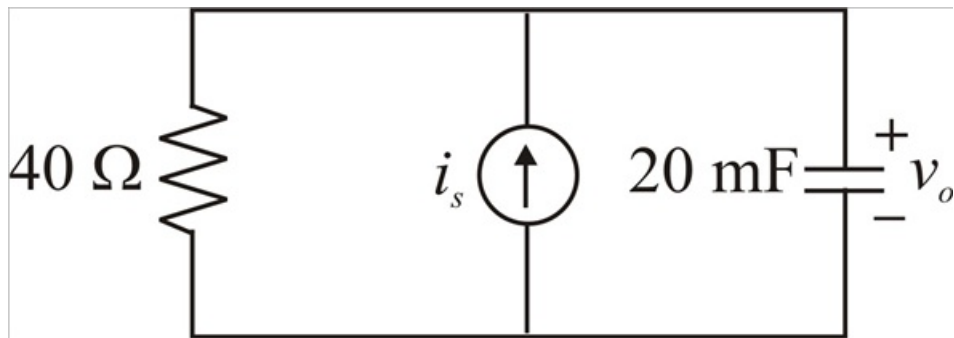

Step 2 of 7

Given that

$$i_s = 5e^{-t}u(t) \text{ A}$$

Applying Fourier Transform,

$$\mathcal{F}[i_s] = \mathcal{F}[5e^{-t}u(t)]$$

$$I_s(\omega) = \frac{5}{1 + j\omega} \text{ A}$$

Converting time domain circuit to frequency domain circuit,


$$X_C = \frac{1}{j\omega C}$$

$$X_{20\text{mF}} = \frac{1}{j\omega \times 20 \times 10^{-3}}$$

$$X_{20\text{mF}} = \frac{50}{j\omega}$$

Thus, the frequency domain circuit is

Step 3 of 7

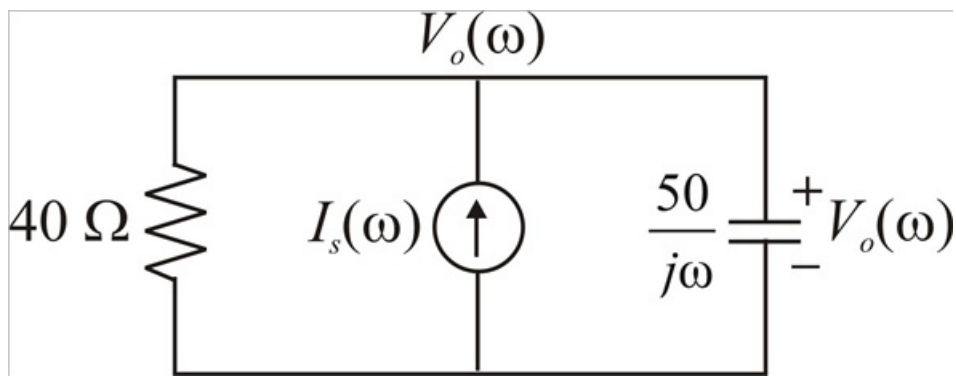

Step 4 of 7

Applying KCL at node $V_o(\omega)$:

$$\frac{V_o(\omega)}{40} + I_s(\omega) + \frac{V_o(\omega)}{\frac{50}{j\omega}} = 0$$

$$\frac{V_o(\omega)}{40} + \frac{j\omega V_o(\omega)}{50} = -I_s(\omega)$$

$$\frac{5V_o(\omega) + 4j\omega V_o(\omega)}{200} = -I_s(\omega)$$

$$\frac{(5 + 4j\omega)V_o(\omega)}{200} = -I_s(\omega)$$

Substitute $I_s(\omega)$ in the above equation

$$\frac{(5 + 4j\omega)V_o(\omega)}{200} = -\left(\frac{5}{1 + j\omega}\right)$$

$$(5 + 4j\omega)V_o(\omega) = -\left(\frac{1000}{1 + j\omega}\right)$$

$$V_o(\omega) = -1000 \left(\frac{1}{(1 + j\omega)(5 + 4j\omega)} \right)$$

Step 5 of 7

Using partial fractions to above equation,

$$V_o(\omega) = \frac{1000}{(1 + j\omega)(5 + 4j\omega)} = 1000 \left(\frac{A}{1 + j\omega} + \frac{B}{5 + 4j\omega} \right) \dots\dots (1)$$

$$\frac{1}{(1 + j\omega)(5 + 4j\omega)} = \frac{A(5 + 4j\omega) + B(1 + j\omega)}{(1 + j\omega)(5 + 4j\omega)}$$

$$1 = A(5 + 4j\omega) + B(1 + j\omega) \dots\dots (2)$$

Step 6 of 7

Put $j\omega = -1$ in equation-(2)

$$1 = A(5 + 4(-1)) + B(1 + (-1))$$

$$A = 1$$

Put $j\omega = 0$ in equation-(2)

$$1 = A(5 + 4(0)) + B(1 + 0)$$

$$1 = 5A + B$$

$$1 = 5(1) + B$$

$$B = -4$$

Step 7 of 7

Substitute A and B in equation-(1)

$$V_o(\omega) = 1000 \left(\frac{1}{1 + j\omega} + \frac{-4}{5 + 4j\omega} \right)$$

$$V_o(\omega) = 1000 \left(\frac{1}{1 + j\omega} - \frac{1}{1.25 + j\omega} \right)$$

Applying inverse Fourier Transform to above equation

$$\mathcal{F}^{-1}[V_o(\omega)] = \mathcal{F}^{-1} \left[1000 \left(\frac{1}{1 + j\omega} - \frac{1}{1.25 + j\omega} \right) \right]$$

$$\mathcal{F}^{-1}[V_o(\omega)] = 1000 \left(\mathcal{F}^{-1} \left[\frac{1}{1 + j\omega} \right] - \mathcal{F}^{-1} \left[\frac{1}{1.25 + j\omega} \right] \right)$$

Therefore, $\boxed{v_o(t) = 1000(e^{-t} - e^{-1.25t})\mu(t) \text{ V}}.$