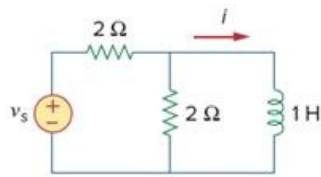


Problem

Use the Fourier transform to find $i(t)$ in the circuit of Fig. 18.47 if $v_s(t) = 10e^{-2t}u(t)$.

Figure 18.47



Step-by-step solution

Step 1 of 5

Consider the following circuit diagram:

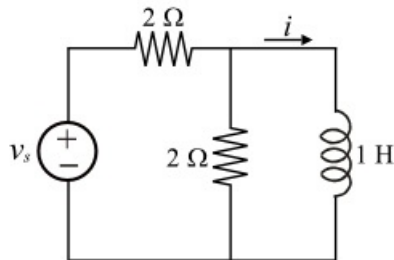


Figure 1

Step 2 of 5

Consider the input source voltage, $v_s(t) = 10e^{-2t}u(t)$.

Redraw the circuit in Figure 1 after converting the voltage source into a current source.

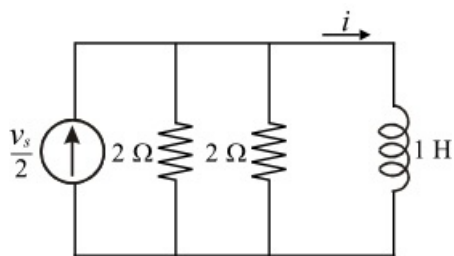


Figure 2

Step 3 of 5

Redraw the circuit in Figure 2 by replacing the two parallel resistances with their equivalent $1\ \Omega$ resistance.

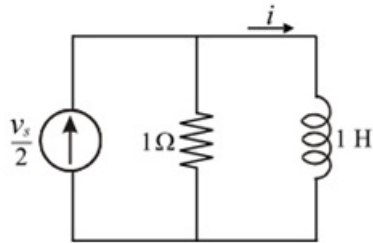


Figure 3

Step 4 of 5

Convert the time domain function v_s into the frequency domain using the Fourier transform pair.

$$\begin{aligned}
 V_s &= \mathcal{F}(v_s) \\
 &= \mathcal{F}[10e^{-2t}u(t)] \\
 &= 10\mathcal{F}[e^{-2t}u(t)] \quad \left(\because e^{-at}u(t) \xleftrightarrow{\mathcal{F}} \frac{1}{a+j\omega} \right) \\
 &= \frac{10}{j\omega+2}
 \end{aligned}$$

Draw the Figure 3 in Frequency domain.

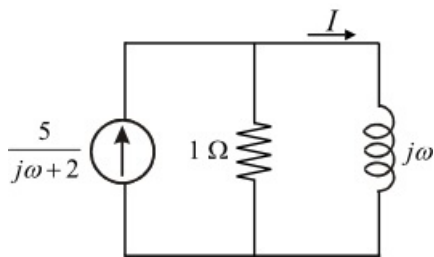


Figure 4

Step 5 of 5

Calculate the current I in Figure 4 using the current division formula.

$$\begin{aligned} I &= \left(\frac{5}{j\omega + 2} \right) \left(\frac{1}{1 + j\omega} \right) \\ &= \left(\frac{5}{(j\omega + 2)(1 + j\omega)} \right) \\ &= \frac{A}{j\omega + 2} + \frac{B}{1 + j\omega} \end{aligned}$$

Here A and B are constants.

Calculate the constant value A , using the residue method.

$$\begin{aligned} A &= (j\omega + 2)I \Big|_{j\omega = -2} \\ &= (j\omega + 2) \left(\frac{5}{(j\omega + 2)(1 + j\omega)} \right) \Big|_{j\omega = -2} \\ &= \left(\frac{5}{(-2 + 1)} \right) \\ &= -5 \end{aligned}$$

Calculate the constant value B using the residue method.

$$\begin{aligned} B &= (j\omega + 1)I \Big|_{j\omega = -1} \\ &= (j\omega + 1) \left(\frac{5}{(j\omega + 2)(j\omega + 1)} \right) \Big|_{j\omega = -1} \\ &= \left(\frac{5}{(2 - 1)} \right) \\ &= 5 \end{aligned}$$

Substitute obtained A and B values in equation I .

$$\begin{aligned} I &= \frac{(-5)}{j\omega + 2} + \frac{5}{1 + j\omega} \\ &= \frac{5}{1 + j\omega} - \frac{5}{2 + j\omega} \end{aligned}$$

Apply the inverse Fourier transform to find $i(t)$

$$\begin{aligned} i(t) &= \mathcal{F}^{-1}(I) \\ &= \mathcal{F}^{-1} \left[\frac{5}{(j\omega + 1)} - \frac{5}{(j\omega + 2)} \right] \quad \left(\because e^{-at}u(t) \xleftrightarrow{\mathcal{F}} \frac{1}{a + j\omega} \right) \\ &= 5e^{-t}u(t) - 5e^{-2t}u(t) \\ &= 5(e^{-t} - e^{-2t})u(t) \text{ A} \end{aligned}$$

Thus, the current $i(t)$ in the circuit of Figure 1 is $\boxed{5(e^{-t} - e^{-2t})u(t) \text{ A}}$.