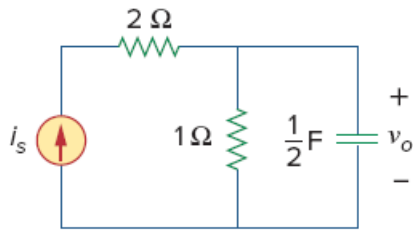


Problem

Find the voltage $v_o(t)$ in the circuit of Fig. 18.49. Let $i_s(t) = 8e^{-tu(t)}$ A.

Figure 18.49



Step-by-step solution

Step 1 of 4

Consider the following circuit diagram:

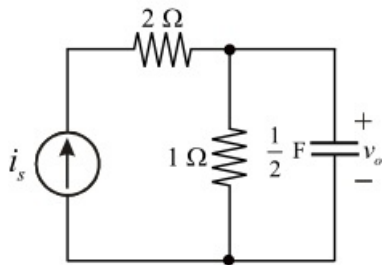


Figure 1

Step 2 of 4

Consider the current source in the circuit, $i_s = 8e^{-t}u(t)$.

Convert the time domain function i_s into the frequency domain using Fourier transform pair.

$$\begin{aligned} I_s &= \mathcal{F}(i_s) \\ &= \mathcal{F}[8e^{-t}u(t)] \\ &= 8\mathcal{F}[e^{-t}u(t)] \quad \left(\because e^{-at}u(t) \xleftrightarrow{\mathcal{F}} \frac{1}{a+j\omega} \right) \\ &= \frac{8}{j\omega+1} \end{aligned}$$

Write the frequency domain function for capacitor value.

$$\frac{1}{2} \text{ F} \longleftrightarrow \frac{1}{j\omega\left(\frac{1}{2}\right)}$$

Draw the Figure 1 in Frequency domain.

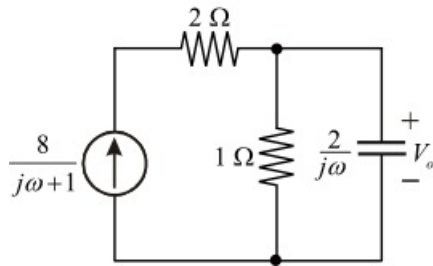


Figure 2

Step 3 of 4

Calculate the output voltage in frequency domain from Figure 2.

$$\begin{aligned} V_o &= \frac{2}{j\omega}(I_o) \\ &= \frac{2}{j\omega} \left(\frac{(1)I_s}{1+\frac{2}{j\omega}} \right) \\ &= \frac{2}{j\omega} \left(\frac{(j\omega)I_s}{j\omega+2} \right) \\ &= 2 \left(\frac{1}{j\omega+2} \right) \left(\frac{8}{j\omega+1} \right) \\ &= \frac{16}{(j\omega+2)(j\omega+1)} \end{aligned}$$

Solve the V_o using the residual partial fraction rule.

$$\begin{aligned} V_o &= \frac{16}{(j\omega+2)(j\omega+1)} \\ &= \frac{A}{(j\omega+2)} + \frac{B}{(j\omega+1)} \end{aligned}$$

Here A and B are constants.

Step 4 of 4

Calculate the constant value A , using the residue method.

$$\begin{aligned} A &= (j\omega + 2)V_o \Big|_{j\omega = -2} \\ &= (j\omega + 2) \left(\frac{16}{(j\omega + 1)(2 + j\omega)} \right) \Big|_{j\omega = -2} \\ &= \left(\frac{16}{(-2 + 1)} \right) \\ &= -16 \end{aligned}$$

Calculate the constant value B using the residue method.

$$\begin{aligned} B &= (j\omega + 1)V_o \Big|_{j\omega = -1} \\ &= (j\omega + 1) \left(\frac{16}{(j\omega + 2)(j\omega + 1)} \right) \Big|_{j\omega = -1} \\ &= \left(\frac{16}{(2 - 1)} \right) \\ &= 16 \end{aligned}$$

Substitute obtained A and B values in equation V_o .

$$V_o = \frac{16}{(j\omega + 1)} + \frac{-16}{(j\omega + 2)}$$

Apply the inverse Fourier transform to find $v(t)$.

$$\begin{aligned} v(t) &= \mathcal{F}^{-1}(V_o) \\ &= \mathcal{F}^{-1} \left[\frac{16}{(j\omega + 1)} + \frac{-16}{(j\omega + 2)} \right] \\ &= \mathcal{F}^{-1} \left(\frac{16}{(j\omega + 1)} \right) - \mathcal{F}^{-1} \left(\frac{16}{(j\omega + 2)} \right) \quad \left(\because e^{-at}u(t) \xleftrightarrow{\mathcal{F}} \frac{1}{a + j\omega} \right) \\ &= 16e^{-t}u(t) - 16e^{-2t}u(t) \\ &= 16(e^{-t} - e^{-2t})u(t) \text{ V} \end{aligned}$$

Thus, the output voltage $v(t)$ is $\boxed{16(e^{-t} - e^{-2t})u(t) \text{ V}}$.