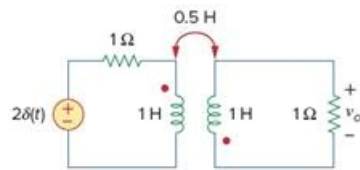


Problem

Determine $v_o(t)$ in the transformer circuit of Fig. 18.52.

Figure 18.52




Step-by-step solution

Step 1 of 3

Consider the circuit shown below:-

Step 2 of 3

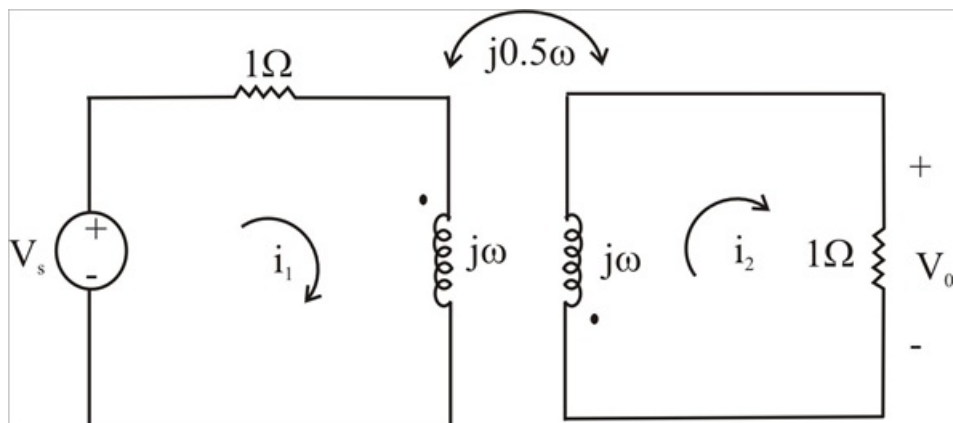

Step 3 of 3

$$\text{for loop 1.} \quad -2 + (1 + j\omega)I_2 + 0.5j\omega I_2 = 0 \quad -(1)$$

$$\text{for loop 2.} \quad (1 + j\omega)I_2 + j0.5\omega I_2 = 0$$

$$I_1 = \frac{(1 + j\omega)I_2}{-j0.5\omega} = \frac{-2(1 + j\omega)I_2}{j\omega}$$

Substituting this into (1)

$$2 = \frac{-2(1 + j\omega)I_2}{j\omega} + \frac{j\omega I_2}{2}$$

$$2j\omega = -\left(4 + j4\omega - \frac{3}{2}\omega^2\right)I_2$$

$$I_2 = \frac{2j\omega}{\left(4 + 4j\omega - 1.5\omega^2\right)}$$

$$V_o = I_2 = \frac{-2j\omega}{4 + j4\omega + (1.5j\omega^2)}$$

$$V_o = \frac{j\omega \frac{4}{3}}{\frac{8}{3} + j\frac{8\omega}{3} + (j\omega)^2}$$

$$= \frac{-4\left(\frac{4}{3} + j\omega\right)}{\left(\frac{4}{3} + j\omega\right)^2 + \left(\frac{\sqrt{8}}{3}\right)^2} + \frac{\frac{16}{3}}{\left(\frac{4}{3} + j\omega\right)^2 + \left(\frac{\sqrt{8}}{3}\right)^2}$$

$$v_o(t) = -4e^{\frac{4t}{3}} \cos\left(\frac{\sqrt{8}}{3}t\right)u(t) + 5.657e^{\frac{-4t}{3}} \sin\left(\frac{\sqrt{8}}{3}t\right)u(t) \text{ Volts}$$