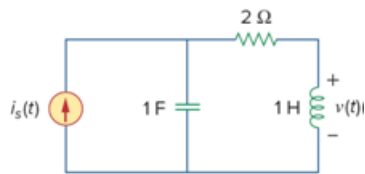


Problem

A band-limited signal has the following Fourier series representation: $i_s(t) = 10 + 8 \cos(2\pi t + 30^\circ) + 5 \cos(4\pi t - 150^\circ)$ mA

If the signal is applied to the circuit in Fig. 18.55, find $v(t)$.

Figure 18.55



Step-by-step solution

Step 1 of 4

Refer to Figure 18.55 in the textbook.

Draw the circuit as shown in Figure 1.

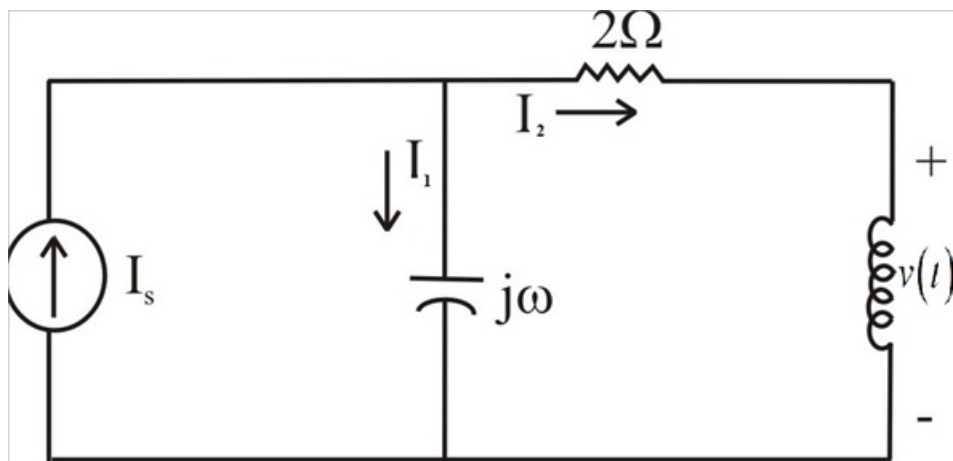


Figure 1

Step 2 of 4

Calculate the current I_2 .

Apply current division rule.

$$\begin{aligned}
 I_2 &= I_s \left(\frac{\left(\frac{1}{j\omega} \right)}{2 + j\omega + \left(\frac{1}{j\omega} \right)} \right) \\
 &= I_s \left(\frac{1}{2j\omega + (j\omega)^2 + 1} \right) \\
 &= I_s \left(\frac{1}{2j\omega - \omega^2 + 1} \right)
 \end{aligned}$$

Step 3 of 4

Determine the voltage across inductor $v(t)$.

$$v = j\omega I_s \left(\frac{1}{2j\omega - \omega^2 + 1} \right) \dots\dots (1)$$

Consider $i_s(t) = 10$.

For dc current, the voltage across inductor is zero.

Therefore, the voltage across inductor for dc current is zero.

Consider $i_s(t) = 8\cos(2\pi t + 30^\circ)$.

Replace 2π for ω in equation 1.

$$\begin{aligned} v &= \frac{8(2\pi|90^\circ)}{1 - (2\pi)^2 + j2(2\pi)} \\ &= \frac{8(2\pi|90^\circ)}{1 - 4\pi^2 + j4\pi} \\ &= \frac{50.27|90^\circ}{-38.48 + j12.566} \\ &= 1.2418|-71.92^\circ \text{ V} \end{aligned}$$

Step 4 of 4

Consider $i_s(t) = 5\cos(4\pi t - 150^\circ)$.

Replace 4π for ω in equation 1.

$$\begin{aligned} v &= \frac{5(4\pi|90^\circ)}{1 - (4\pi)^2 + j2(4\pi)} \\ &= \frac{5(4\pi|90^\circ)}{1 - 16\pi^2 + j8\pi} \\ &= \frac{62.83|90^\circ}{-156.91 + j25.13} \\ &= 0.3954|-80.9^\circ \text{ V} \end{aligned}$$

Write the voltage across inductor as,

$$\begin{aligned} v(t) &= 0 + 1.2418\cos(2\pi t - 71.92^\circ + 30^\circ) + 0.3954\cos(4\pi t - 80.9 - 150^\circ) \\ &= 1.2418\cos(2\pi t - 41.92^\circ) + 0.3954\cos(4\pi t - 230.9^\circ) \\ &= 1.2418\cos(2\pi t - 41.92^\circ) + 0.3954\cos(4\pi t + 129.1^\circ) \text{ mV} \end{aligned}$$

Therefore, the voltage across inductor is

$$\boxed{1.2418\cos(2\pi t - 41.92^\circ) + 0.3954\cos(4\pi t + 129.1^\circ) \text{ mV}}.$$