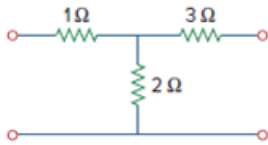


Problem

Obtain the y parameters for the T network shown in Fig. 19.16.

Figure 19.16




Step-by-step solution

Step 1 of 10

Refer to Figure 19.16 in the text book.

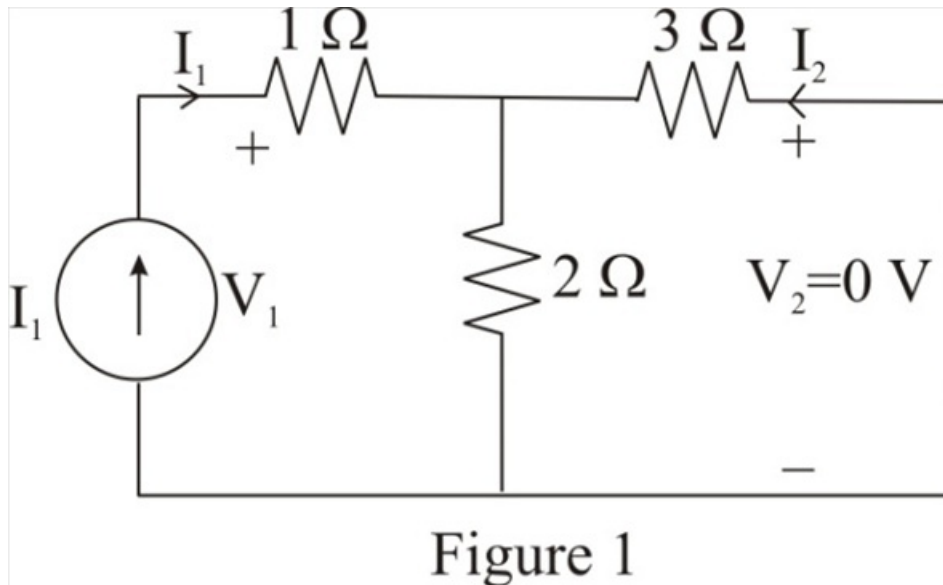Connect the current source I_1 as shown in Figure 1. Identify the currents and voltages in the circuit.



Step 2 of 10

Consider the expression for the voltage V_1 .

$$\begin{aligned} V_1 &= I_1 (1 + 2 \parallel 3) \\ &= I_1 \left(1 + \frac{(2)(3)}{2+3} \right) \\ &= I_1 \left(1 + \frac{6}{5} \right) \\ &= I_1 (1 + 1.2) \end{aligned}$$

$$V_1 = I_1 (2.2)$$

Therefore, the expression for the voltage V_1 is $I_1 (2.2)$.

Step 3 of 10

Consider the expression for the current $\mathbf{I_2}$.

$$\begin{aligned}\mathbf{I_2} &= -\mathbf{I_1} \left(\frac{2}{2+3} \right) \\ &= -\mathbf{I_1} \left(\frac{2}{5} \right) \\ &= -\mathbf{I_1} (0.4)\end{aligned}$$

Therefore, the expression for the current $\mathbf{I_2}$ is $-\mathbf{I_1} (0.4)$.

Step 4 of 10

Determine the expression for the short circuit input admittance $\mathbf{y_{11}}$.

$$\mathbf{y_{11}} = \frac{\mathbf{I_1}}{\mathbf{V_1}}$$

Substitute $\mathbf{I_1} (2.2)$ for $\mathbf{V_1}$.

$$\begin{aligned}\mathbf{Y_{11}} &= \frac{\mathbf{I_1}}{\mathbf{I_1} (2.2)} \\ &= 454.5 \text{ mS}\end{aligned}$$

Therefore, the expression for the short circuit input admittance $\mathbf{y_{11}}$ is 454.5 mS .

Step 5 of 10

Determine the value of the short circuit transfer admittance $\mathbf{y_{21}}$ from port-2 to port-1.

$$\mathbf{y_{21}} = \frac{\mathbf{I_2}}{\mathbf{V_1}}$$

Substitute $\mathbf{I_1} (2.2)$ for $\mathbf{V_1}$ and $-\mathbf{I_1} (0.4)$ for $\mathbf{I_2}$

$$\begin{aligned}\mathbf{y_{21}} &= \frac{-\mathbf{I_1} (0.4)}{\mathbf{I_1} (2.2)} \\ &= -181.82 \text{ mS}\end{aligned}$$

Therefore, the value of the short circuit transfer admittance $\mathbf{y_{21}}$ from port-2 to port-1 is

-181.82 mS .

Step 6 of 10

Connect the current source I_2 as shown in Figure 2. Identify the currents and voltages in the circuit.

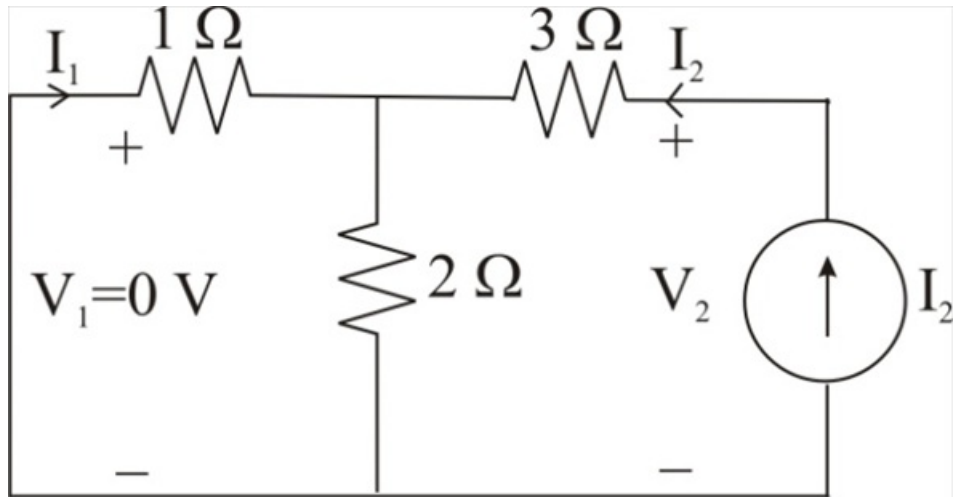


Figure 2

Step 7 of 10

Consider the expression for the voltage V_2 .

$$\begin{aligned} V_2 &= I_2 (3 + 2 \parallel 1) \\ &= I_2 \left(3 + \frac{(2)(1)}{2+1} \right) \\ &= I_2 \left(3 + \frac{2}{3} \right) \\ &= I_2 (3 + 0.667) \end{aligned}$$

$$V_2 = I_2 (3.667)$$

Therefore, the expression for the voltage V_2 is $I_2 (3.667)$.

Step 8 of 10

Consider the expression for the current I_1 .

$$\begin{aligned} I_1 &= -I_2 \left(\frac{2}{2+1} \right) \\ &= -I_2 \left(\frac{2}{3} \right) \\ &= -I_2 (0.667) \end{aligned}$$

Therefore, the expression for the current I_1 is $-I_2 (0.667)$.

Step 9 of 10

Determine the value of the short circuit transfer admittance y_{12} from port-1 to port-2.

$$y_{12} = \frac{I_1}{V_2}$$

Substitute $I_2(3.667)$ for V_2 and $-I_2(0.667)$ for I_1 .

$$\begin{aligned} y_{12} &= \frac{I_2(-0.667)}{I_2(3.667)} \\ &= -181.81 \text{ mS} \end{aligned}$$

Therefore, the value of the short circuit transfer admittance y_{12} from port-1 to port-2 is

$$\boxed{-181.82 \text{ mS}}.$$

Step 10 of 10

Determine the expression for the short circuit output admittance y_{22} .

$$y_{22} = \frac{I_2}{V_2}$$

Substitute $I_2(3.667)$ for V_2 .

$$\begin{aligned} y_{22} &= \frac{I_2}{I_2(3.667)} \\ &= 272.7 \text{ mS} \end{aligned}$$

Therefore, the expression for the short circuit output admittance y_{22} is $\boxed{272.7 \text{ mS}}$.