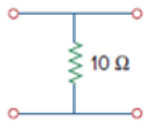


Problem

For the single-element two-port network in Fig. 19.64(a), y_{11} is:

- (a) 0
- (b) 5
- (c) 10
- (d) 20
- (e) undefined

Figure 19.64(a)



Step-by-step solution

Step 1 of 1

No exist