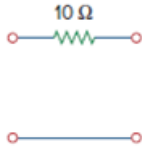


Problem

For the single-element two-port network in Fig. 19.64(b), h_{21} is:


- (a) $-0.$
- (b) -1
- (c) 0
- (d) 10
- (e) undefined

Figure 19.64(b)



Step-by-step solution

Step 1 of 1

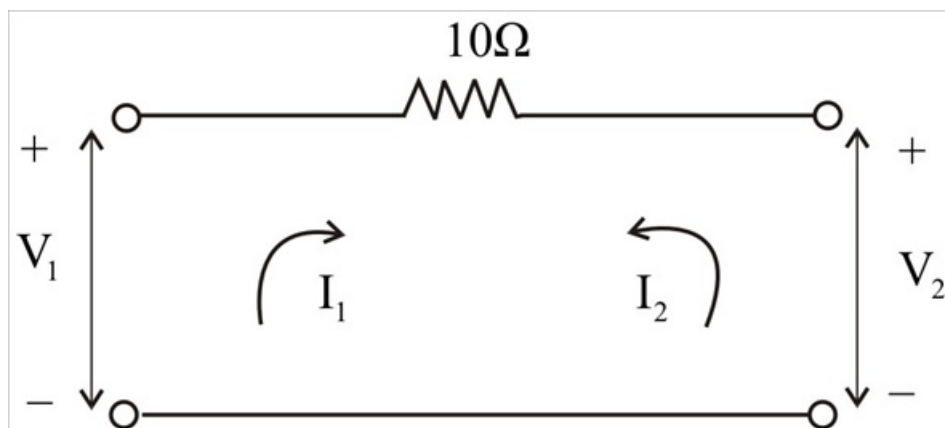

We have

$$10I_1 + 10I_2 = 0$$

$$\Rightarrow h_{21} = \frac{I_2}{I_1} = \frac{-10}{10} = -1$$