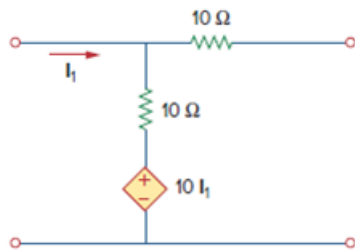


Problem

Compute the z parameters of the circuit in Fig. 19.70.

Figure 19.70



Step-by-step solution

Step 1 of 8

Refer to Figure 19.70 in the text book.

Connect the voltage source V_1 as shown in Figure 1. Identify the currents and voltages in the circuit.

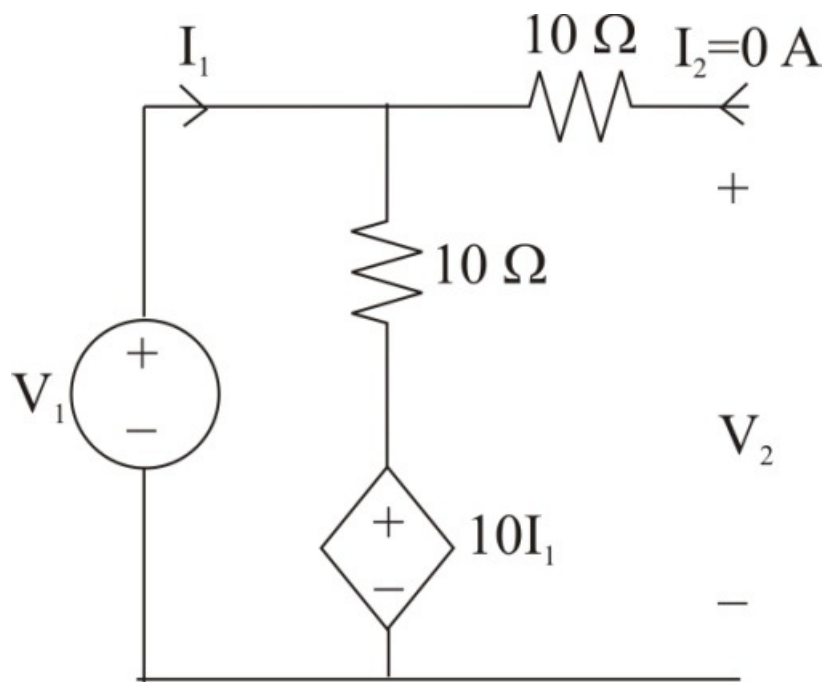


Figure 1

Step 2 of 8

Consider the expression for the voltage V_1 .

$$\begin{aligned} V_1 &= I_1(10) + 10I_1 \\ &= I_1(20) \end{aligned}$$

Therefore, the expression for the voltage V_1 is $I_1(20)$.

Consider the expression for the voltage V_2 .

$$\begin{aligned} V_2 &= I_1(10) + 10I_1 \\ &= I_1(20) \end{aligned}$$

Therefore, the expression for the voltage V_2 is $I_1(20)$.

Step 3 of 8

Determine the expression for the open circuit input impedance z_{11} .

$$z_{11} = \frac{V_1}{I_1}$$

Substitute $I_1(20)$ for V_1 .

$$\begin{aligned} z_{11} &= \frac{I_1(20)}{I_1} \\ &= 20 \Omega \end{aligned}$$

Therefore, the expression for the open circuit input impedance z_{11} is 20Ω .

Step 4 of 8

Determine the value of the open circuit transfer impedance z_{21} from port-2 to port-1.

$$z_{21} = \frac{V_2}{I_1}$$

Substitute $I_1(20)$ for V_2 .

$$\begin{aligned} z_{21} &= \frac{I_1(20)}{I_1} \\ &= 20 \Omega \end{aligned}$$

Therefore, the value of the open circuit transfer impedance z_{21} from port-2 to port-1 is

$$20 \Omega.$$

Step 5 of 8

Connect the voltage source V_2 as shown in Figure 2. Identify the currents and voltages in the circuit.

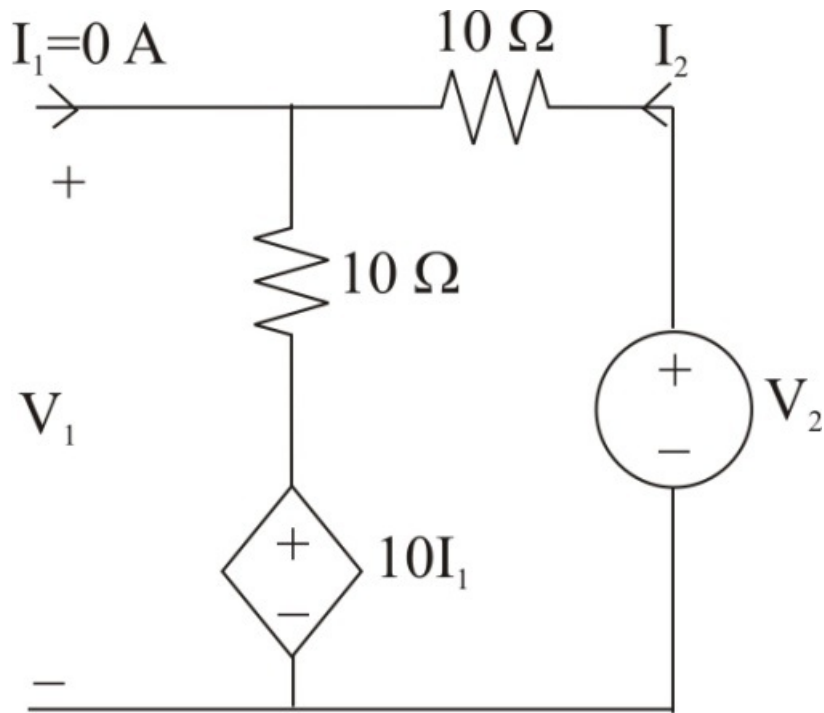


Figure 1

Step 6 of 8

Notice that the dependent source is shorted since the value of I_1 .

Consider the expression for the voltage V_2 .

$$\begin{aligned} V_2 &= I_2(10+10) \\ &= I_2(20) \end{aligned}$$

Therefore, the expression for the voltage V_2 is $I_2(20)$.

Consider the expression for the voltage V_1 .

$$V_1 = I_2(10)$$

Therefore, the expression for the voltage V_1 is $I_2(10)$.

Step 7 of 8

Determine the value of the open circuit transfer impedance z_{12} from port-1 to port-2.

$$z_{12} = \frac{V_1}{I_2}$$

Substitute $I_2(10)$ for V_1 .

$$\begin{aligned} z_{12} &= \frac{I_2(10)}{I_2} \\ &= 10 \Omega \end{aligned}$$

Therefore, the value of the open circuit transfer impedance z_{12} from port-1 to port-2 is

$$\boxed{10 \Omega}.$$

Step 8 of 8

Determine the expression for the open circuit output impedance $\mathbf{z_{22}}$.

$$\mathbf{z_{22}} = \frac{\mathbf{V_2}}{\mathbf{I_2}}$$

Substitute $\mathbf{I_2(20)}$ for $\mathbf{V_2}$.

$$\begin{aligned}\mathbf{z_{22}} &= \frac{\mathbf{I_2(20)}}{\mathbf{I_2}} \\ &= 20 \, \Omega\end{aligned}$$

Therefore, the expression for the open circuit output impedance $\mathbf{z_{22}}$ is $\mathbf{20 \, \Omega}$.