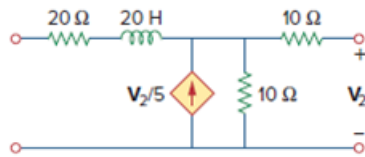


Problem

Calculate the z parameters of the circuit in Fig. 19.71 as functions of s .

Figure 19.71



Step-by-step solution

Step 1 of 10

Refer to Figure 19.71 in the text book.

Connect the voltage source $V_1(s)$ as shown in Figure 1. Represent the parameters in Laplace notation. Identify the currents and voltages in the circuit.

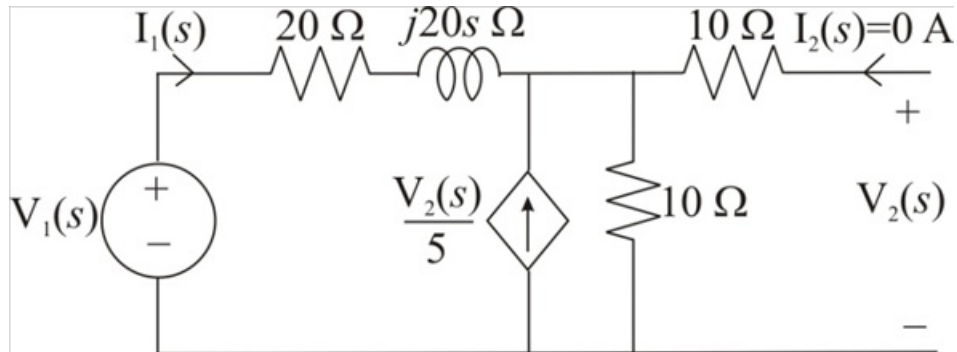


Figure 1

Step 2 of 10

Consider the expression for the voltage $V_2(s)$.

$$V_2(s) = \left[I_1(s) + \frac{V_2(s)}{5} \right] (10)$$

$$V_2(s) = 10I_1(s) + 2V_2(s)$$

$$2V_2(s) - V_2(s) = -10I_1(s)$$

$$V_2(s) = -10I_1(s)$$

Therefore, the expression for the voltage $V_2(s)$ is $-10I_1(s)$.

Step 3 of 10

Consider the expression for the voltage $V_1(s)$.

$$\begin{aligned} V_1(s) &= I_1(s)(20 + 20s) + \left[I_1(s) + \frac{V_2(s)}{5} \right](10) \\ &= I_1(s)(20 + 20s) + 10I_1(s) + 2V_2(s) \\ &= I_1(s)(20 + 20s + 10) + 2V_2(s) \end{aligned}$$

Substitute $-10I_1(s)$ for $V_2(s)$.

$$\begin{aligned} V_1(s) &= I_1(s)(30 + 20s) + 2[-10I_1(s)] \\ &= I_1(s)(30 + 20s) - 20I_1(s) \\ &= I_1(s)(30 + 20s - 20) \\ &= I_1(s)(10 + 20s) \end{aligned}$$

Therefore, the expression for the voltage $V_1(s)$ is $I_1(s)(10 + 20s)$.

Step 4 of 10

Determine the expression for the open circuit input impedance $z_{11}(s)$.

$$z_{11}(s) = \frac{V_1(s)}{I_1(s)}$$

Substitute $I_1(s)(10 + 20s)$ for $V_1(s)$.

$$\begin{aligned} z_{11}(s) &= \frac{I_1(s)(10 + 20s)}{I_1(s)} \\ &= 10 + 20s \, \Omega \end{aligned}$$

Therefore, the expression for the open circuit input impedance $z_{11}(s)$ is $10 + 20s \, \Omega$.

Step 5 of 10

Determine the value of the open circuit transfer impedance $z_{21}(s)$ from port-2 to port-1.

$$z_{21}(s) = \frac{V_2(s)}{I_1(s)}$$

Substitute $-10I_1(s)$ for $V_2(s)$.

$$\begin{aligned} z_{21}(s) &= \frac{-10I_1(s)}{I_1(s)} \\ &= -10 \, \Omega \end{aligned}$$

Therefore, the value of the open circuit transfer impedance $z_{21}(s)$ from port-2 to port-1 is

$$\boxed{-10 \, \Omega}.$$

Step 6 of 10

Connect the voltage source $\mathbf{V}_2(s)$ as shown in Figure 2. Identify the currents and voltages in the circuit.

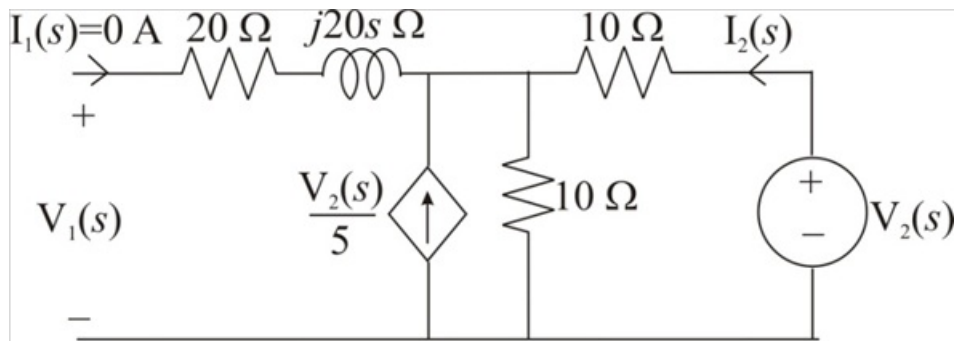


Figure 2

Step 7 of 10

Consider the expression for the voltage $\mathbf{V}_2(s)$.

$$\mathbf{V}_2(s) = \mathbf{I}_2(s)(10) + \left[\mathbf{I}_2(s) + \frac{\mathbf{V}_2(s)}{5} \right](10)$$

$$\mathbf{V}_2(s) = \mathbf{I}_2(s)(10) + 10\mathbf{I}_2(s) + 2\mathbf{V}_2(s)$$

$$2\mathbf{V}_2(s) - \mathbf{V}_2(s) = -20\mathbf{I}_2(s)$$

$$\mathbf{V}_2(s) = -20\mathbf{I}_2(s)$$

Therefore, the expression for the voltage $\mathbf{V}_2(s)$ is $-20\mathbf{I}_2(s)$.

Step 8 of 10

Consider the expression for the voltage $\mathbf{V}_1(s)$.

$$\mathbf{V}_1(s) = \left[\mathbf{I}_2(s) + \frac{\mathbf{V}_2(s)}{5} \right](10)$$

$$= 10\mathbf{I}_2(s) + 2\mathbf{V}_2(s)$$

Substitute $-20\mathbf{I}_2(s)$ for $\mathbf{V}_2(s)$.

$$\mathbf{V}_1(s) = 10\mathbf{I}_2(s) + 2[-20\mathbf{I}_2(s)]$$

$$= 10\mathbf{I}_2(s) - 40\mathbf{I}_2(s)$$

$$= -30\mathbf{I}_2(s)$$

Therefore, the expression for the voltage $\mathbf{V}_1(s)$ is $-30\mathbf{I}_2(s)$.

Step 9 of 10

Determine the value of the open circuit transfer impedance $\mathbf{z}_{12}(s)$ from port-1 to port-2.

$$\mathbf{z}_{12}(s) = \frac{\mathbf{V}_1(s)}{\mathbf{I}_2(s)}$$

Substitute $-30\mathbf{I}_2(s)$ for $\mathbf{V}_1(s)$.

$$\begin{aligned}\mathbf{z}_{12}(s) &= \frac{-30\mathbf{I}_2(s)}{\mathbf{I}_2(s)} \\ &= -30 \, \Omega\end{aligned}$$

Therefore, the value of the open circuit transfer impedance $\mathbf{z}_{12}(s)$ from port-1 to port-2 is

$$\boxed{-30 \, \Omega}.$$

Step 10 of 10

Determine the expression for the open circuit output impedance $\mathbf{z}_{22}(s)$.

$$\mathbf{z}_{22}(s) = \frac{\mathbf{V}_2(s)}{\mathbf{I}_2(s)}$$

Substitute $-20\mathbf{I}_2(s)$ for $\mathbf{V}_2(s)$.

$$\begin{aligned}\mathbf{z}_{22}(s) &= \frac{-20\mathbf{I}_2(s)}{\mathbf{I}_2(s)} \\ &= -20 \, \Omega\end{aligned}$$

Therefore, the expression for the open circuit output impedance $\mathbf{z}_{22}(s)$ is $\boxed{-20 \, \Omega}$.