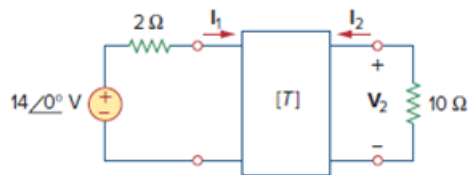


Problem

Find I_1 and I_2 if the transmission parameters for the two-port in Fig. 19.36 are

$$\begin{bmatrix} 5 & 10\Omega \\ 0.4\text{ S} & 1 \end{bmatrix}$$

Figure 19.36



Step-by-step solution

Step 1 of 6

Substituting the given ABCD parameters into

$$V_1 = AV_2 - BI_2$$


$$I_1 = CV_2 - DI_2$$

$$V_1 = 5V_2 - 10I_2 \quad \rightarrow (1)$$

$$I_1 = 0.4V_2 - I_2 \quad \rightarrow (2)$$

Step 2 of 6

Given circuit is

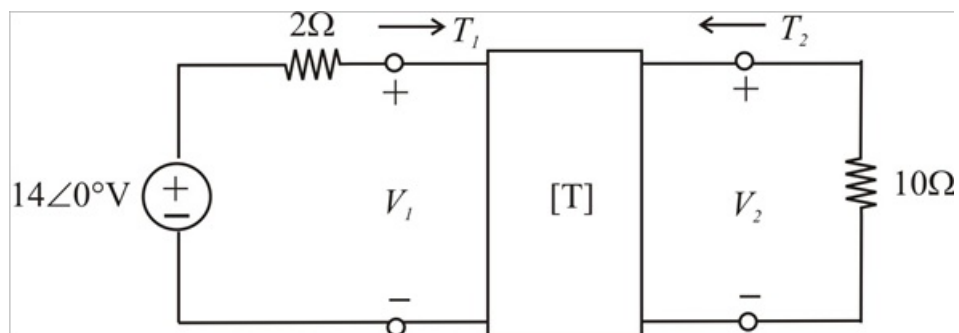

Step 3 of 6

Apply KVL, we get

$$-14 + 2I_1 + V_1 = 0$$

$$V_1 = 14 - 2I_1$$

Then

$$V_2 = -10I_2$$

Step 4 of 6

Substituting V_1, V_2 in equation (1) and (2), then $14 - 2I_1 = 5V_2 - 10I_2$

$$14 - 2I_1 = 5(-10I_2) - 10I_2$$

$$14 - 2I_1 + 60I_2 = 0$$

$$-I_1 + 30I_2 = -7$$

$$I_1 - 30I_2 = 7 \quad \rightarrow (3)$$

Step 5 of 6

Hence

$$I_1 = 0.4(-10I_2) - I_2$$

$$I_1 + 5I_2 = 0 \quad \rightarrow (4)$$

By solving (3) and (4) we obtain

$$I_1 - 30I_2 = 7$$

$$\begin{array}{r} I_1 + 5I_2 = 0 \\ -35I_2 = 7 \end{array}$$

$$I_2 = -\frac{1}{5}$$

$$\therefore \boxed{I_2 = -0.2\text{A}}$$

Step 6 of 6

From equation (4), we get

$$I_1 + 5(-0.2) = 0$$

$$\therefore \boxed{I_1 = 1\text{A}}$$