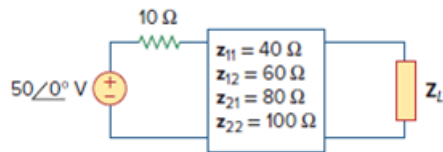


Problem

Determine the average power delivered to $Z_L = 5 + j4$ in the network of Fig. 19.74. *Note:* The voltage is rms.

Figure 19.74



Step-by-step solution

Step 1 of 7

Consider the following circuit diagram:

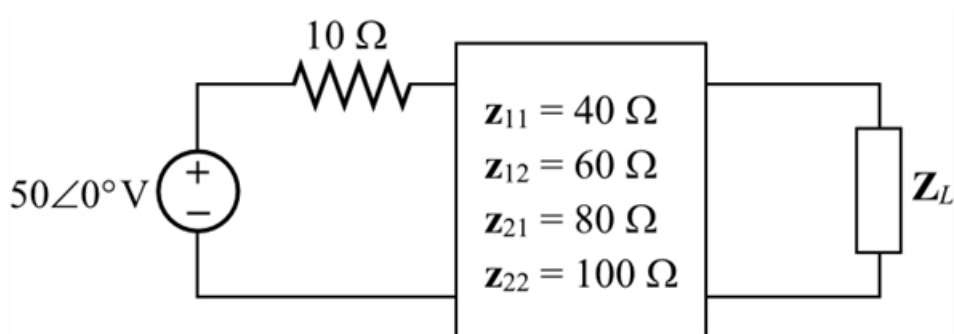


Figure 1

Step 2 of 7

Write the current and voltage expressions of $\mathbf{z}$ parameters.

$$\begin{aligned} \mathbf{V}_1 &= \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \\ &= 40\mathbf{I}_1 + 60\mathbf{I}_2 \quad \dots\dots (1) \end{aligned}$$

And,

$$\begin{aligned} \mathbf{V}_2 &= \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \\ &= 80\mathbf{I}_1 + 100\mathbf{I}_2 \quad \dots\dots (2) \end{aligned}$$

Step 3 of 7

Draw the circuit with voltage notations and current directions.

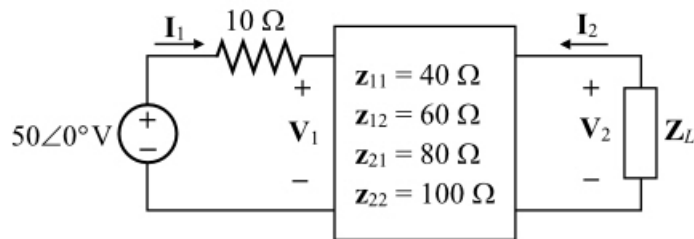


Figure 2

Step 4 of 7

Apply Kirchhoff's voltage law to the right side loop.

$$10\mathbf{I}_1 + \mathbf{V}_1 = 50\angle 0^\circ$$

$$\mathbf{V}_1 = 50\angle 0^\circ - 10\mathbf{I}_1 \dots\dots (3)$$

From Figure 2, the voltage across the load impedance:

$$\mathbf{V}_2 = -\mathbf{Z}_L \mathbf{I}_2$$

$$= -(5 + j4)\mathbf{I}_2 \dots\dots (4)$$

Step 5 of 7

Substitute $50\angle 0^\circ - 10\mathbf{I}_1$ for $\mathbf{V}_1$ in the equation (1).

$$50 - 10\mathbf{I}_1 = 40\mathbf{I}_1 + 60\mathbf{I}_2$$

$$50\mathbf{I}_1 + 60\mathbf{I}_2 = 50$$

$$5\mathbf{I}_1 + 6\mathbf{I}_2 = 5 \dots\dots (5)$$

Substitute $-(5 + j4)\mathbf{I}_2$ for $\mathbf{V}_2$ in the equation (1).

$$-(5 + j4)\mathbf{I}_2 = 80\mathbf{I}_1 + 100\mathbf{I}_2$$

$$80\mathbf{I}_1 = -100\mathbf{I}_2 - (5 + j4)\mathbf{I}_2$$

$$\mathbf{I}_1 = -\left(\frac{105 + j4}{80}\right)\mathbf{I}_2$$

$$= -(1.3125 + j0.05)\mathbf{I}_2 \dots\dots (6)$$

Step 6 of 7

Substitute $-(1.3125 + j0.05)\mathbf{I}_2$ for $\mathbf{I}_1$ in the equation (5).

$$-(5)(1.3125 + j0.05)\mathbf{I}_2 + 6\mathbf{I}_2 = 5$$

$$(-6.5625 - j0.25 + 6)\mathbf{I}_2 = 5$$

$$(0.5625 - j0.25)\mathbf{I}_2 = 5$$

$$\mathbf{I}_2 = \frac{5}{0.5625 - j0.25}$$

$$= -7.4226 + j3.2989$$

$$= 8.123\angle 156^\circ \text{ A}$$

Step 7 of 7

Calculate the average power delivered to the load.

$$\begin{aligned} P &= |\mathbf{I}_2|^2 Z_L \\ &= (8.123)^2 (5) \\ &= (65.98)(5) \\ &= 330 \text{ W} \end{aligned}$$

Therefore, the average power, P delivered to the load is 330 W.