

Problem


For the two-port circuit in Fig. 19.76,

$$[z] = \begin{bmatrix} 40 & 60 \\ 80 & 120 \end{bmatrix} \Omega$$

(a) Find Z_L for maximum power transfer to the load.

(b) Calculate the maximum power delivered to the load.

Figure 19.76

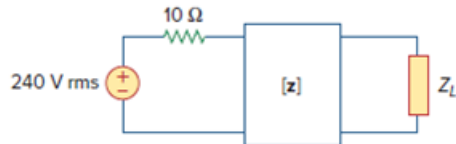


Step-by-step solution

Step 1 of 12


Refer to Figure 19.76 in the text book.

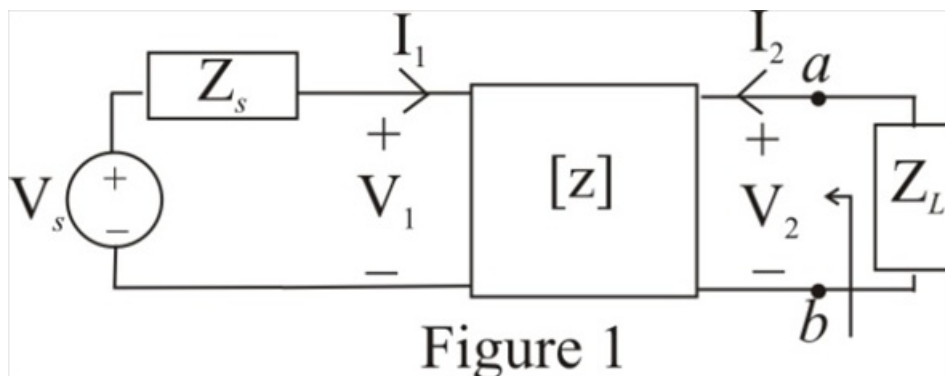Consider the circuit diagram shown in Figure 1



Step 2 of 12

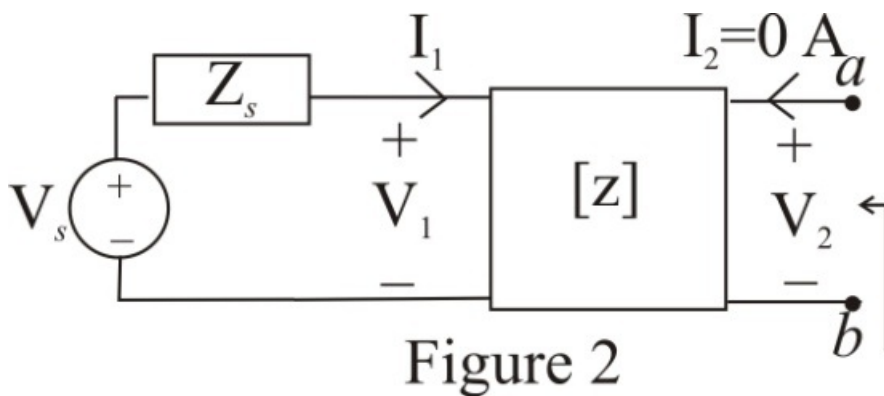Disconnect the load impedance and redraw the circuit.



Step 3 of 12

Consider the $\mathbf{z}$ -parameter equation at output port.

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$

Substitute 0 A for $\mathbf{I}_2$.

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}(0)$$

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1$$

$$\mathbf{I}_1 = \frac{\mathbf{V}_2}{\mathbf{z}_{21}}$$

Therefore, the expression for the current $\mathbf{I}_1$ is $\frac{\mathbf{V}_2}{\mathbf{z}_{21}}$.

Step 4 of 12

Consider the $\mathbf{z}$ -parameter equation at input port.

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

Substitute $\mathbf{V}_s - \mathbf{I}_1\mathbf{Z}_s$ for $\mathbf{V}_1$ and 0 A for $\mathbf{I}_2$.

$$\mathbf{V}_s - \mathbf{I}_1\mathbf{Z}_s = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}(0)$$

$$\mathbf{V}_s - \mathbf{I}_1\mathbf{Z}_s = \mathbf{z}_{11}\mathbf{I}_1$$

$$\mathbf{V}_s = (\mathbf{z}_{11} + \mathbf{Z}_s)\mathbf{I}_1$$

Substitute $\frac{\mathbf{V}_2}{\mathbf{z}_{21}}$ for $\mathbf{I}_1$.

$$\mathbf{V}_s = (\mathbf{z}_{11} + \mathbf{Z}_s)\left(\frac{\mathbf{V}_2}{\mathbf{z}_{21}}\right)$$

$$\mathbf{V}_2 = \mathbf{V}_s\left(\frac{\mathbf{z}_{21}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)$$

Here, the voltage $\mathbf{V}_s$ represents the Thevenin's voltage $\mathbf{V}_{Th}$.

$$\mathbf{V}_{Th} = \mathbf{V}_s\left(\frac{\mathbf{z}_{21}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right) \dots\dots (1)$$

Therefore, the value of the Thevenin's voltage $\mathbf{V}_{Th}$ across the terminals a-b is,

$$\mathbf{V}_s\left(\frac{\mathbf{z}_{21}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right).$$

Step 5 of 12

To find the Thevenin's impedance apply a voltage source at the output port and disconnect the source voltage as shown in Figure 3.

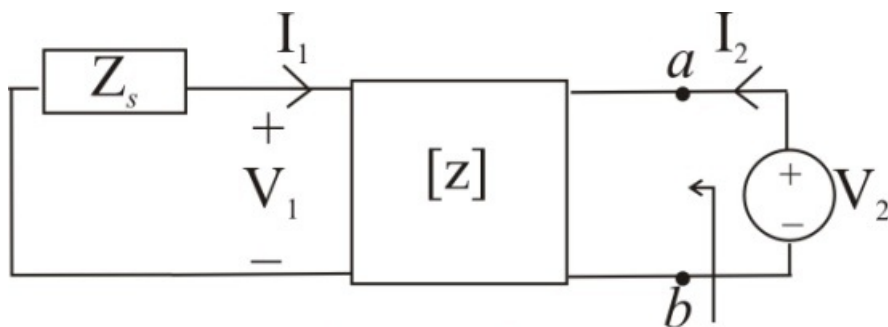


Figure 3

Step 6 of 12

Consider the $\mathbf{z}$ -parameter equation at input port.

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

Substitute $-\mathbf{I}_1\mathbf{Z}_s$ for $\mathbf{V}_1$.

$$-\mathbf{I}_1\mathbf{Z}_s = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

$$-\mathbf{I}_1\mathbf{Z}_s = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

$$(\mathbf{z}_{11} + \mathbf{Z}_s)\mathbf{I}_1 = -\mathbf{z}_{12}\mathbf{I}_2$$

$$\mathbf{I}_1 = -\left(\frac{\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)\mathbf{I}_2$$

Therefore, the expression for the current $\mathbf{I}_1$ is $-\left(\frac{\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)\mathbf{I}_2$.

Step 7 of 12

Consider the $\mathbf{z}$ -parameter equation at output port.

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$

Substitute $-\left(\frac{\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)\mathbf{I}_2$ for $\mathbf{I}_1$.

$$\mathbf{V}_2 = \mathbf{z}_{21}\left(-\left(\frac{\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)\mathbf{I}_2\right) + \mathbf{z}_{22}\mathbf{I}_2$$

$$\mathbf{V}_2 = \left(\mathbf{z}_{22} - \frac{\mathbf{z}_{21}\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)\mathbf{I}_2$$

$$\frac{\mathbf{V}_2}{\mathbf{I}_2} = \mathbf{z}_{22} - \frac{\mathbf{z}_{21}\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}$$

The ratio $\frac{\mathbf{V}_2}{\mathbf{I}_2}$ represents the Thevenin's impedance $\mathbf{Z}_{Th}$.

$$\mathbf{Z}_{Th} = \mathbf{z}_{22} - \frac{\mathbf{z}_{21}\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s} \dots\dots (2)$$

Therefore, the expression for the current $\mathbf{I}_1$ is $\frac{\mathbf{V}_2}{\mathbf{z}_{21}}$.

(a)

Recall equation (2).

$$\mathbf{Z}_{Th} = \mathbf{z}_{22} - \frac{\mathbf{z}_{21}\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}$$

Substitute $10\ \Omega$ for $\mathbf{Z}_s$, $40\ \Omega$ for $\mathbf{z}_{11}$, $60\ \Omega$ for $\mathbf{z}_{12}$, $80\ \Omega$ for $\mathbf{z}_{21}$ and $120\ \Omega$ for $\mathbf{z}_{22}$.

$$\begin{aligned}\mathbf{Z}_{Th} &= 120 - \frac{(80)(60)}{40 + 10} \\ &= 120 - \frac{4800}{50} \\ &= 120 - 96 \\ &= 24\ \Omega\end{aligned}$$

Therefore, the value of the Thevenin's impedance is, $24\ \Omega$.

To transfer the maximum power to the load, the value of the load impedance must be equal to the Thevenin's impedance. That is $\mathbf{Z}_L = 24\ \Omega$.

Step 8 of 12

(b)

Recall equation (1).

$$V_{Th} = V_s \left(\frac{z_{21}}{z_{11} + Z_s} \right)$$

Substitute 240 for V_s , 10Ω for Z_s , 40Ω for z_{11} and 80Ω for z_{21} .

$$\begin{aligned} V_{Th} &= (240) \left(\frac{80}{10 + 40} \right) \\ &= (240) \left(\frac{80}{50} \right) \\ &= (24)(16) \\ &= 384 \text{ Vrms} \end{aligned}$$

Therefore, the value of the Thevenin's voltage V_{Th} is 384 Vrms.

Step 9 of 12

Draw the Thevenin's equivalent circuit diagram.

Step 10 of 12

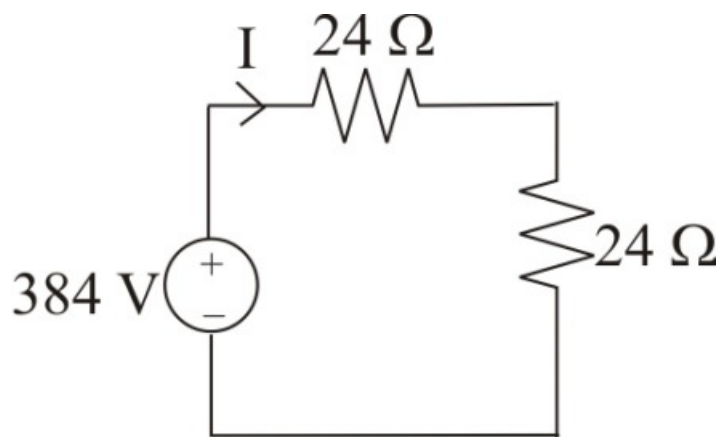


Figure 4

Step 11 of 12

Calculate the current passing in the circuit.

$$\begin{aligned} I &= \frac{384}{24 + 24} \\ &= \frac{384}{48} \\ &= 8 \text{ A rms} \end{aligned}$$

Therefore, the value of the current in the circuit is 8 A rms.

Step 12 of 12

Calculate the value of the maximum power absorbed by the load.

$$P_{\max} = \mathbf{I}^2 \mathbf{Z}_L$$

Substitute 8 A rms for $\mathbf{I}$ and $24 \, \Omega$ for $\mathbf{Z}_L$.

$$\begin{aligned} P_{\max} &= (8)^2 (24) \\ &= (64)(24) \\ &= 1.536 \text{ kW} \end{aligned}$$

Therefore, the value of the maximum power absorbed $P_{\max}$ by the load is 1.536 kW.