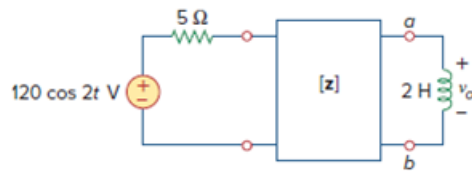


Problem

For the circuit in Fig. 19.77, at $\omega = 2 \text{ rad/s}$, $\mathbf{z}_{11} = 10 \Omega$, $\mathbf{z}_{12} = \mathbf{z}_{21} = j6 \Omega$, $\mathbf{z}_{22} = 4 \Omega$. Obtain the Thevenin equivalent circuit at terminals $a-b$ and calculate v_o .

Figure 19.77




Step-by-step solution

Step 1 of 13


Refer to Figure 19.77 in the text book.

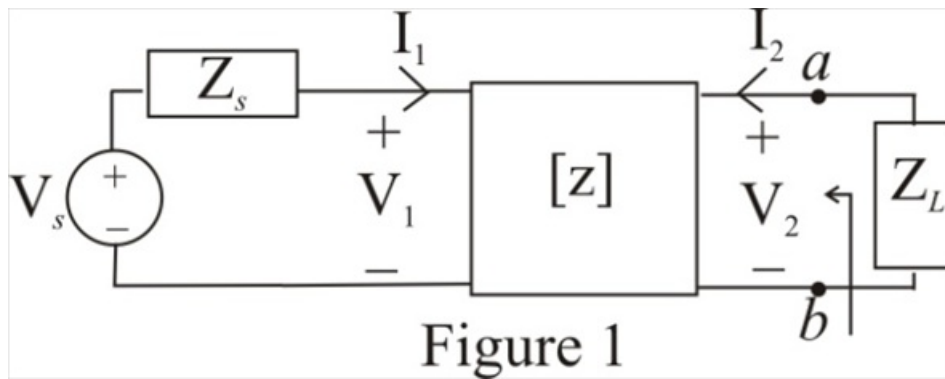Consider the circuit diagram shown in Figure 1



Step 2 of 13

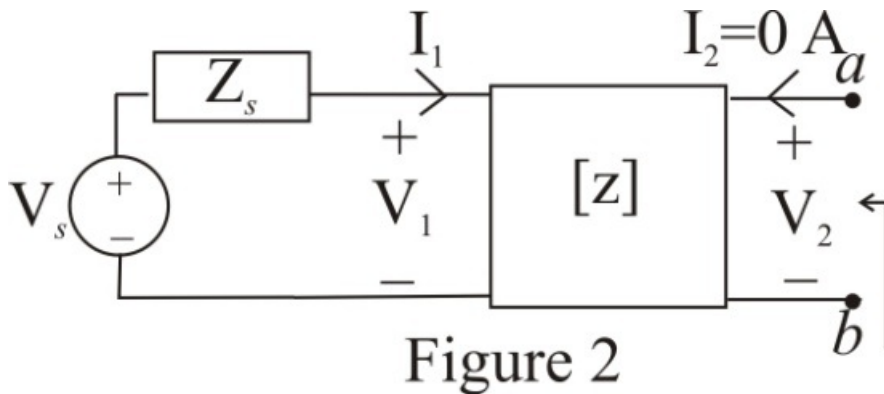Disconnect the load impedance and redraw the circuit.



Step 3 of 13

Consider the **z**-parameter equation at output port.

$$V_2 = z_{21}I_1 + z_{22}I_2$$

Substitute 0 A for I_2 .

$$V_2 = z_{21}I_1 + z_{22}(0)$$

$$V_2 = z_{21}I_1$$

$$I_1 = \frac{V_2}{z_{21}}$$

Therefore, the expression for the current I_1 is $\frac{V_2}{z_{21}}$.

Step 4 of 13

Consider the **z**-parameter equation at input port.

$$V_1 = z_{11}I_1 + z_{12}I_2$$

Substitute $V_s - I_1 Z_s$ for V_1 and 0 A for I_2 .

$$V_s - I_1 Z_s = z_{11}I_1 + z_{12}(0)$$

$$V_s - I_1 Z_s = z_{11}I_1$$

$$V_s = (z_{11} + Z_s)I_1$$

Substitute $\frac{V_2}{z_{21}}$ for I_1 .

$$V_s = (z_{11} + Z_s) \left(\frac{V_2}{z_{21}} \right)$$

$$V_2 = V_s \left(\frac{z_{21}}{z_{11} + Z_s} \right)$$

Here, the voltage V_s represents the Thevenin's voltage V_{Th} .

$$V_{Th} = V_s \left(\frac{z_{21}}{z_{11} + Z_s} \right) \dots\dots (1)$$

Therefore, the value of the Thevenin's voltage V_{Th} across the terminals a-b is,

$$V_s \left(\frac{z_{21}}{z_{11} + Z_s} \right).$$

Step 5 of 13

To find the Thevenin's impedance apply a voltage source at the output port and disconnect the source voltage as shown in Figure 3.

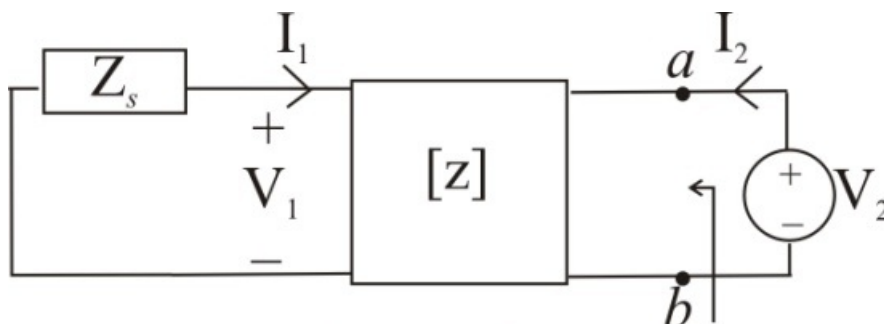


Figure 3

Step 6 of 13

Consider the **z**-parameter equation at input port.

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

Substitute $-\mathbf{I}_1\mathbf{Z}_s$ for $\mathbf{V}_1$.

$$-\mathbf{I}_1\mathbf{Z}_s = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

$$-\mathbf{I}_1\mathbf{Z}_s = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

$$(\mathbf{z}_{11} + \mathbf{Z}_s)\mathbf{I}_1 = -\mathbf{z}_{12}\mathbf{I}_2$$

$$\mathbf{I}_1 = -\left(\frac{\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)\mathbf{I}_2$$

Therefore, the expression for the current $\mathbf{I}_1$ is $-\left(\frac{\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)\mathbf{I}_2$.

Step 7 of 13

Consider the **z**-parameter equation at output port.

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$

Substitute $-\left(\frac{\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)\mathbf{I}_2$ for $\mathbf{I}_1$.

$$\mathbf{V}_2 = \mathbf{z}_{21}\left(-\left(\frac{\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)\mathbf{I}_2\right) + \mathbf{z}_{22}\mathbf{I}_2$$

$$\mathbf{V}_2 = \left(\mathbf{z}_{22} - \frac{\mathbf{z}_{21}\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}\right)\mathbf{I}_2$$

$$\frac{\mathbf{V}_2}{\mathbf{I}_2} = \mathbf{z}_{22} - \frac{\mathbf{z}_{21}\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}$$

The ratio $\frac{\mathbf{V}_2}{\mathbf{I}_2}$ represents the Thevenin's impedance $\mathbf{Z}_{Th}$.

$$\mathbf{Z}_{Th} = \mathbf{z}_{22} - \frac{\mathbf{z}_{21}\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s} \dots\dots (2)$$

Therefore, the expression for the current $\mathbf{I}_1$ is $\frac{\mathbf{V}_2}{\mathbf{z}_{21}}$.

Recall equation (2).

$$\mathbf{Z}_{Th} = \mathbf{z}_{22} - \frac{\mathbf{z}_{21}\mathbf{z}_{12}}{\mathbf{z}_{11} + \mathbf{Z}_s}$$

Substitute $5\ \Omega$ for $\mathbf{Z}_s$, $10\ \Omega$ for $\mathbf{z}_{11}$, $j6\ \Omega$ for $\mathbf{z}_{12}$, $j6\ \Omega$ for $\mathbf{z}_{21}$ and $4\ \Omega$ for $\mathbf{z}_{22}$.

$$\mathbf{Z}_{Th} = 4 - \frac{(j6)(j6)}{10 + 5}$$

$$= 4 + \frac{36}{15}$$

$$= 4 + 2.4$$

$$= 6.4\ \Omega$$

Therefore, the value of the Thevenin's impedance is, $6.4\ \Omega$.

Step 8 of 13

Consider the value of the voltage source.

$$v = 120 \cos 2t \text{ V}$$

Convert to phasor form.

$$\mathbf{V} = 120 \angle 0^\circ \text{ V}$$

Therefore, the value of the voltage source in phasor form is $120 \angle 0^\circ \text{ V}$

Step 9 of 13

Recall equation (1).

$$\mathbf{V}_{Th} = \mathbf{V}_s \left(\frac{\mathbf{z}_{21}}{\mathbf{z}_{11} + \mathbf{Z}_s} \right)$$

Substitute $120 \angle 0^\circ \text{ V}$ for $\mathbf{V}_s$, 5Ω for $\mathbf{Z}_s$, 10Ω for $\mathbf{z}_{11}$ and $j6 \Omega$ for $\mathbf{z}_{21}$.

$$\begin{aligned} \mathbf{V}_{Th} &= (120 \angle 0^\circ) \left(\frac{j6}{10 + 5} \right) \\ &= (120 \angle 0^\circ) \left(\frac{6 \angle 90^\circ}{15} \right) \\ &= (8 \angle 0^\circ) (6 \angle 90^\circ) \\ &= 48 \angle 90^\circ \text{ V} \end{aligned}$$

Therefore, the value of the Thevenin's voltage $\mathbf{V}_{Th}$ is $48 \angle 90^\circ \text{ V}$.

Step 10 of 13

Calculate the reactance due to the load inductance.

$$\mathbf{X}_L = j\omega L$$

Substitute 2 rad/s for ω and 2 H for L .

$$\begin{aligned} \mathbf{X}_L &= j(2)(2) \\ &= j4 \Omega \end{aligned}$$

Therefore, the value of the reactance due to inductance is $j4 \Omega$.

Step 11 of 13

Draw the Thevenin's equivalent circuit diagram.

Step 12 of 13

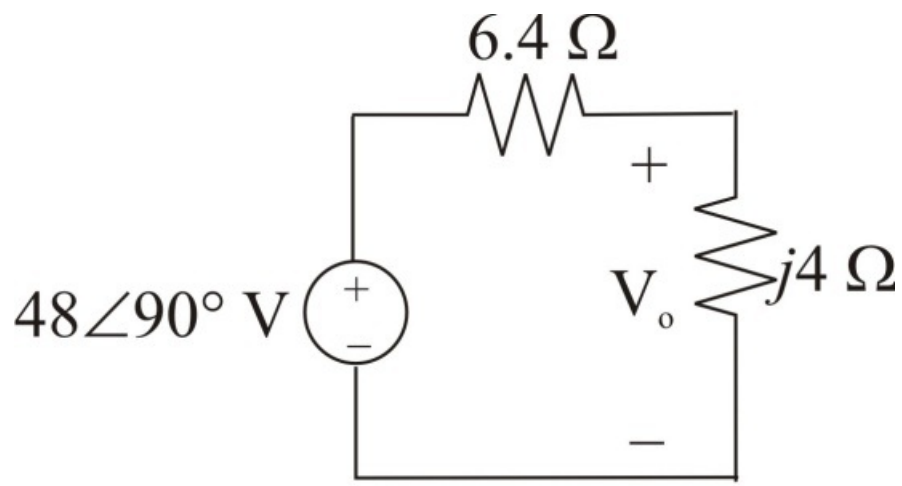


Figure 4

Step 13 of 13

Calculate the voltage $\mathbf{V_o}$ using voltage division rule.

$$\begin{aligned}\mathbf{V_o} &= (48\angle 90^\circ) \left(\frac{j4}{6.4 + j4} \right) \\ &= (48\angle 90^\circ)(0.281 + j0.449) \\ &= (48\angle 90^\circ)(0.53\angle 57.96^\circ) \\ &= 25.44\angle 147.96^\circ \text{ V}\end{aligned}$$

Convert the voltage to time domain.

$$v_o = 25.44 \cos(2t + 147.96^\circ) \text{ V}$$

Therefore, the value of the output voltage is $25.44 \cos(2t + 147.96^\circ) \text{ V}$.