

Problem

Realize the following transfer function using an LC ladder network terminated in a $1\text{-}\Omega$ resistor:


$$H(s) = \frac{2}{s^3 + s^2 + 4s + 2}$$

Step-by-step solution

Step 1 of 8

The denominator of the given transfer function is a third – order network, so that the LC ladder network with two inductors and one capacitor.

Step 2 of 8

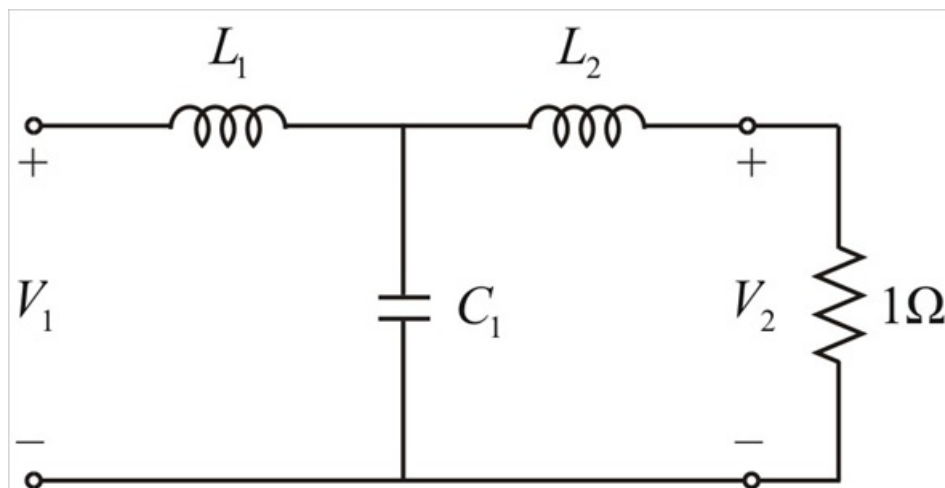

Step 3 of 8

The terms in the denominator into odd or even groups, then

$$D(s) = (s^3 + 4s) + (s^2 + 2)$$

Hence

$$H(s) = \frac{2}{(s^3 + 4s) + (s^2 + 2)}$$

Divide the numerator and denominator by the odd parts of the denominator, we get

$$H(s) = \frac{\frac{2}{s^3 + 4s}}{1 + \frac{s^2 + 2}{s^3 + 4s}} \text{ ---- (1)}$$

By the admittance parameters

$$H(s) = \frac{-y_{21}}{y_L + y_{22}} \text{ ---- (2)}$$

Where $y_L = 1$ by comparing equations (1), (2), we get

$$y_{21} = \frac{-2}{s^3 + 4s}$$


$$y_{22} = \frac{s^2 + 2}{s^3 + 4s}$$

Step 4 of 8

y_{22} will automatically realize y_{21} , y_{22} is the output driving – point admittance, the admittance of the network with the input port short – circuited. Thus, y_{22} is the short – circuit output admittance

We short – circuit the input port then circuit is

Step 5 of 8

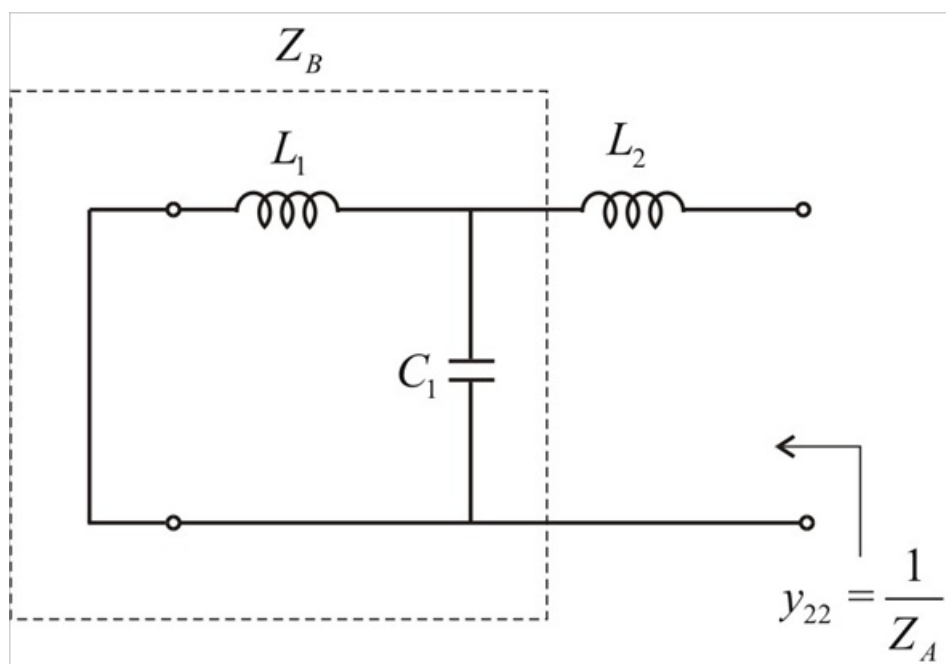

Step 6 of 8

To get L_3 , let

$$Z_A = \frac{1}{y_{22}}$$

$$Z_A = \frac{s^3 + 4s}{s^2 + 2}$$

$$Z_A = \frac{s(s^2 + 4)}{s^2 + 2}$$

We get $Z_A = sL_2 + Z_B$ ----- (3)

Thus, by Long division method,

$$\begin{array}{r} s^2 + 2 \overline{) s^3 + 4s} \quad (s \\ \underline{s^3 + 2s} \\ 2s \end{array}$$


Hence $Z_A = s + \frac{2s}{s^2 + 2}$ ----- (4)

Comparing equation (3) and (4), we get

$$\therefore \boxed{L_2 = 1\text{H}}$$

$$Z_B = \frac{2s}{s^2 + 2}$$

Step 7 of 8

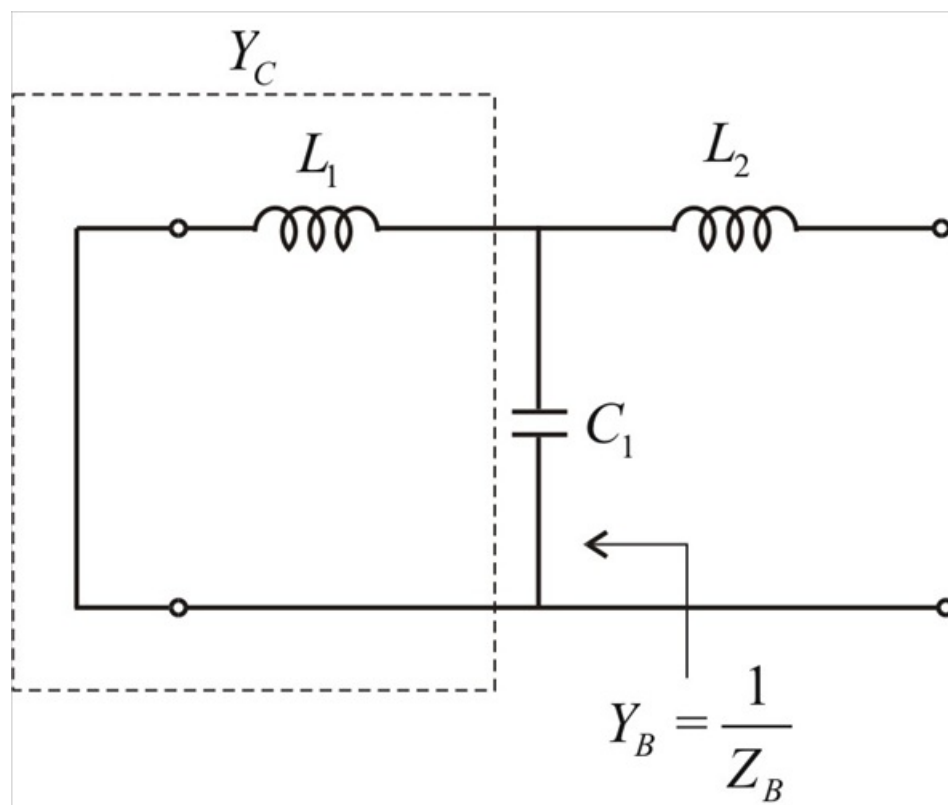

Step 8 of 8

Let $Y_B = \frac{1}{Z_B}$

$$Y_B = \frac{s^2 + 2}{2s}$$

$$Y_B = \frac{s}{2} + \frac{1}{s} \text{ ----- (5)}$$

$$Y_B = sC_1 + Y_C \text{ ----- (6)}$$

By comparing (5) and (6), we get

$$\boxed{\therefore C_1 = 0.5 \text{ F}}$$

$$Y_C = \frac{1}{s}$$

$$Y_C = \frac{1}{sL_1}$$

Then $\boxed{L_1 = 1\text{H}}$

Thus, the LC ladder network with $L_1 = L_2 = 1\text{H}$, $C_1 = 0.5 \text{ F}$