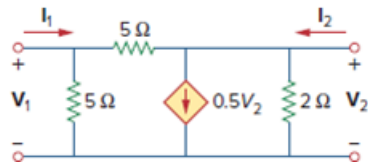


Problem

Obtain the y parameters of the two-port network in Fig. 19.83.

Figure 19.83



Step-by-step solution

Step 1 of 8

Consider the following circuit diagram:

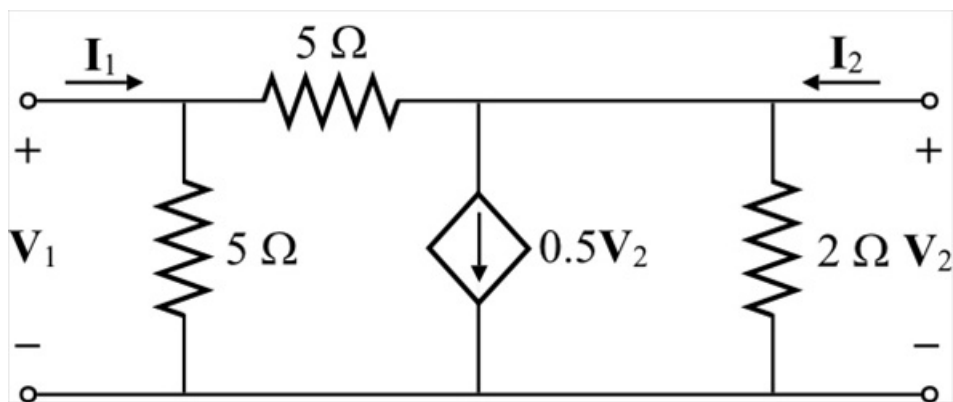


Figure 1

Step 2 of 8

Write the y -parameters.

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \dots (1)$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \dots (2)$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \dots (3)$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \dots (4)$$

Step 3 of 8

To calculate parameters y_{11} and y_{21} , short circuit the output source, and connect a test voltage source to the input port. Draw the modified circuit diagram.

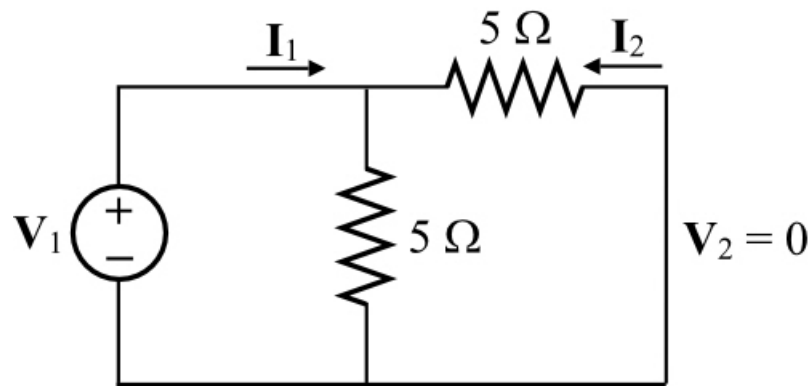


Figure 2

Step 4 of 8

Apply Kirchhoff's voltage law to the right side loop.

$$5(I_2 - I_1) + 5I_2 = 0$$

$$-5I_1 + (5 + 5)I_2 = 0$$

$$10I_2 = 5I_1$$

$$I_2 = \frac{I_1}{2}$$

Step 5 of 8

Apply Kirchhoff's voltage law to the left side loop.

$$V_1 = 5(I_2 + I_1)$$

$$= 5\left(-\frac{I_1}{2} + I_1\right)$$

$$= 5\left(\frac{-I_1 + 2I_1}{2}\right)$$

$$= \frac{5I_1}{2}$$

Step 6 of 8

Calculate the parameter y_{11} .

$$\begin{aligned} y_{11} &= \frac{I_1}{V_1} \\ &= \frac{I_1}{\left(\frac{5I_1}{2}\right)} \\ &= \frac{2}{5} \\ &= 0.4 \text{ S} \end{aligned}$$

Calculate the parameter y_{21} .

$$\begin{aligned} y_{21} &= \frac{I_2}{V_1} \\ &= \frac{I_1}{\frac{5I_1}{2}} \\ &= \frac{2}{5} \\ &= \frac{1}{5} \\ &= 0.2 \text{ S} \end{aligned}$$

To calculate the parameters y_{12} and y_{22} , short the input port and connect a test voltage source to the output port.

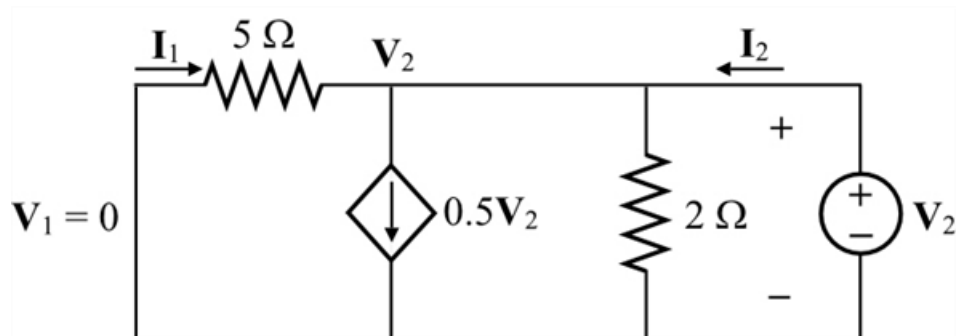


Figure 2

Step 7 of 8

Apply Kirchhoff's current law at node V_2 .

$$\begin{aligned} \frac{V_2}{5} + 0.5V_2 + \frac{V_2}{2} &= I_2 \\ (0.2 + 0.5 + 0.5)V_2 &= I_2 \\ 1.2V_2 &= I_2 \\ \frac{I_2}{V_2} &= 1.2 \text{ S} \\ y_{22} &= 1.2 \text{ S} \end{aligned}$$

Step 8 of 8

Apply Kirchhoff's current law at node V_2 .

$$0.5V_2 + \frac{V_2}{2} = I_1 + I_2$$

$$0.5V_2 + \frac{V_2}{2} = I_1 + 1.2V_2$$

$$(0.5 + 0.5 - 1.2)V_2 = I_1$$

$$-0.2V_2 = I_1$$

$$\frac{I_1}{V_2} = -0.2 \text{ S}$$

$$y_{12} = -0.2 \text{ S}$$

Therefore, the y parameters, $\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$ are $\boxed{\begin{bmatrix} 0.4 & -0.2 \\ 0.2 & 1.2 \end{bmatrix} \text{ S}}$.