

## Problem

Draw the two-port network that has the following  $y$  parameters:

$$[y] = \begin{bmatrix} 1 & -0.5 \\ -0.5 & 1.5 \end{bmatrix} \text{S}$$

## Step-by-step solution

## Step 1 of 1

$$[Y] = \begin{bmatrix} 1 & -0.5 \\ -0.5 & 1.5 \end{bmatrix}$$

$$Y_{11} - Y_{12} = 0.5\text{S} \quad Y_{22} - Y_{12} = 1\text{S}$$

