


Problem

The h parameters of the two-port of Fig. 19.95 are:

$$[h] = \begin{bmatrix} 600\ \Omega & 0.04 \\ 30 & 2\ \text{mS} \end{bmatrix}$$

Given the $Z_s = 2\ \text{k}\Omega$ and $Z_L = 400\ \Omega$, find Z_{in} and Z_{out} .

Figure 19.95

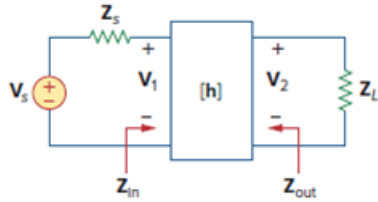

Step-by-step solution

Step 1 of 4

Consider the following circuit diagram:

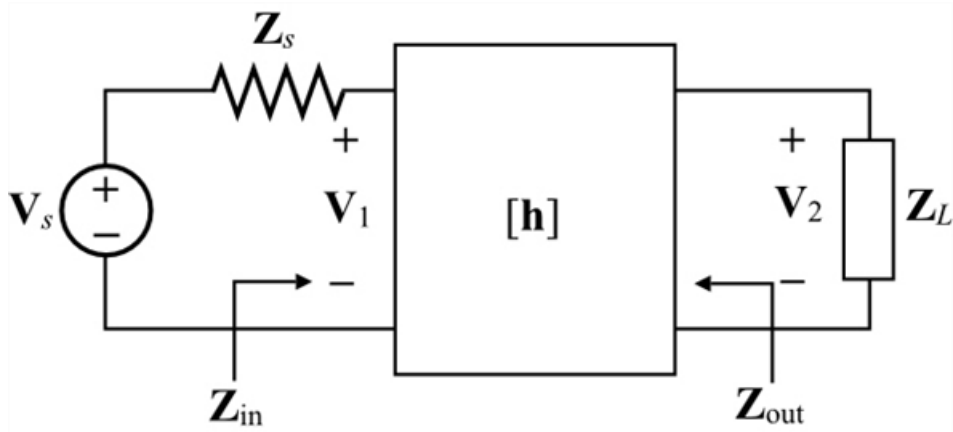


Figure 1

Step 2 of 4

Draw the equivalent circuit diagram of Figure 1.

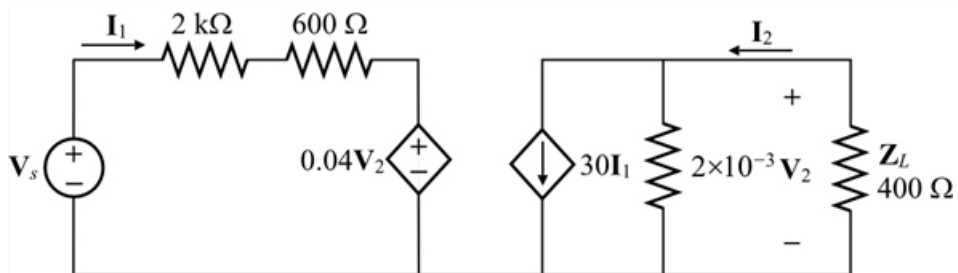


Figure 2

Step 3 of 4

Calculate the input impedance.

$$\begin{aligned}Z_{\text{in}} &= \mathbf{h}_{11} - \frac{\mathbf{h}_{12}\mathbf{h}_{21}R_L}{1 + \mathbf{h}_{22}R_L} \\&= 600 - \frac{(0.04)(30)(400)}{1 + (0.002)(400)} \\&= 600 - \frac{480}{1 + 0.8} \\&= 600 - \frac{480}{1.8} \\&= 600 - 266.67 \\&= 333.33 \, \Omega\end{aligned}$$

Therefore, the input impedance, Z_{in} is $\boxed{333.33 \, \Omega}$.

Step 4 of 4

Calculate the output impedance.

$$\begin{aligned}Z_{\text{out}} &= \frac{R_s + \mathbf{h}_{11}}{(\mathbf{h}_{22} + \mathbf{h}_{21}R_s) - \mathbf{h}_{12}\mathbf{h}_{21}} \\&= \frac{2000 + 600}{(2000 + 600)(0.002) - (30)(0.04)} \\&= \frac{2600}{(2600)(0.002) - 1.2} \\&= \frac{2600}{5.2 - 1.2} \\&= \frac{2600}{4} \\&= 650 \, \Omega\end{aligned}$$

Therefore, the output impedance, Z_{out} is $\boxed{650 \, \Omega}$.