

Problem

The h parameters of a two-port device are given by

$$\begin{aligned} h_{11} &= 600 \, \Omega, & h_{12} &= 10^{-3}, & h_{21} &= 120, \\ h_{22} &= 2 \times 10^{-6} \, \text{S} \end{aligned}$$

Draw a circuit model of the device including the value of each element.

Step-by-step solution

Step 1 of 2

Draw the equivalent model circuit including given h -parameters values.

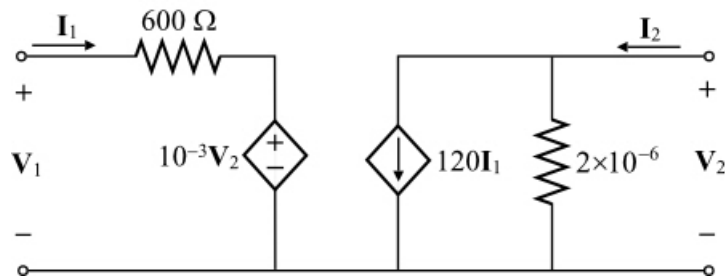


Figure 1

Step 2 of 2

Hence, the Circuit shown in Figure 1 is the circuit model of the device including each value element.