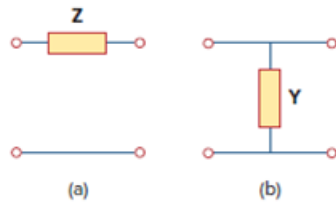


Problem

Find the transmission parameters for the single-element two-port networks in Fig. 19.98.

Figure 19.98



Step-by-step solution

Step 1 of 7

Refer to Figure 19.98 in the textbook.

For part (a), redraw the Figure.

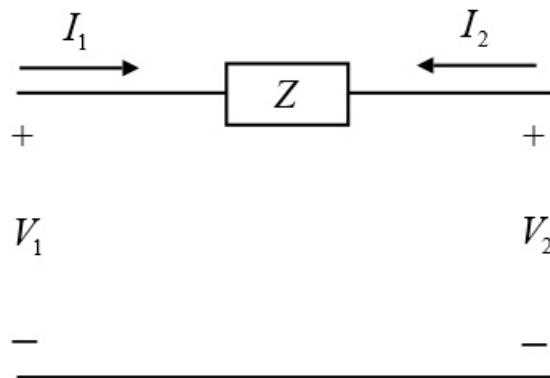


Figure 1

Step 2 of 7

Write the transmission equation.

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

For Transmission parameter A ,

$$I_2 = 0$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$A = \frac{V_1}{V_1}$$

$$= 1$$

For Transmission parameter B ,

$$V_2 = 0$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0}$$

$$I_2 = -I_1$$

$$A = \frac{V_1}{I_1}$$

$$= \frac{V_1}{V_1}$$

$$Z$$

$$= Z \Omega.$$

Step 3 of 7

For Transmission parameter C ,

$$I_2 = 0$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$I_1 = -I_2$$

$$= 0$$

$$C = \frac{0}{V_2}$$

$$= 0$$

For Transmission parameter D ,

$$V_2 = 0$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$$

$$I_1 = -I_2$$

$$D = \frac{1}{1}$$

$$= 1$$

Therefore, the transmission parameters are $A = 1, B = Z \Omega, C = 0, D = 1$.

Step 4 of 7

For part (b), redraw the Figure.

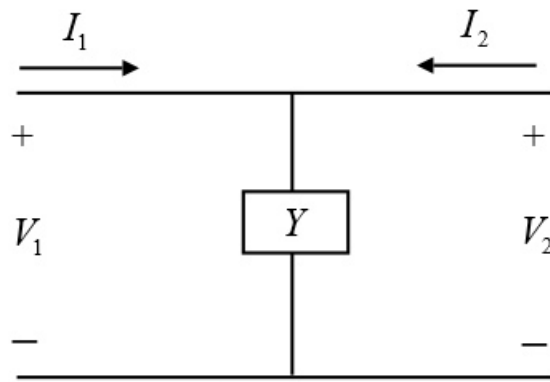


Figure 2

Step 5 of 7

Write the transmission equation.

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

For Transmission parameter A ,

$$I_2 = 0$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$V_2 = V_1$$

$$A = \frac{V_1}{V_1}$$

$$= 1$$

Step 6 of 7

For Transmission parameter B ,

$$V_2 = 0$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0}$$

$$V_1 = V_2$$

$$B = \frac{0}{-I_2}$$

$$= 0$$

Step 7 of 7

For Transmission parameter C ,

$$I_2 = 0$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$V_2 = V_1$$

$$C = \frac{I_1}{V_1}$$
$$= Y S$$

For Transmission parameter D ,

$$V_2 = 0$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$$

Since, voltage across Y is 0.

$$I_1 = -I_2$$

$$D = \frac{1}{1}$$
$$= 1$$

Therefore, the transmission parameters are $A = 1, B = 0 \Omega, C = Y S, D = 1$.