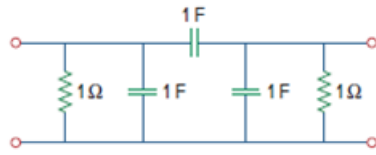


Problem


Using impedances in the s -domain, obtain the transmission parameters for the circuit in Fig. 19.103.

Figure 19.103



Step-by-step solution

Step 1 of 7

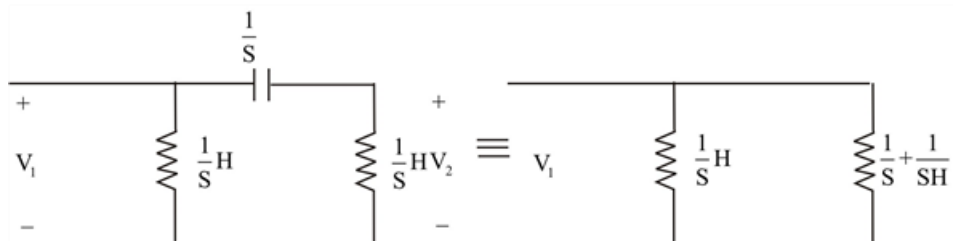


Step 2 of 7

$$\begin{aligned}
 I_2 &= \frac{I_1 \times \left(\frac{1}{s} + 1 \right)}{\frac{1}{s+1} + \frac{1}{s} + \frac{1}{s} + 1} \\
 &= \frac{I_1 \left(\frac{1}{s+1} \right)}{\frac{2s+s+1}{(s+1)s}} = \frac{sI_1}{3s+1} \\
 V_1 &= I_1 \left(\frac{1}{s+1} \parallel \left(\frac{1}{s} + \frac{1}{s+1} \right) \right) \\
 V_1 &= I_1 \left(\frac{1}{s+1} \parallel \frac{2s+1}{s(s+1)} \right) \\
 &= I_1 \left(\frac{\frac{2s+1}{s(s+1)}}{\frac{3s+1}{s(s+1)}} \right) = \frac{I_1 (2s+1)}{(3s+1)(s+1)}
 \end{aligned}$$

Step 3 of 7


$$\begin{aligned}
 \frac{V_1}{V_2} &= \frac{I_1 (2s+1)}{(3s+1)(s+1)} \times \frac{(3s+1) \times (s+1)}{sI_1} \cdot \frac{2s+1}{(s+1)} (s+1) \\
 A &= \frac{2s+1}{s(s+1)} \times (s+1) \cdot 2 + \frac{1}{s}
 \end{aligned}$$

Step 4 of 7

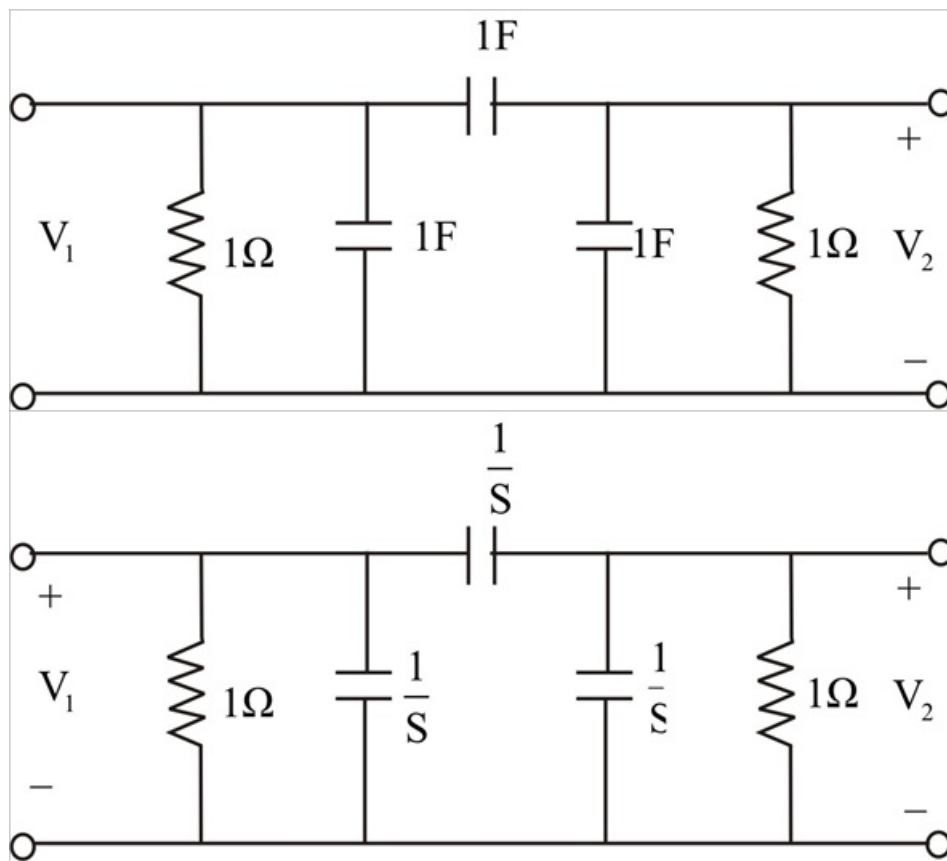

Step 5 of 7
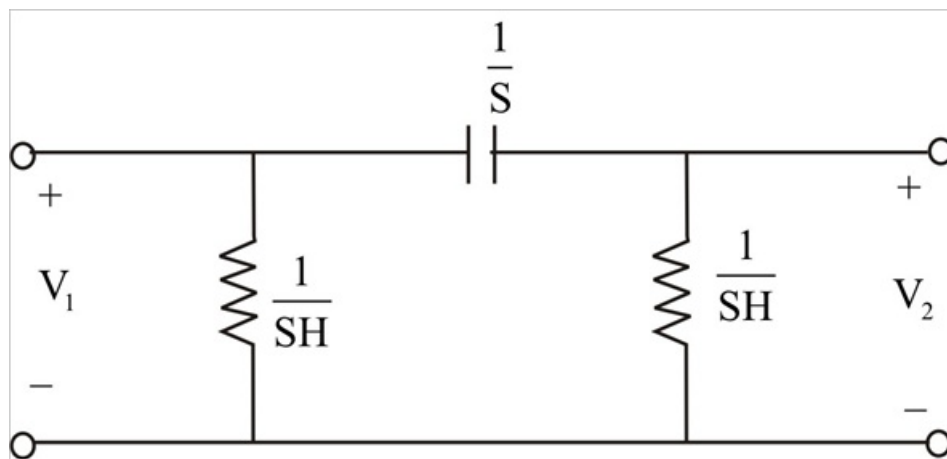
$$\left(1 \parallel \frac{1}{s}\right) = \frac{\frac{1}{s}}{1 + \frac{1}{s}} = \frac{1}{s+1}$$



Step 6 of 7

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$B = \left. \frac{-V_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$



$$D = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

Setting $I_2 = 0$

$$\frac{V_1}{V_2} = \frac{2S+1(+S1)}{S(S+1)}$$

$$\Rightarrow \frac{I_1(2S+1)}{(3S+1)(S+1)V_2} = \frac{2S+1}{S(S+1)}$$
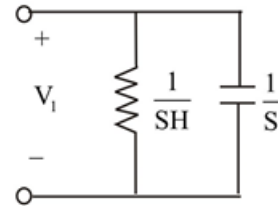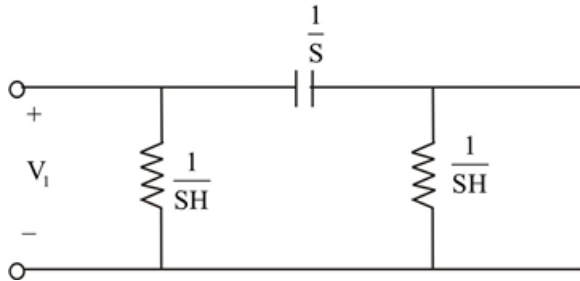
$$\frac{I_1}{V_2} = \frac{(3S+1)(S+1)}{S}$$



Step 7 of 7

$$B = \frac{-V_2}{I_2} = \frac{+I_1 \left(\frac{1}{S} + 1 \right)}{\frac{1}{S} + 1 + \frac{1}{S}} = I_2$$

$$= \frac{+I_1 \left(\frac{1}{S} \times \frac{1}{S+1} \right) \times \left(\frac{1}{S} + \frac{1}{S} + 1 \right)}{\left(\frac{1}{S} + \frac{1}{S+1} \right) \times I_1 \left(\frac{1}{S} + 1 \right)} = \frac{1}{S}$$

$$D = \frac{-I_1}{I_2}$$

$$= \frac{-I_1 \left(\frac{1}{S+1} + \frac{1}{S} \right)}{+I_1 \left(\frac{1}{S} + 1 \right)} = \frac{(2S+1)}{S} = 2 + \frac{1}{S}$$

$$= \begin{bmatrix} 2 + \frac{1}{S} & \frac{1}{S} \\ \frac{(3S+1)(S+1)}{S} & 2 + \frac{1}{S} \end{bmatrix}$$