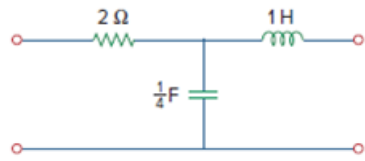


Problem


Derive the s -domain expression for the t parameters of the circuit in Fig. 19.104.

Figure 19.104




Step-by-step solution

Step 1 of 7

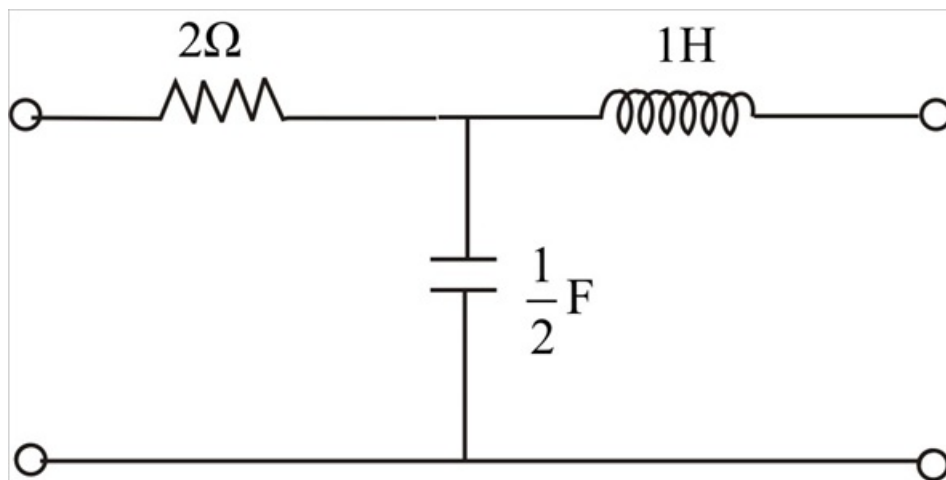


Step 2 of 7

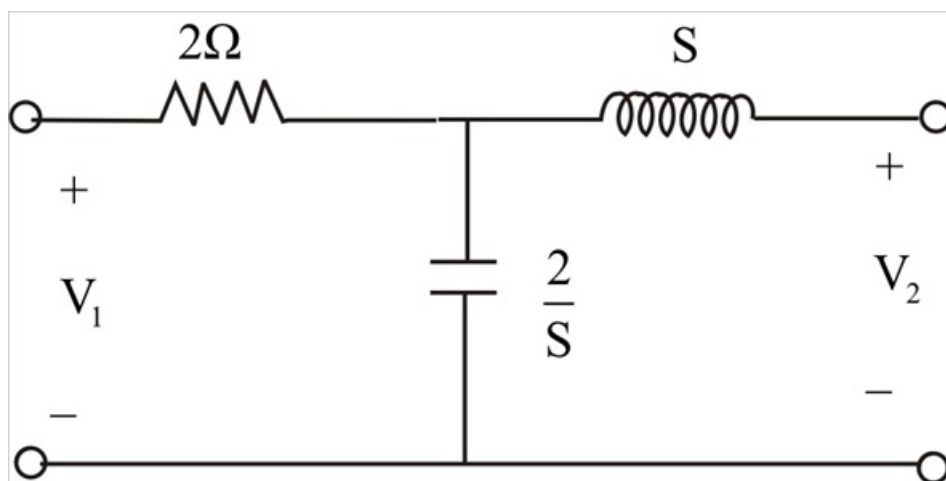

Step 3 of 7

$$a = \left. \frac{V_2}{V_1} \right|_{I_1=0} \quad b = \left. \frac{-V_2}{I_1} \right|_{V_1=0} \quad c = \left. \frac{I_2}{V_1} \right|_{I_1=0} \quad d = \left. \frac{-I_2}{I_1} \right|_{V_1=0}$$

From $I_1 = 0$

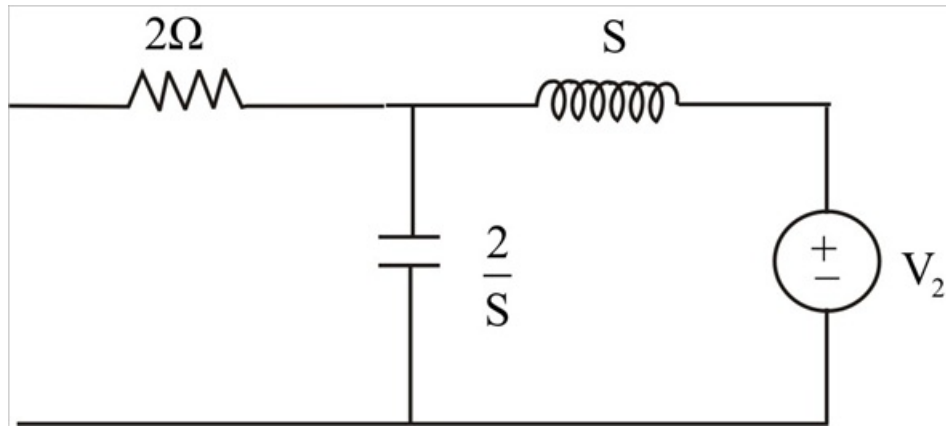


Step 4 of 7

$$\begin{aligned} \frac{V_a}{V_1} &= \frac{V_1 \frac{1}{\sqrt{\left(S + \frac{2}{S}\right) \times \frac{2}{S}}}}{V_1} \\ &= \frac{\frac{1}{\frac{2}{S}}}{\left(S + \frac{2}{S}\right)} = \frac{\frac{1}{2}}{S^2 + 2} = \frac{S^2 + 2}{2} \\ C &= \frac{I_2}{V_1} = \frac{\frac{V_2}{S + \frac{2}{S}}}{\frac{V_2}{S + \frac{2}{S}} \times \frac{2}{S}} = \frac{S}{2} \end{aligned}$$

Step 5 of 7

For $V_1 = 0$

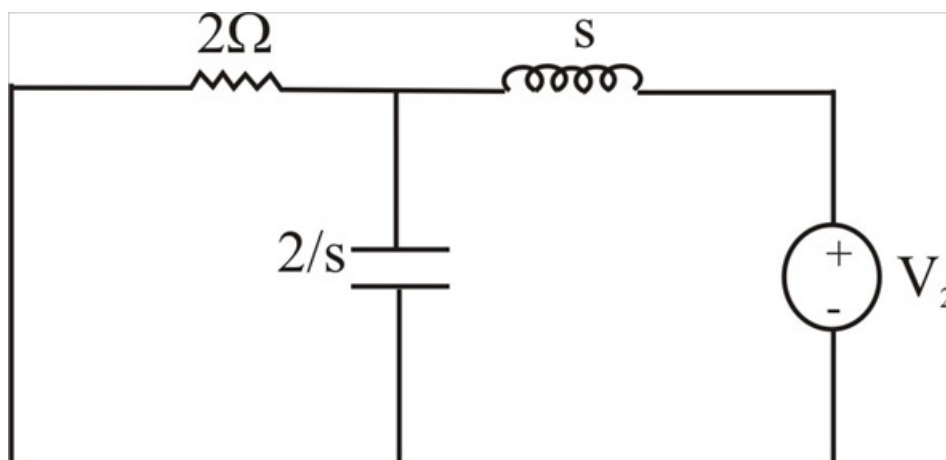

Step 6 of 7

$$\begin{aligned}
\frac{-V_2}{I_1} &= \frac{-V_2}{\left(I_2 + \frac{2}{S}\right)\left(\frac{2}{S} + 2\right)} \\
&= \frac{-I_2 \left(2 \parallel \frac{2}{S} + s\right)}{\frac{I_2 \frac{2}{S}}{\frac{(2S+2)}{S}}} \\
&= \frac{-\frac{4}{S}}{\frac{2S + \frac{2}{S}}{1}} + S \\
&= \frac{-4 + 2S^2 + 2S}{(2S+2)} = -2(S^2 + S + 2)
\end{aligned}$$

Step 7 of 7

$$\frac{-I_2}{I_1} = \frac{-I_2}{I_2 \left(\frac{2}{S}\right) \times \frac{1}{2 + \frac{2}{S}}} = \frac{-1}{\frac{2}{S} \left(\frac{1}{\frac{2S+2}{S}}\right)} = -(S+1)$$

$a = \frac{S^2 + 2}{2}$	$b = -2(S^2 + S + 2)$	$c = \frac{S}{2}$	$a = (-S + 1)$
-------------------------	-----------------------	-------------------	----------------