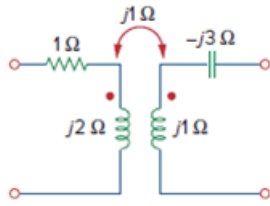


Problem

Obtain the t parameters for the network in Fig. 19.105.

Figure 19.105



Step-by-step solution

Step 1 of 8

Refer to Figure 19.105 in the textbook for the circuit.

Write the expressions for t -parameters.

$$a = \left. \frac{V_2}{V_1} \right|_{I_1=0} \quad b = \left. \frac{-V_2}{I_1} \right|_{V_1=0}$$

$$c = \left. \frac{I_2}{V_1} \right|_{I_1=0} \quad d = \left. \frac{-I_2}{I_1} \right|_{V_1=0}$$

Here,

a = Open circuit voltage gain.

b = Negative short circuit transfer impedance

c = Open circuit transfer admittance

d = Negative short circuit current gain

Step 2 of 8

To determine a and c , leave the input port open so that $I_1 = 0$ and place a voltage source V_2 at the output port.

Redraw the circuit as shown in Figure 1.

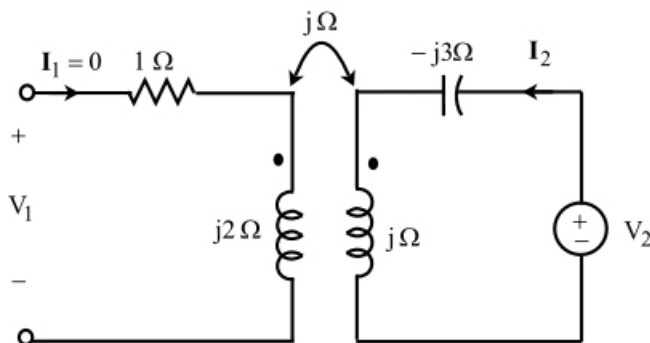


Figure 1

Step 3 of 8

Apply kirchhoff's voltage law at the output port.

$$\begin{aligned} V_2 &= I_2(j - j3) \\ &= -j2I_2 \end{aligned}$$

Apply kirchhoff's voltage law at the input port.

$$\begin{aligned} V_1 &= I_1(1\Omega + j2) + (j\Omega)(-I_2) \\ &= 0 - jI_2 \quad (\text{since } I_1 = 0) \\ &= -jI_2 \end{aligned}$$

Step 4 of 8

Determine the parameters a and c.

$$\begin{aligned} a &= \left. \frac{V_2}{V_1} \right|_{I_1=0} \\ &= \frac{-j2I_2}{-jI_2} \\ &= 2 \end{aligned}$$

$$\begin{aligned} c &= \left. \frac{I_2}{V_1} \right|_{I_1=0} \\ &= \frac{I_2}{-jI_2} \\ &= j \end{aligned}$$

Step 5 of 8

To determine b and d, short circuit the input port so that $V_1 = 0$ and place a voltage source V_2 at the output port.

Redraw the circuit as shown in Figure 2.

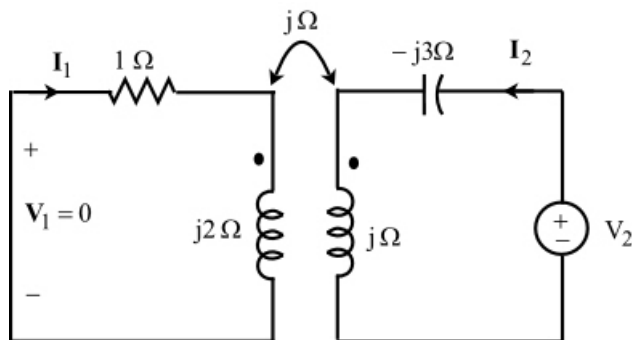


Figure 2

Step 6 of 8

Apply kirchhoff's voltage law to the mesh 1.

$$0 = I_1(1\Omega + j2) - jI_2$$

$$I_2 = I_1 \left(\frac{1\Omega + j2}{j} \right)$$

$$\frac{I_2}{I_1} = 2 - j$$

Step 7 of 8

Apply kirchhoff's voltage law to the mesh 2.

$$\begin{aligned} \mathbf{V}_2 &= \mathbf{I}_2(j - j3) - j(\mathbf{I}_1) \\ &= -j2\mathbf{I}_2 - j\mathbf{I}_1 \end{aligned}$$

Substitute $(2 - j)\mathbf{I}_1$ for $\mathbf{I}_2$.

$$\begin{aligned} \mathbf{V}_2 &= -j2((2 - j)\mathbf{I}_1) - j\mathbf{I}_1 \\ &= \mathbf{I}_1(-j4 - 2 - j) \end{aligned}$$

$$\frac{\mathbf{V}_2}{\mathbf{I}_1} = -j5 - 2$$

Step 8 of 8

Determine the parameters b and d.

$$\begin{aligned} b &= \left. \frac{-\mathbf{V}_2}{\mathbf{I}_1} \right|_{\mathbf{V}_1=0} \\ &= -(-j5 - 2) \\ &= 2 + j5 \end{aligned}$$

$$\begin{aligned} d &= \left. \frac{-\mathbf{I}_2}{\mathbf{I}_1} \right|_{\mathbf{V}_1=0} \\ &= -(2 - j) \\ &= j - 2 \end{aligned}$$

Therefore, the t-parameters for the network is,

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix} = \begin{bmatrix} 2 & 2 + j5 \\ j & j - 2 \end{bmatrix}.$$