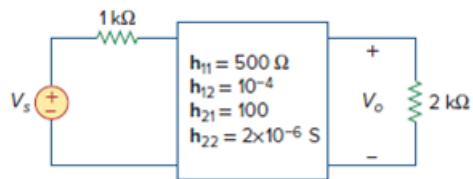


Problem

For the network of Fig. 19.107, obtain V_o/V_s .

Figure 19.107



Step-by-step solution

Step 1 of 4

Consider the following h parameter network:

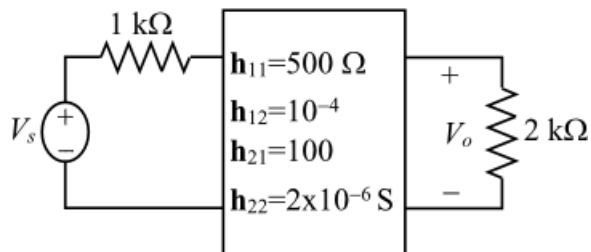


Figure 1

Step 2 of 4

Draw the equivalent h parameter circuit.

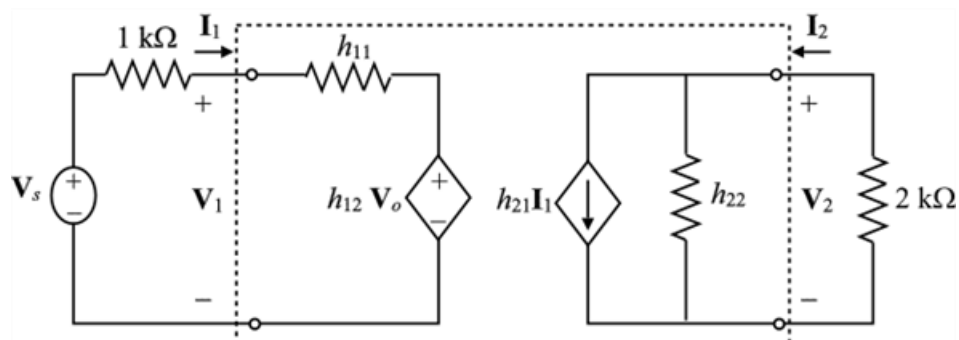


Figure 2: Equivalent h -parameter circuit

Step 3 of 4

Apply Kirchhoff's voltage law to the input loop.

$$-V_s + 10^3 I_1 + V_1 = 0$$

$$V_1 + 1000 I_1 = V_s$$

Substitute $h_{11} I_1 + h_{12} V_o$ for V_1 .

$$h_{11} I_1 + h_{12} V_o + 1000 I_1 = V_s$$

Substitute 500 for h_{11} and 10^{-4} for h_{12} .

$$500 I_1 + 10^{-4} V_o + 1000 I_1 = V_s$$

$$10^{-4} V_o + 1500 I_1 = V_s \dots\dots (1)$$

Apply Kirchhoff's voltage law to the output loop.

$$I_2 = h_{22} V_o + h_{21} I_1$$

Substitute 2×10^{-6} for h_{22} and 100 for h_{21} .

$$I_2 = 2 \times 10^{-6} V_o + 100 I_1$$

$$\text{Also, } I_2 = -\frac{V_o}{2000}$$

Substitute $-\frac{V_o}{2000}$ for I_2 .

$$-\frac{V_o}{2000} = 2 \times 10^{-6} V_o + 100 I_1$$

$$100 I_1 = -\frac{V_o}{2000} - 2 \times 10^{-6} V_o$$

$$100 I_1 = -5.02 \times 10^{-4} V_o$$

$$I_1 = -5.02 \times 10^{-6} V_o$$

Step 4 of 4

Substitute $-5.02 \times 10^{-6} V_o$ for I_1 in equation (1).

$$10^{-4} V_o + (1500)(-5.02 \times 10^{-6} V_o) = V_s$$

$$10^{-4} V_o - 7.53 \times 10^{-3} V_o = V_s$$

$$-7.43 \times 10^{-3} V_o = V_s$$

$$\frac{V_o}{V_s} = \frac{1}{-7.43 \times 10^{-3}}$$

$$\frac{V_o}{V_s} = -134.6$$

Thus, the ratio, $\frac{V_o}{V_s}$ is -134.6.