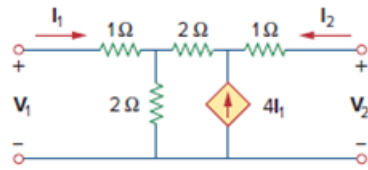


Problem

Use *PSpice* or *MultiSim* to rework Prob. 19.31.

Determine the hybrid parameters for the network in Fig. 19.89.

Figure 19.89



Step-by-step solution

Step 1 of 9

Consider the following circuit diagram:

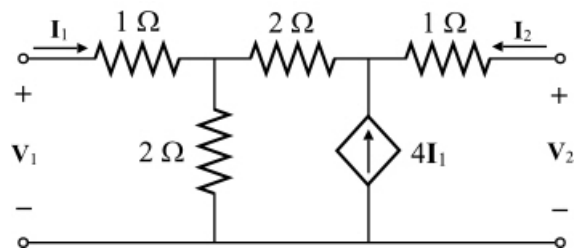


Figure 1

Step 2 of 9

Write the hybrid parameters.

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \dots\dots (1)$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \dots\dots (2)$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad \dots\dots (3)$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \quad \dots\dots (4)$$

Step 3 of 9

PSpice analysis:

- Open the CIS Demo software.
- Once you are in the capture session frame, click on the menu item File, select new, and then click on Project.
- In the New Project box, type 'selected file name' in the Name text box. Ensure that the Analog or Mixed-signal circuit Wizard is activated.
- Connected the circuit diagram as per the Circuit.
- Double click on each component and enter the given values.
- Click the New Simulation Profile icon and enter a name in the Name text box. You will need to enter the appropriate settings for this project in the Simulation
- Setting box. Click the Analysis tab, and select Bias Point from the Analysis type list. Click OK and save the document.
- Click on the run icon. You will observe the A/D Demo screen. When you close this screen, you will observe the bias voltages and currents.

Step 4 of 9

To calculate the values of h_{11} and h_{21} parameters, connect a 1 V test voltage source to input port and short circuit the output port.

The following is the PSpice schematic:

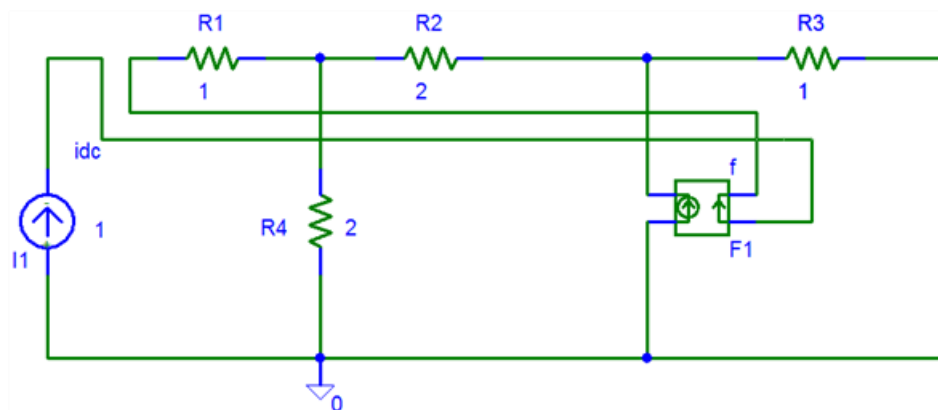


Figure 2

Step 5 of 9

Run the Schematic, the following is the schematic circuit with voltage and current values.

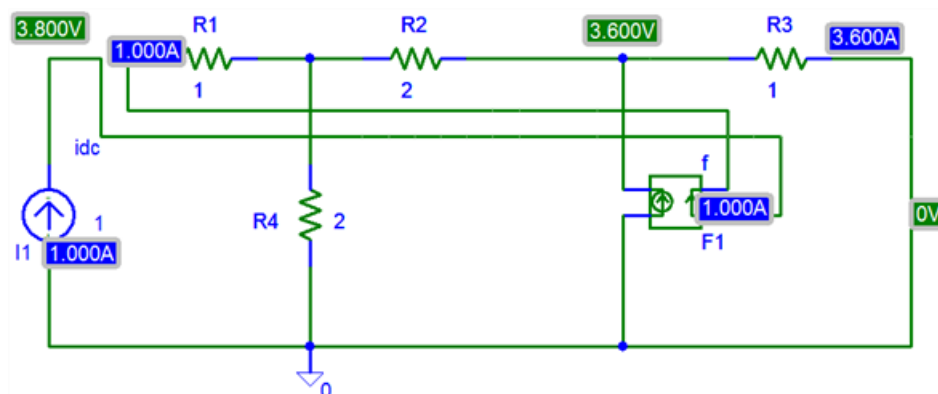


Figure 3

Step 6 of 9

From the Figure 3,

$$I_1 = 1 \text{ A}$$

$$I_2 = -3.6 \text{ A}$$

$$V_1 = 3.8 \text{ V}$$

$$V_2 = 0 \text{ V}$$

Substitute 3.8 V for V_1 in the equation (1).

$$\begin{aligned} h_{11} &= \left. \frac{V_1}{I_1} \right|_{V_2=0} \\ &= \frac{3.8}{1} \\ &= 3.8 \Omega \end{aligned}$$

Substitute 1 A for I_1 and -3.6 A for I_2 in the equation (3).

$$\begin{aligned} h_{21} &= \left. \frac{I_2}{I_1} \right|_{V_2=0} \\ &= \frac{-3.6}{1} \\ &= -3.6 \end{aligned}$$

Step 7 of 9

To calculate the values of h_{12} and h_{22} parameters, connect a 1 V test current source to output port and open circuit the input port.

The following is the PSpice schematic:

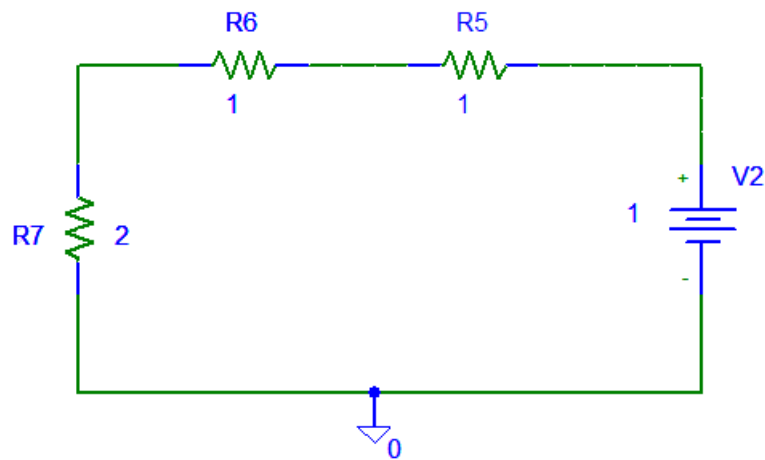


Figure 4

Step 8 of 9

Run the Schematic, the following is the schematic circuit with voltage and current values.

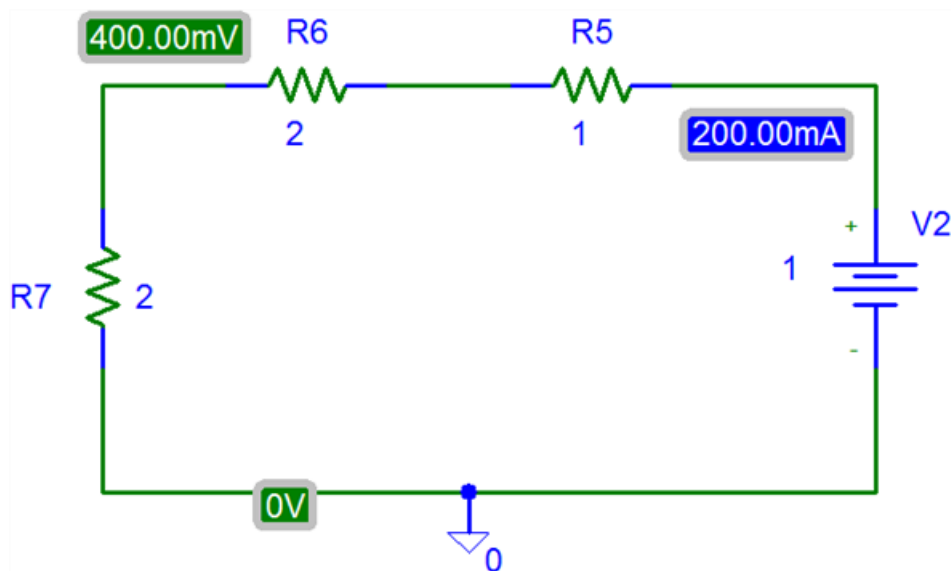


Figure 5

Step 9 of 9

From the Figure 5,

$$I_1 = 0 \text{ A}$$

$$I_2 = 200 \text{ mA}$$

$$V_1 = 400 \text{ mV}$$

$$V_2 = 1 \text{ V}$$

Substitute 400 mV for V_1 and 1 V for V_2 in the equation (2).

$$\begin{aligned} h_{12} &= \left. \frac{V_1}{V_2} \right|_{I_1=0} \\ &= \frac{400 \times 10^{-3}}{1} \\ &= 0.4 \end{aligned}$$

Substitute 200 mA for I_2 and 1 V for V_2 in the equation (4).

$$\begin{aligned} h_{22} &= \left. \frac{I_2}{V_2} \right|_{I_1=0} \\ &= \frac{200 \text{ mA}}{1 \text{ V}} \\ &= 0.2 \text{ S} \end{aligned}$$

Therefore, the hybrid parameters, $\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$ are $\begin{bmatrix} 3.8 \Omega & 0.4 \\ -3.6 & 0.2 \text{ S} \end{bmatrix}$.