

Problem

For the transistor network of Fig. 19.130,

$$\begin{array}{ll} h_{fe} = 80, & h_{ie} = 1.2 \text{ k}\Omega \\ h_{re} = 1.5 \times 10^{-4}, & h_{oe} = 20 \text{ }\mu\text{S} \end{array}$$

Determine the following:


(a) voltage gain $A_v = V_o/V_s$,

(b) current gain $A_i = I_o/I_i$,

(c) input impedance Z_{in} ,

(d) output impedance Z_{out} .

Figure 19.130

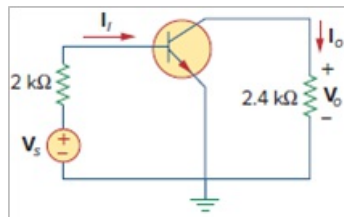

Step-by-step solution

Step 1 of 5

Consider the following circuit diagram:

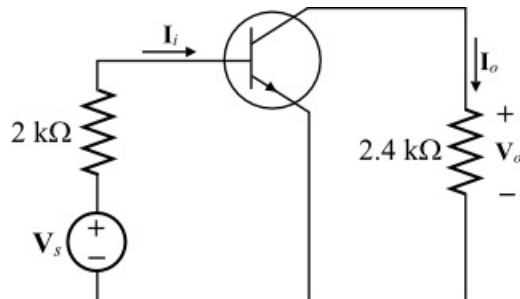


Figure 1

Step 2 of 5

(a)

Calculate the voltage gain of the transistor.

$$\begin{aligned} A_v &= \frac{V_o}{V_s} \\ &= \frac{-h_{fe}R_L}{h_{ie} + (h_{ie}h_{oe} - h_{re}h_{fe})R_L} \\ &= \frac{-(80)(2.4 \times 10^3)}{1200 + [(1200)(20 \times 10^{-6}) - (1.5 \times 10^{-4})(80)](2.4 \times 10^3)} \\ &= \frac{-192 \times 10^3}{1200 + [0.024 - 0.012](2.4 \times 10^3)} \\ &= \frac{-192 \times 10^3}{1200 + [0.012](2.4 \times 10^3)} \\ &= \frac{-192 \times 10^3}{1200 + 28.8} \\ &= \frac{-192 \times 10^3}{1228.8} \\ &= -156.25 \end{aligned}$$

Step 3 of 5

Therefore, the voltage gain for the transistor, A_v is -156.25.

Step 4 of 5

(b)

Calculate the current gain of the transistor.

$$\begin{aligned} A_i &= \frac{I_o}{I_i} \\ &= \frac{h_{fe}}{1 + h_{oe}R_L} \\ &= \frac{80}{1 + (20 \times 10^{-6})(2.4 \times 10^3)} \\ &= \frac{80}{1 + 0.048} \\ &= \frac{80}{1.048} \\ &= 76.33 \end{aligned}$$

Therefore, the current gain of the transistor, A_i is 76.33.

Step 5 of 5

(c)

Calculate the input impedance.

$$\begin{aligned}Z_{in} &= h_{ie} - \frac{h_{re}h_{fe}R_L}{1+h_{oe}R_L} \\&= 1200 - \frac{(10^{-4})(80)(2.4 \times 10^3)}{1+(20 \times 10^{-6})(2.4 \times 10^3)} \\&= 1200 - \frac{19.2}{1+0.048} \\&= 1200 - \frac{19.2}{1.048} \\&= 1200 - 18.32 \\&= 1181.68 \Omega\end{aligned}$$

Therefore, the input impedance, Z_{in} is $\boxed{1181.68 \Omega}$.

(d)

Calculate the output impedance.

$$\begin{aligned}Z_{out} &= \frac{R_s + h_{ie}}{(R_s + h_{ie})h_{oe} - h_{re}h_{fe}} \\&= \frac{2000 + 1200}{(2000 + 1200)(20 \times 10^{-6}) - (1.5 \times 10^{-4})(80)} \\&= \frac{3200}{0.064 - 0.012} \\&= \frac{3200}{0.052} \\&= 61.54 \text{ k}\Omega\end{aligned}$$

Therefore, the output impedance, Z_{out} is $\boxed{61.54 \text{ k}\Omega}$.