

Chapter 2, Problem 2RQ

Problem

An electric heater draws 10 A from a 120-V line. The resistance of the heater is:

- (a) 1200 Ω
- (b) 120 Ω
- (c) 12 Ω
- (d) 1.2 Ω

Step-by-step solution

Step 1 of 1

(C)
12 Ω