

Chapter 2, Problem 4RQ

Problem

The maximum current that a 2W, 80 kΩ resistor can safely conduct is:

- (a) 160 kA
- (b) 40 kA
- (c) 5 mA
- (d) 25 μA

Step-by-step solution

Step 1 of 3

Write the expression for power dissipated by a resistor R .

$$p = i^2 R$$

$$i^2 = \frac{p}{R}$$

$$i = \sqrt{\frac{p}{R}} \dots\dots (1)$$

Step 2 of 3

Determine the maximum value of current.

Substitute 2 W for p and 80 kΩ for R in equation (1).

$$\begin{aligned} i &= \sqrt{\frac{2}{80 \times 10^3}} \\ &= \sqrt{25 \times 10^{-6}} \\ &= 5 \times 10^{-3} \\ &= 5 \text{ mA} \end{aligned}$$

The current value (5 mA) does not match with option-(a), option-(b) and option-(d).

Hence, the options (a), (b) and (d) are wrong.

Step 3 of 3

From the calculations, the maximum current that a 2 W, 80 kΩ resistor can safely conduct is,

$$\boxed{5 \text{ mA}}.$$

Hence, the correct option is $\boxed{(c)}$.