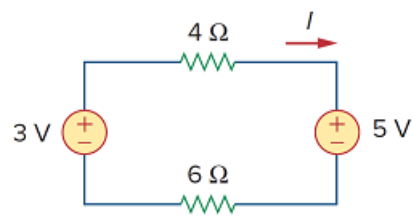


Problem

The current I in the circuit of Fig. 2.63 is:

- (a) -0.8 A
- (b) -0.2 A
- (c) 0.2 A
- (d) 0.8 A

Figure 2.63:




Step-by-step solution

Step 1 of 2

Refer to the circuit in Figure 2.63 in the textbook.

Redraw the circuit as shown in Figure 1.

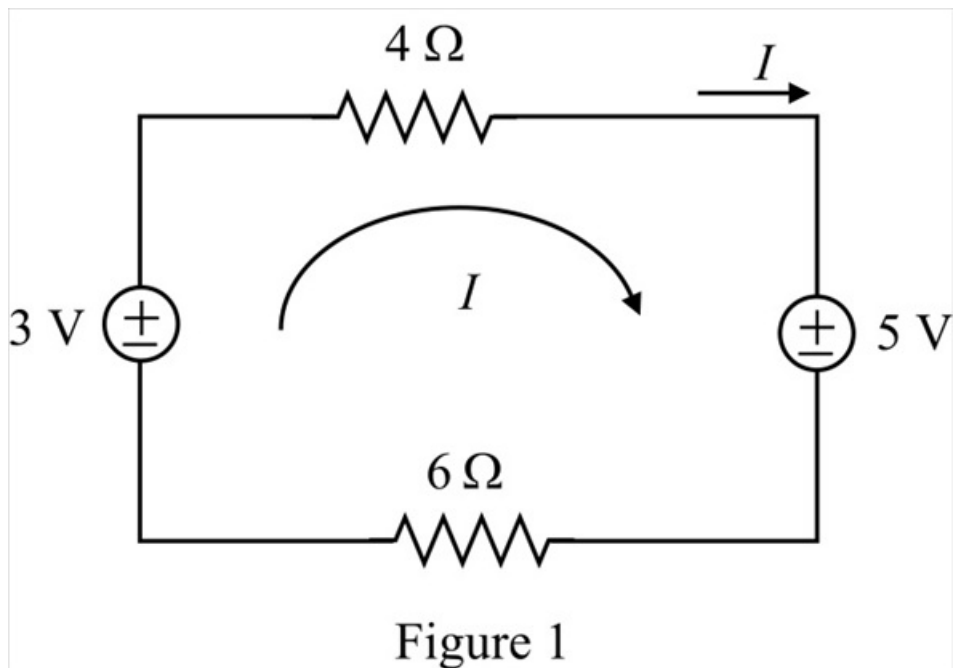

Step 2 of 2

Apply Kirchhoff's voltage law to the circuit in Figure 1.

$$-3 + 4I + 5 + 6I = 0$$

$$10I + 2 = 0$$

$$10I = -2$$

$$I = \frac{-2}{10}$$

$$= -0.2 \text{ A}$$

Thus, the value of current I is -0.2 A.