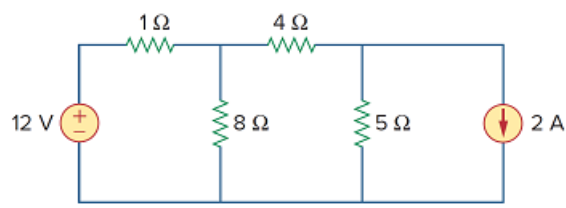


Problem

Determine the number of branches and nodes in the circuit of Fig. 2.71.


Figure 2.71:



Step-by-step solution


Step 1 of 1

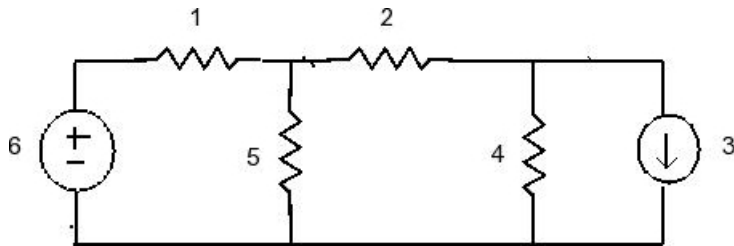Branches = any single element such as a voltage source or resistor



So, we have 6 total branches

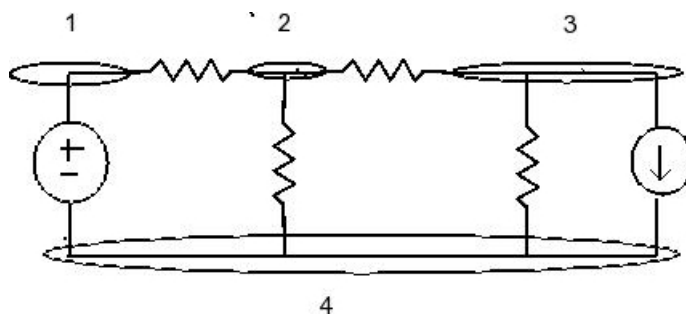Node = the point of connection between two or more branches



So, we have 4 nodes

6 branches and 4 nodes