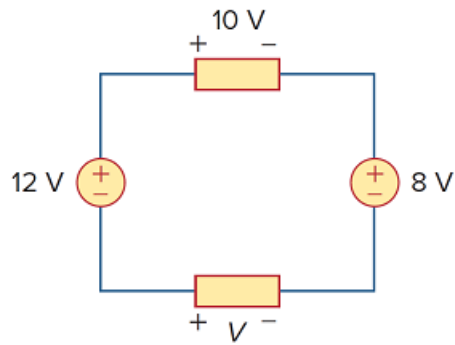


Problem

In the circuit in Fig. 2.65, V is:

- (a) 30 V
- (b) 14 V
- (c) 10 V
- (d) 6 V

Figure 2.65:




Step-by-step solution

Step 1 of 2

Refer to the circuit diagram in Figure 2.65 in the textbook.

Redraw the circuit diagram.

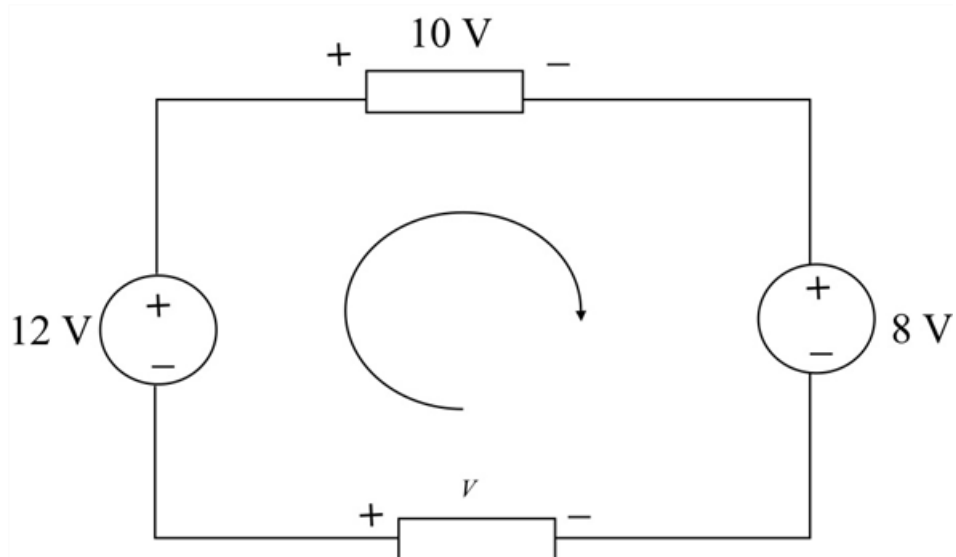

Step 2 of 2

Apply Kirchhoff's voltage law around loop.

$$-12 \text{ V} + 10 \text{ V} + 8 \text{ V} - V = 0$$

$$V = 6 \text{ V}$$

Thus, correct option is **d** or **6 V**.