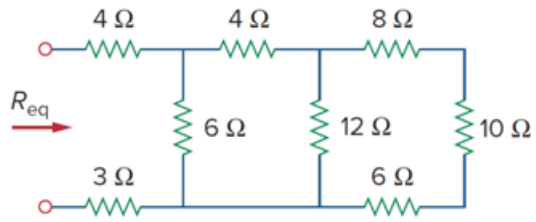


Problem

By combining the resistors in Fig. 2.36, find R_{eq} .

Figure 2.36:



Step-by-step solution

Step 1 of 4

Consider the circuit of textbook Figure 2.36. The resistors $8\ \Omega$, $10\ \Omega$ and $6\ \Omega$ are in series. Therefore, their equivalent resistance is,

$$8\ \Omega + 10\ \Omega + 6\ \Omega = 24\ \Omega$$

The resultant diagram is as shown in Figure 1.

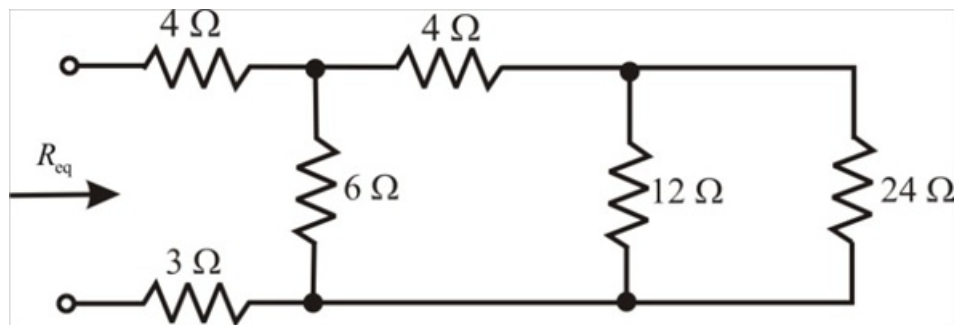


Figure 1

Step 2 of 4

The resistors 24Ω and 12Ω in Figure 1 are in parallel. Therefore their equivalent resistance is,

$$(12 \parallel 24) = \frac{(12)(24)}{36} \\ = 8 \Omega$$

The resultant diagram is as shown in Figure 2.

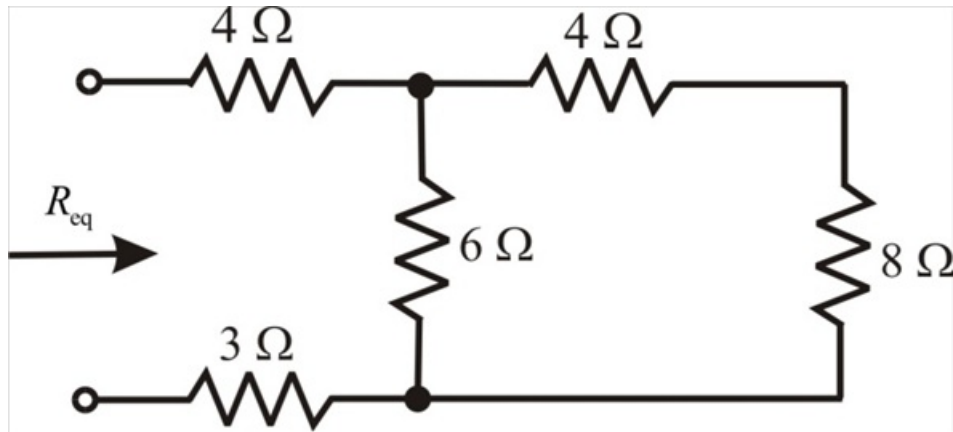


Figure 2

Step 3 of 4

The resistors 4Ω and 8Ω are in series and the resultant is in parallel to 6Ω . Therefore their equivalent resistance is,

$$[(8+6) \parallel 6] = 12 \parallel 6 \\ = \frac{(12)(6)}{18} \\ = 4 \Omega$$

The resultant diagram is as shown in Figure 3.

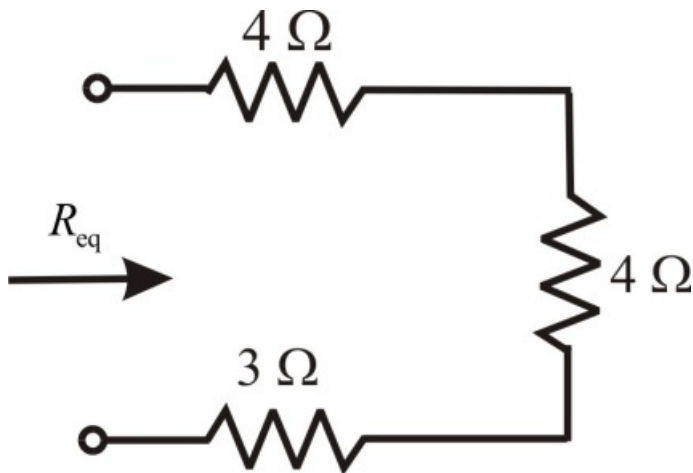


Figure 3

Step 4 of 4

The equivalent resistance of Figure 3 is,

$$R_{eq} = 4 + 4 + 3 \\ = 11 \Omega$$

Therefore, the equivalent resistance of the textbook Figure 2.36 is $R_{eq} = 11 \Omega$.