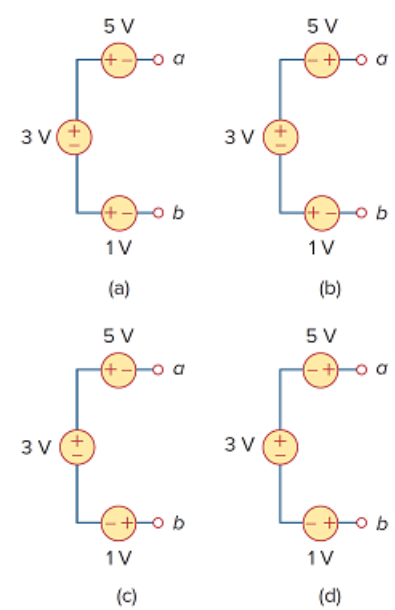


Problem

Which of the circuits in Fig. 2.66 will give you $V_{ab} = 7\text{ V}$?

Figure 2.66:



Step-by-step solution

Step 1 of 1

Answer: (d)

