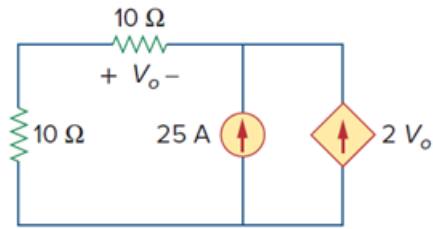


Problem

Find V_o in the circuit in Fig. 2.86 and the power absorbed by the dependent source.

Figure 2.86:



Step-by-step solution

Step 1 of 5

Refer to Figure 2.86 in the textbook.

Draw the circuit diagram with voltage notations.

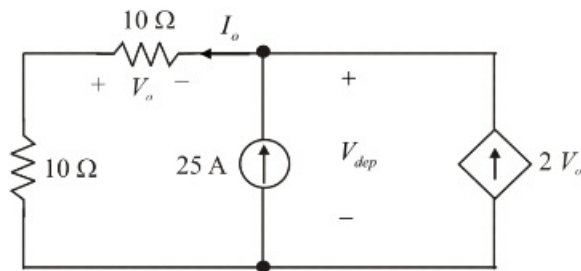


Figure 1

Step 2 of 5

Use Ohm's law to Figure 1, the voltage across top $10\ \Omega$ resistor is,

$$V_o = -10I_o \dots\dots (1)$$

Apply Kirchhoff's current law to Figure 1 and calculate the current, i_o .

$$25 + 2V_o = I_o$$

Substitute $-10I_o$ for V_o .

$$25 + 2(-10I_o) = I_o$$

$$25 - 20I_o = I_o$$

$$21I_o = 25$$

$$I_o = \frac{25}{21}$$

$$I_o = 1.19\text{ A}$$

Step 3 of 5

Substitute 1.19 A for I_o in equation (1).

$$\begin{aligned}V_o &= -10(1.19) \\ &= -11.9\text{ V}\end{aligned}$$

Therefore, the voltage, V_o is $\boxed{-11.9\text{ V}}$.

Step 4 of 5

Apply Kirchhoff's voltage law to Figure 1.

$$\begin{aligned}-V_{dep} + 10I_o + 10I_o &= 0 \\ V_{dep} &= 20I_o\end{aligned}$$

Substitute 1.19 A for I_o .

$$\begin{aligned}V_{dep} &= 20(1.19) \\ &= 23.8\text{ V}\end{aligned}$$

Step 5 of 5

The power absorbed by the dependent source is,

$$P_{dep} = -V_{dep}(2V_o)$$

Substitute 23.8 V for V_{dep} and -11.9 V for V_o .

$$\begin{aligned}P_{dep} &= -(23.8)((2)(-11.9)) \\ &= 566.44\text{ W}\end{aligned}$$

Therefore, the power absorbed by the dependent source is $\boxed{566.44\text{ W}}$.