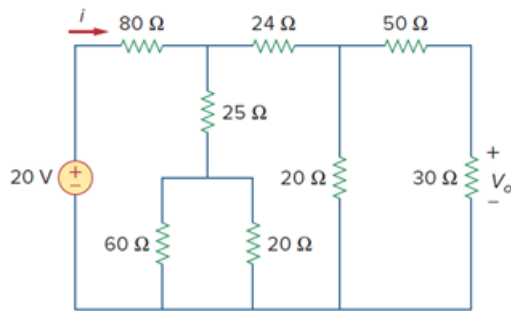


Problem

Find i and V_o in the circuit of Fig. 2.100.

Figure 2.100:



Step-by-step solution

Step 1 of 8

Consider the following circuit diagram:

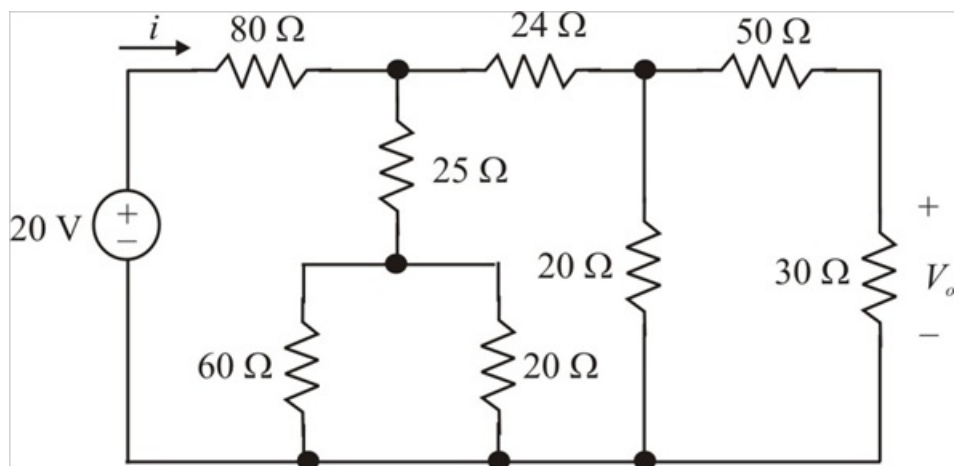


Figure 1

Step 2 of 8

The 50 Ω and 30 Ω resistors are in series. Their combined resistance is,

$$50\Omega + 30\Omega = 80\Omega$$

The 20 Ω and 60 Ω resistors are in parallel. Their combined resistance is,

$$20\Omega \parallel 60\Omega = \frac{20 \times 60}{20 + 60} \\ = 15\Omega$$

Step 3 of 8

Then the reduced circuit is shown in Figure 2.

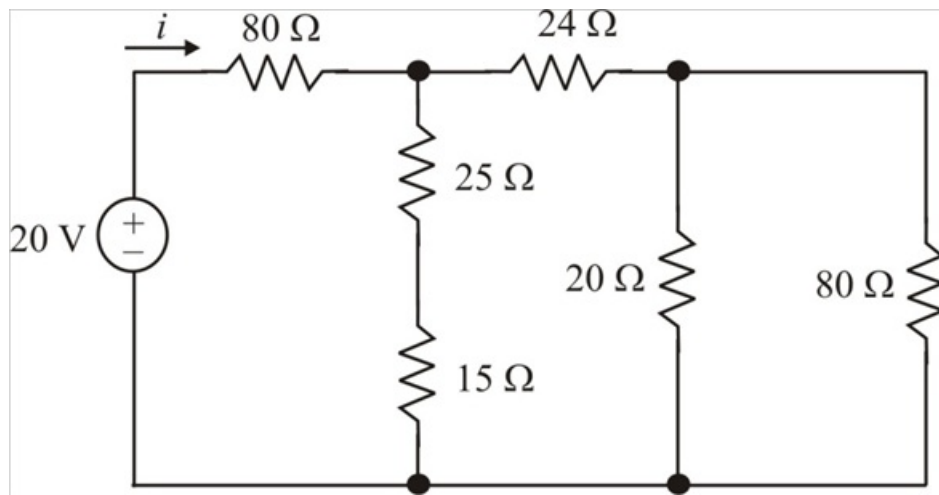


Figure 2

Step 4 of 8

The 15 Ω and 25 Ω resistors are in series. Their combined resistance is,

$$15\Omega + 25\Omega = 40\Omega$$

The 20 Ω and 80 Ω resistors are in parallel. Their combined resistance is,

$$\begin{aligned} 20\Omega \parallel 80\Omega &= \frac{20 \times 80}{20 + 80} \\ &= 16\Omega \end{aligned}$$

Step 5 of 8

Then the reduced circuit is shown in Figure 3.

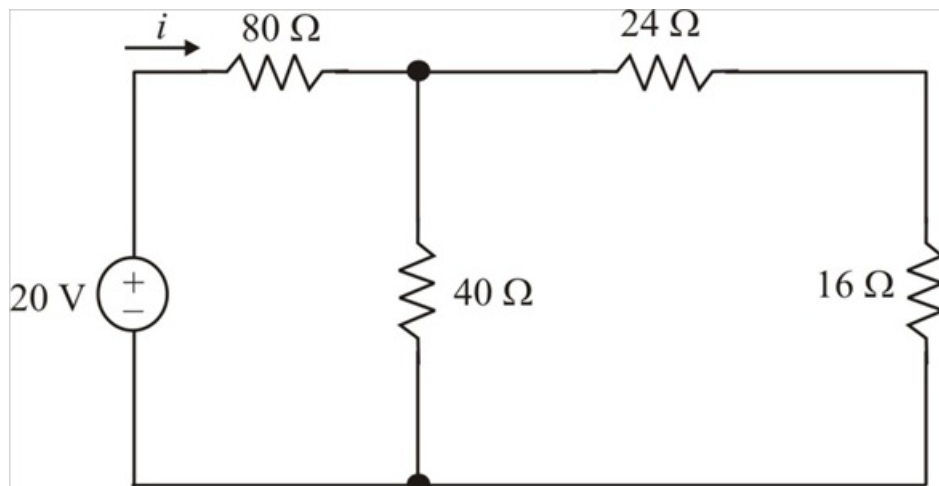


Figure 3

Step 6 of 8

The 16 Ω and 24 Ω resistors are in series. Their combined resistance is,

$$16\Omega + 24\Omega = 40\Omega$$

This 40 Ω and 40 Ω resistors are in parallel. Their combined resistance is,

$$40\Omega \parallel 40\Omega = \frac{40 \times 40}{40 + 40} \\ = 20\Omega$$

This 20 Ω and 80 Ω resistors are in series. Their combined resistance is,

$$20\Omega + 80\Omega = 100\Omega$$

By using Ohms law, the current i can be calculated as follows.

$$i = \frac{V}{R} \\ = \frac{20}{100} \\ = 200\text{mA}$$

Therefore, the value of current i is 200mA.

Step 7 of 8

Consider the following circuit diagram.

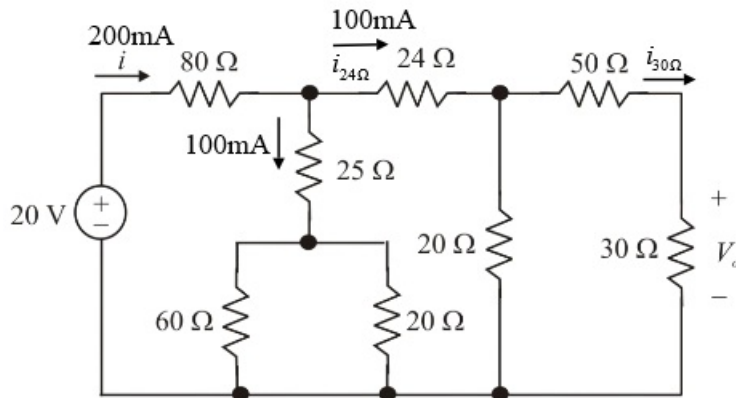


Figure 4

Step 8 of 8

Since the two branch resistances are equal 40 Ω and 40 Ω , the current is divided equally. Hence the current through the 24 Ω resistor is 100mA.

Apply current division rule, the current passing through 30 Ω resistor is,

$$i_{30\Omega} = \frac{20}{20 + 80} i_{24\Omega} \\ = \frac{20}{20 + 80} (100\text{mA}) \\ = 20\text{mA}$$

By using Ohms law, the current V_o can be calculated as follows.

$$V_o = i_{30\Omega} R \\ = (20\text{mA})(30) \\ = 0.6\text{V}$$

Therefore, the value of voltage, V_o is 0.6V.