

Problem

If the three bulbs of Prob. 2.59 are connected in parallel to the 120-V source, calculate the current through each bulb.

Step-by-step solution

Step 1 of 2

Three bulbs of 40 W, 60 W and 100 W are connected in parallel to 120 V source. The circuit is as shown in Figure 1.

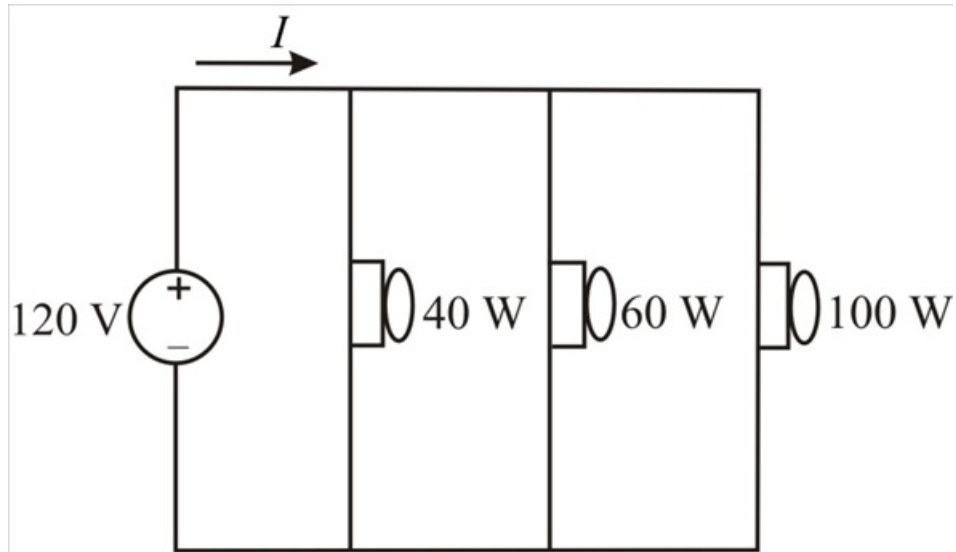


Figure 1

Step 2 of 2

The current through 40 W bulb is,

$$\begin{aligned} I_{40\text{ W}} &= \frac{P_{40\text{ W}}}{120} \\ &= \frac{40}{120} \\ &= 0.33 \text{ A} \end{aligned}$$

The current through 60 W bulb is,

$$\begin{aligned} I_{60\text{ W}} &= \frac{P_{60\text{ W}}}{120} \\ &= \frac{60}{120} \\ &= 0.5 \text{ A} \end{aligned}$$

The current through 100 W bulb is,

$$\begin{aligned} I_{100\text{ W}} &= \frac{P_{100\text{ W}}}{120} \\ &= \frac{100}{120} \\ &= 0.833 \text{ A} \end{aligned}$$

Therefore, the currents through the bulbs are $I_{40\text{ W}} = 0.33\text{ A}$, $I_{60\text{ W}} = 0.5\text{ A}$, $I_{100\text{ W}} = 0.833\text{ A}$.